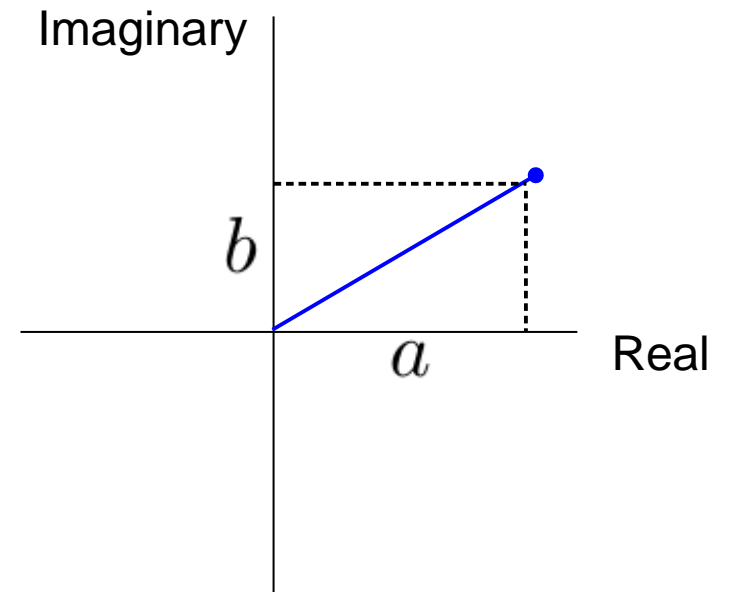


# **Lab 3: Capacitors and Inductors in AC circuits**

# Review of Complex Numbers

$$j = \sqrt{-1}$$

$$z = a + jb$$




# Review of Complex Numbers

$$j = \sqrt{-1}$$

$$z = a + jb = Ae^{j\phi}$$

$$A = \sqrt{a^2 + b^2}$$
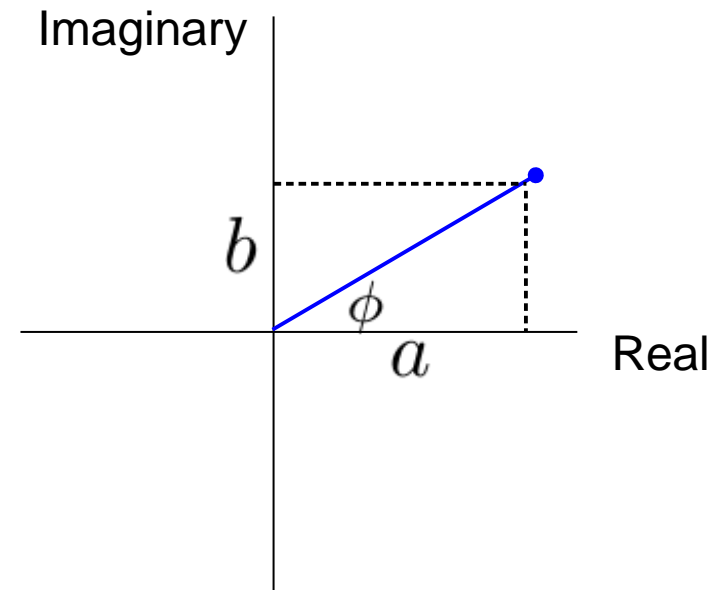
$$\phi = \tan^{-1} \left( \frac{b}{a} \right)$$



# Review of Complex Numbers

$$j = \sqrt{-1}$$


$$z = a + jb = Ae^{j\phi}$$

$$A = \sqrt{a^2 + b^2}$$

$$\phi = \tan^{-1} \left( \frac{b}{a} \right)$$


$$e^{j\phi} = \cos \phi + j \sin \phi$$
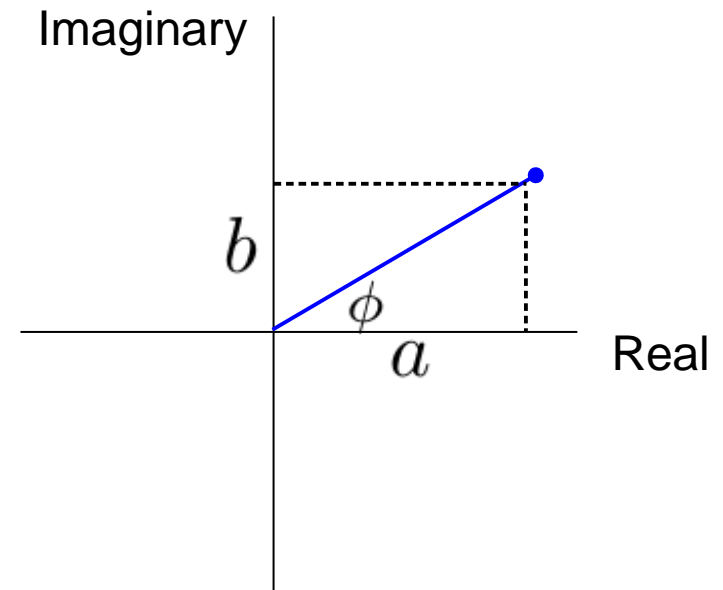
$$e^{j\frac{\pi}{2}} = \cos\left(\frac{\pi}{2}\right) + j \sin\left(\frac{\pi}{2}\right) = j$$



OUR ESSENTIAL WORKING ASSUMPTION:

**AC  $\equiv$  SINUSOIDAL FUNCTION**

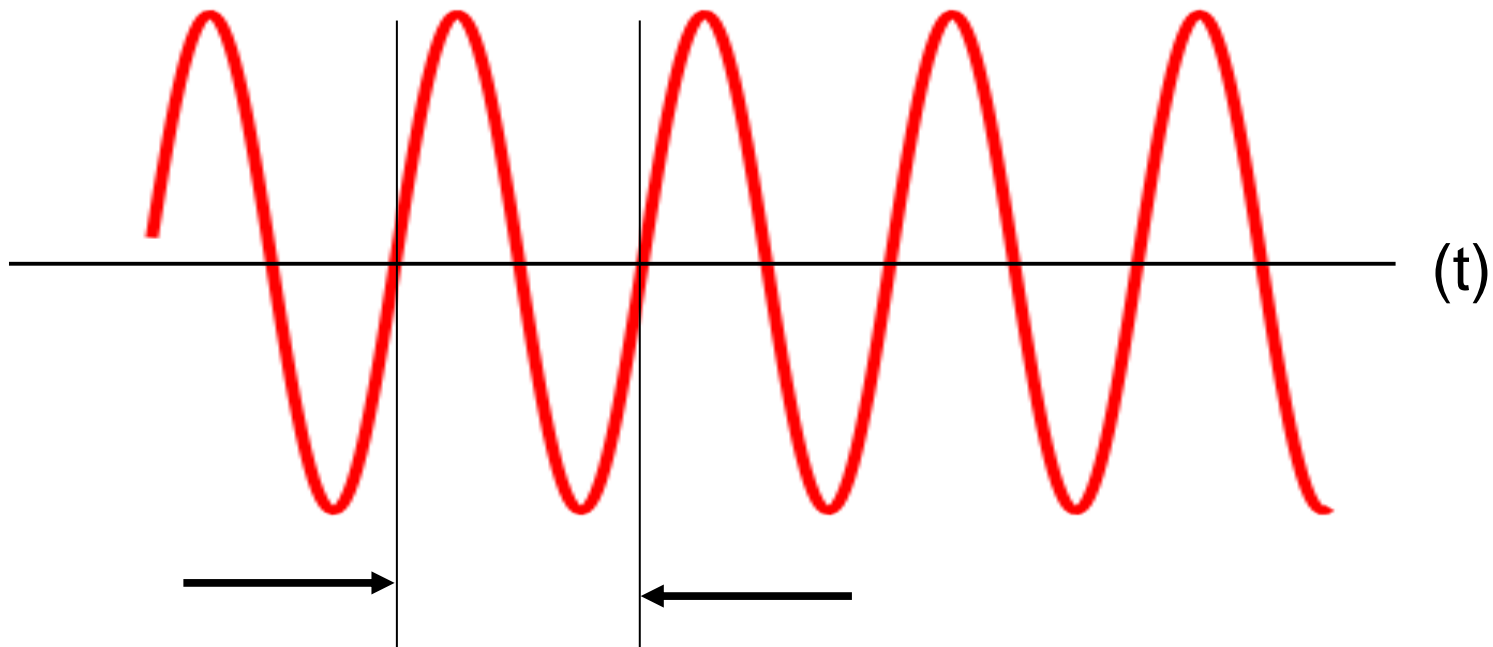

*T: Period*

*Frequency:  $f = 1/T$*

# Capacitor in AC circuit

$$V_{ac} = V_o \sin \omega t$$

$$\omega = 2\pi f$$

$\omega$  : radians/sec  
 $f$  : Herz (1/sec)



# Capacitor in AC circuit

$$V_{ac} = V_o \sin \omega t$$




$$\omega = 2\pi f$$


$\omega$  : radians/sec  
 $f$  : Herz (1/sec)

**VOLTAGE**

**CURRENT**

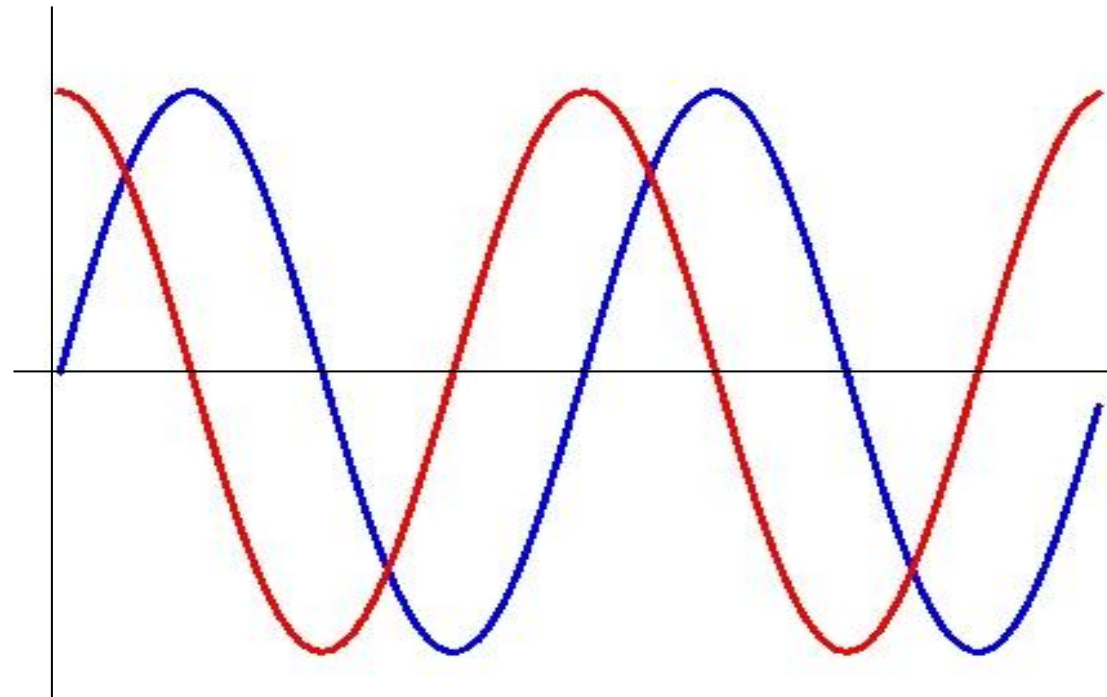


# Inductor in AC circuit

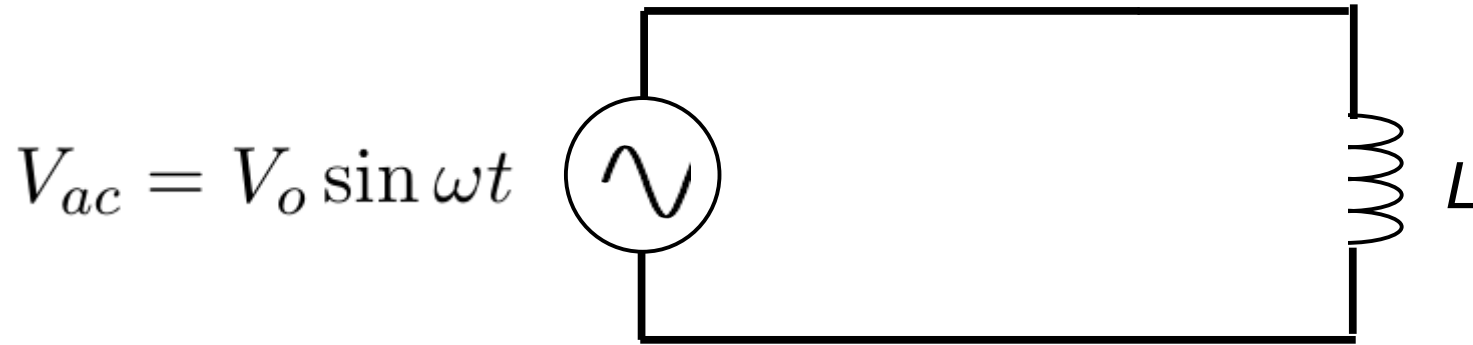




# Inductor in AC circuit

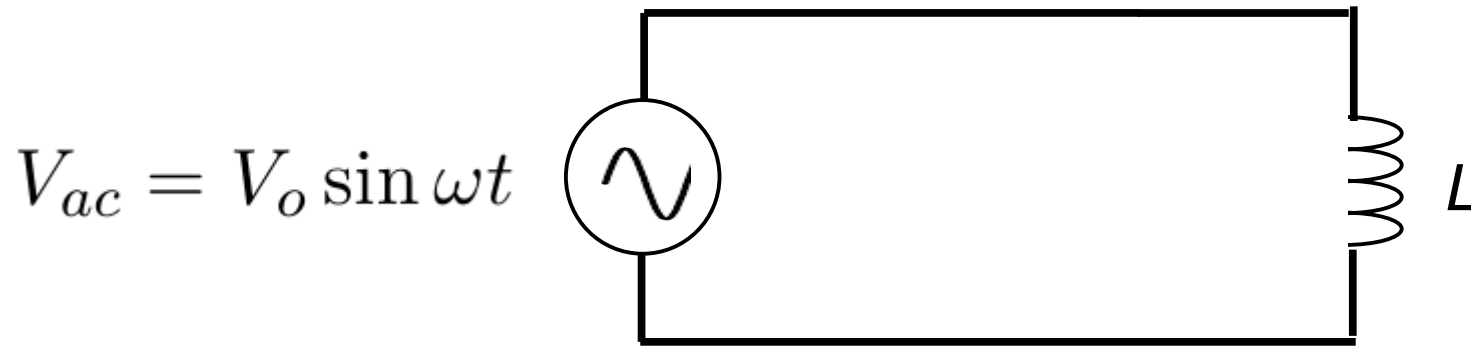


**VOLTAGE**


**CURRENT**

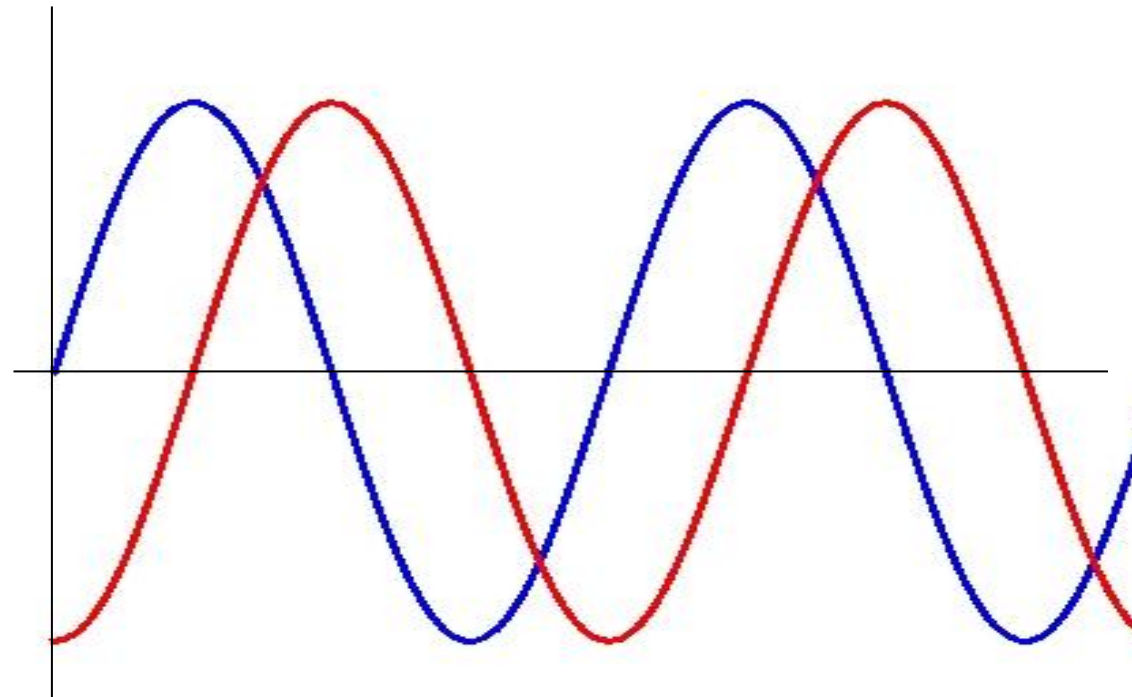

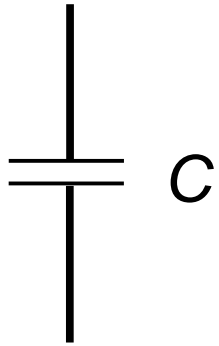
# Ohm's Law for L and C: Impedance ( $Z$ )



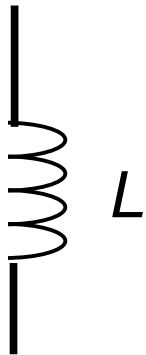
$$Z_C = \frac{V_C}{I_C} = \frac{V_o \sin \omega t}{\omega C V_o \cos \omega t} = \frac{V_o \sin \omega t}{\omega C V_o \sin \left( \omega t + \frac{\pi}{2} \right)}$$


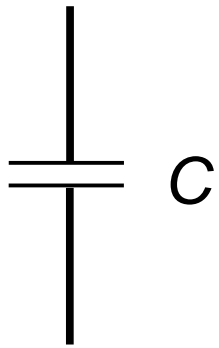
# Ohm's Law for L and C: Impedance ( $Z$ )



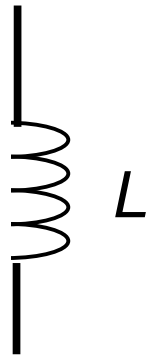
$$Z_C = \frac{V_C}{I_C} = \frac{V_o \sin \omega t}{\omega C V_o \cos \omega t} = \frac{V_o \sin \omega t}{\omega C V_o \sin \left( \omega t + \frac{\pi}{2} \right)}$$




$$Z_L = \frac{V_L}{I_L} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \cos \omega t} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \sin \left( \omega t + \frac{\pi}{2} \right)}$$
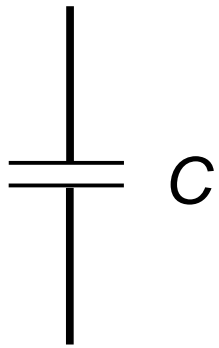
# Ohm's Law for L and C: Impedance ( $Z$ )



$$Z_C = \frac{V_C}{I_C} = \frac{V_o \sin \omega t}{\omega C V_o \cos \omega t} = \frac{V_o \sin \omega t}{\omega C V_o \sin \left( \omega t + \frac{\pi}{2} \right)}$$


90° phase shift

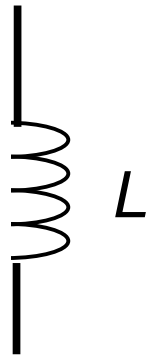


$$Z_L = \frac{V_L}{I_L} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \cos \omega t} = \frac{V_o \sin \omega t}{-(V_o/\omega L) \sin \left( \omega t + \frac{\pi}{2} \right)}$$

90° phase shift
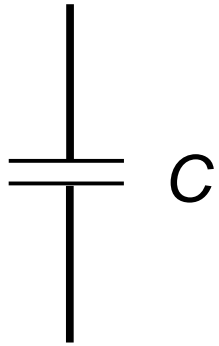
# Ohm's Law for L and C: Impedance ( $Z$ )



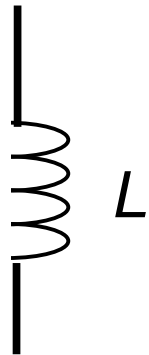
$$Z_C = \frac{V_C}{I_C} = \frac{1}{j\omega C}$$



$$Z_L = \frac{V_L}{I_L} = \frac{\omega L}{-j} = j\omega L$$


90° phase-shift in polar form:  $e^{j\frac{\pi}{2}} = \cos\left(\frac{\pi}{2}\right) + j \sin\left(\frac{\pi}{2}\right) = j$

# Impedance of a Resistor:

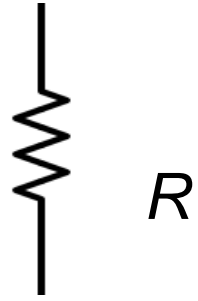


$$Z_R = \frac{V_R}{I_R} = R$$
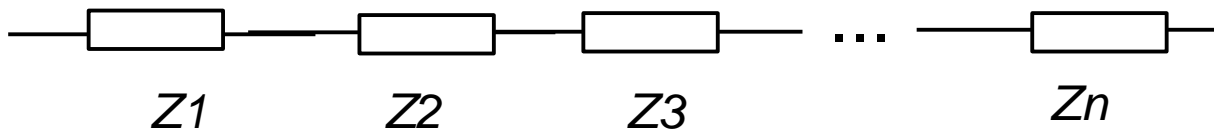
# Impedance arithmetic: same as a resistor




$$Z_{total} = \sum_i^n Z_i$$

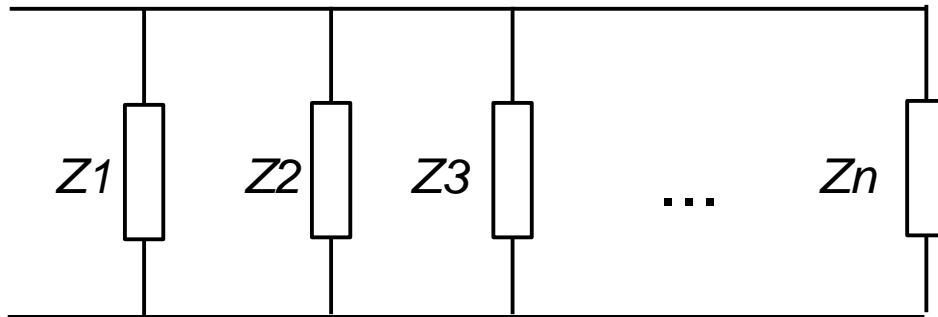

$$\frac{1}{Z_{total}} = \sum_i^n \frac{1}{Z_i}$$

# EXAMPLE 1

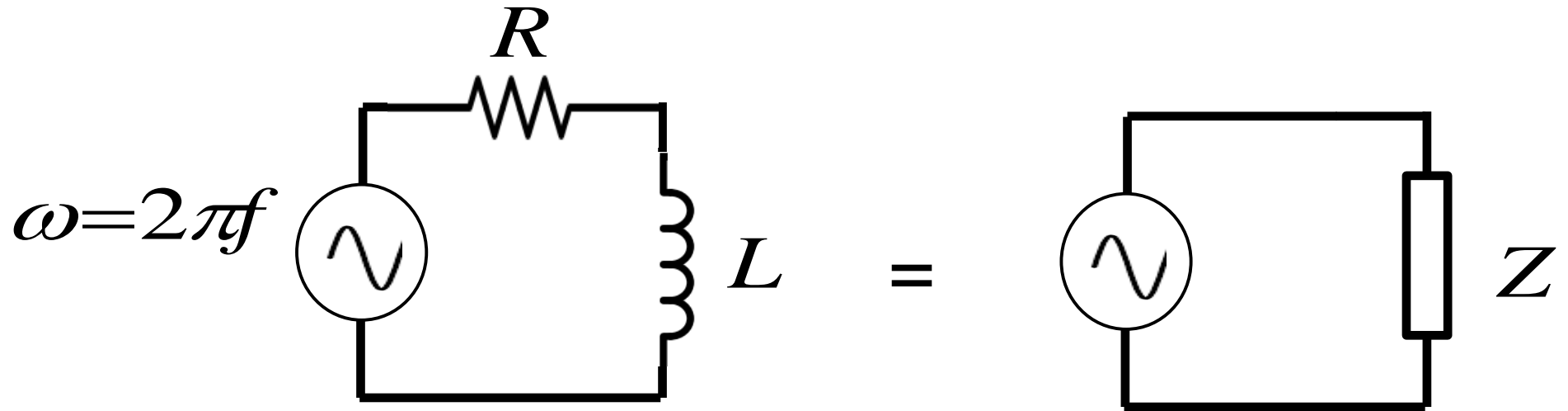


$$Z = Z_R + Z_L = R + j\omega L$$

Resistance

Reactance




# EXAMPLE 2

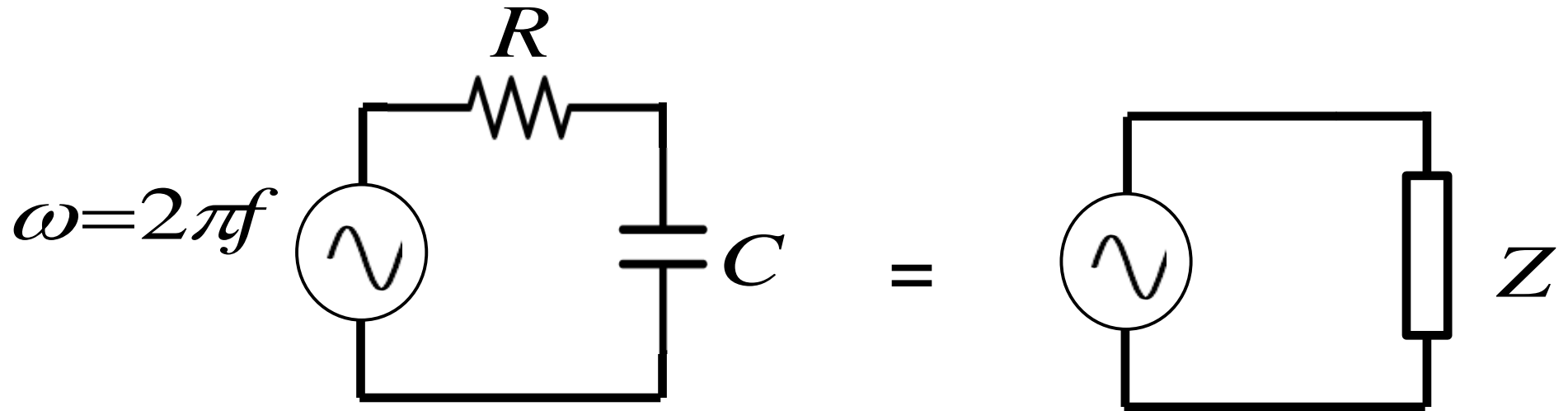

$$Z = Z_R + Z_L = R - \frac{j}{\omega C}$$


Resistance      Reactance

# EXAMPLE 3: Voltage Divider

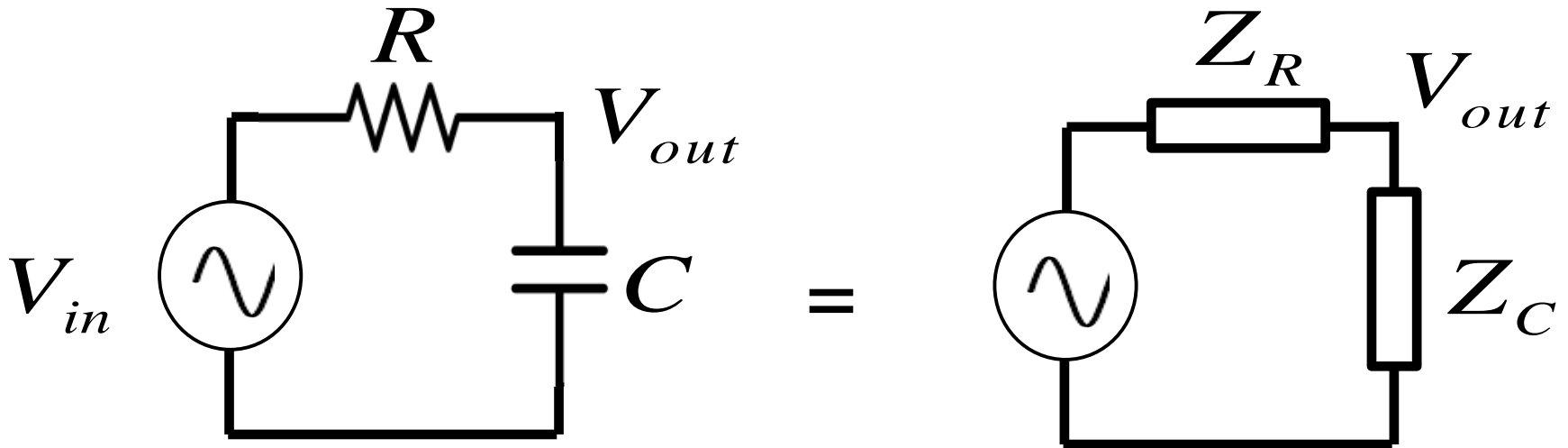


$$\frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_R + Z_C} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

# EXAMPLE 4: Voltage Divider

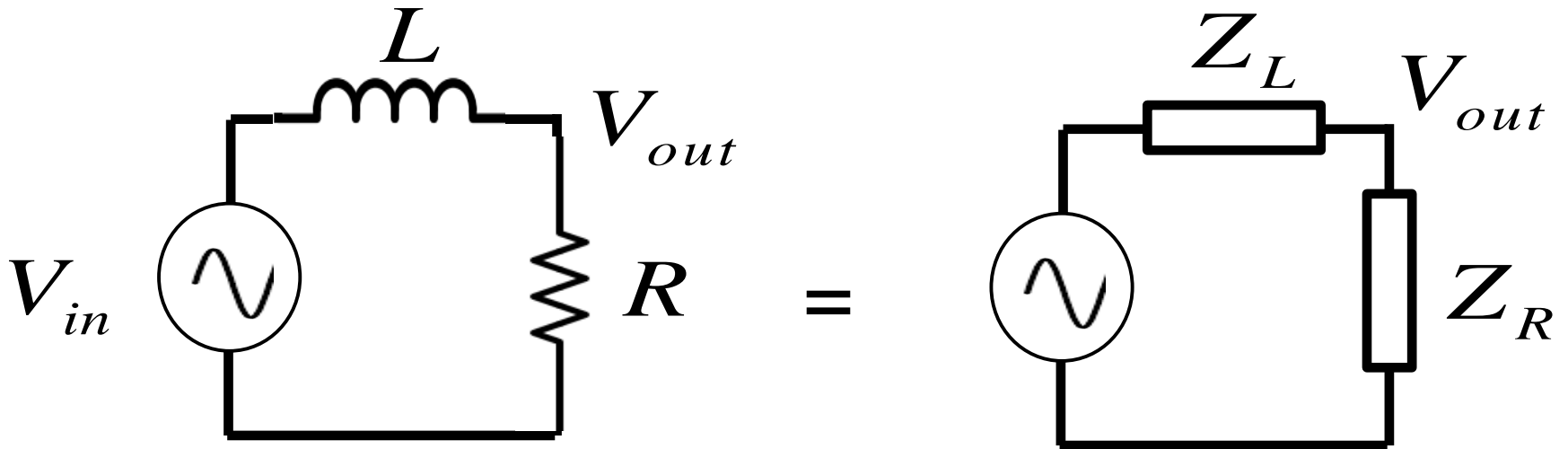

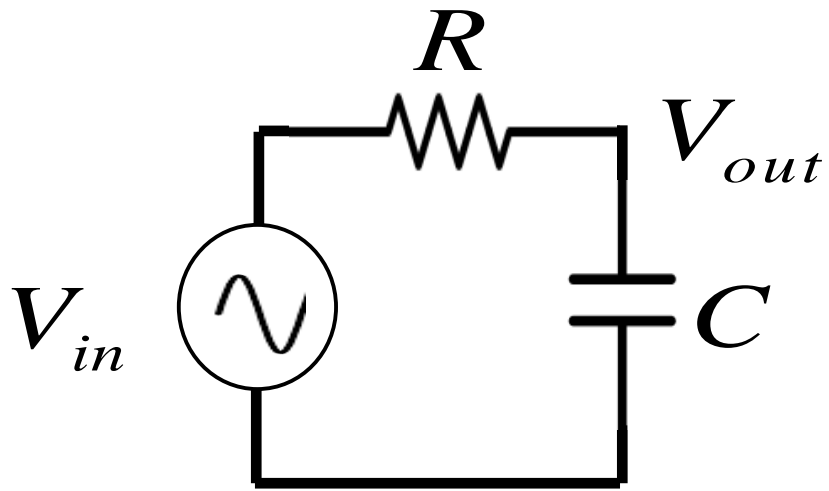
$$\frac{V_{out}}{V_{in}} = \frac{Z_R}{Z_R + Z_L} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$



$R = 217.8 \Omega$   
 $C = 145.6 \text{ nF}$

### AMPLITUDE

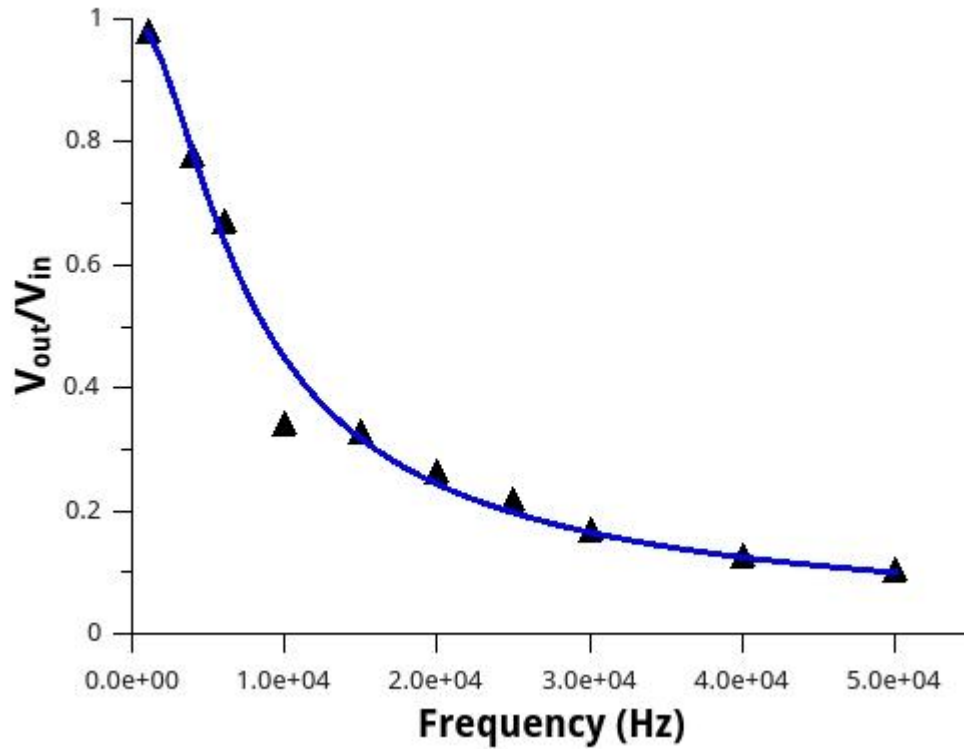

### PHASE

