

Lab 4: AC circuits (II)

REVIEW

AC analysis of circuits using complex numbers


Assumptions:

i) Steady-state


ii) Sinusoidal waveforms: $V_o \sin \omega t$

Ohm's Law for L and C:

Impedance (Z) Measured in ohms

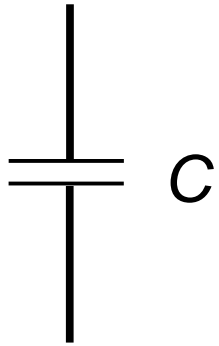

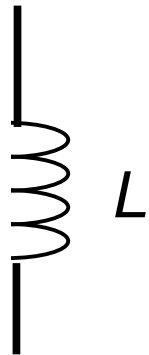
$$Z_C = \frac{V_C}{I_C} = \frac{1}{j\omega C}$$



$$Z_L = \frac{V_L}{I_L} = \frac{\omega L}{-j} = j\omega L$$


90o phase-shift in polar form: $e^{j\frac{\pi}{2}} = \cos\left(\frac{\pi}{2}\right) + j \sin\left(\frac{\pi}{2}\right) = j$

AC circuit: High-pass


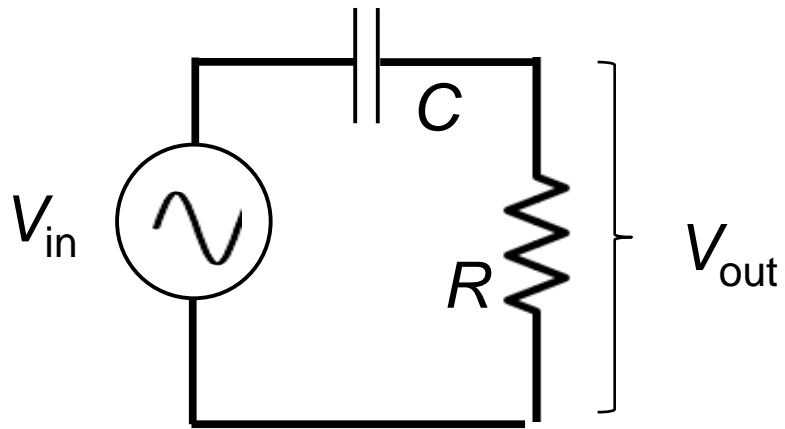


$$\frac{V_{OUT}(\omega)}{V_{IN}(\omega)} = \frac{R}{R + 1/j\omega C}$$

AC circuit: High-pass

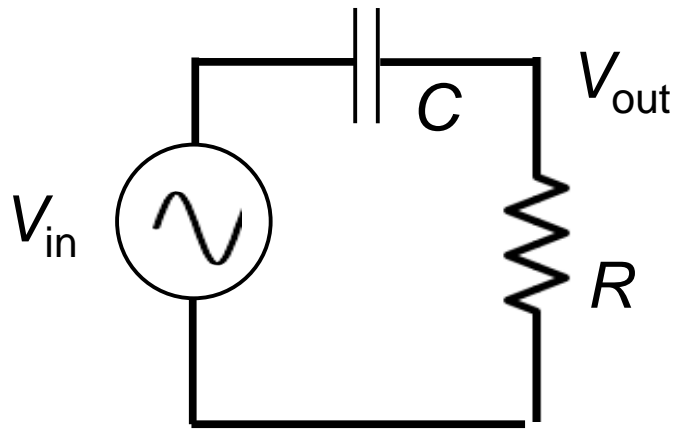

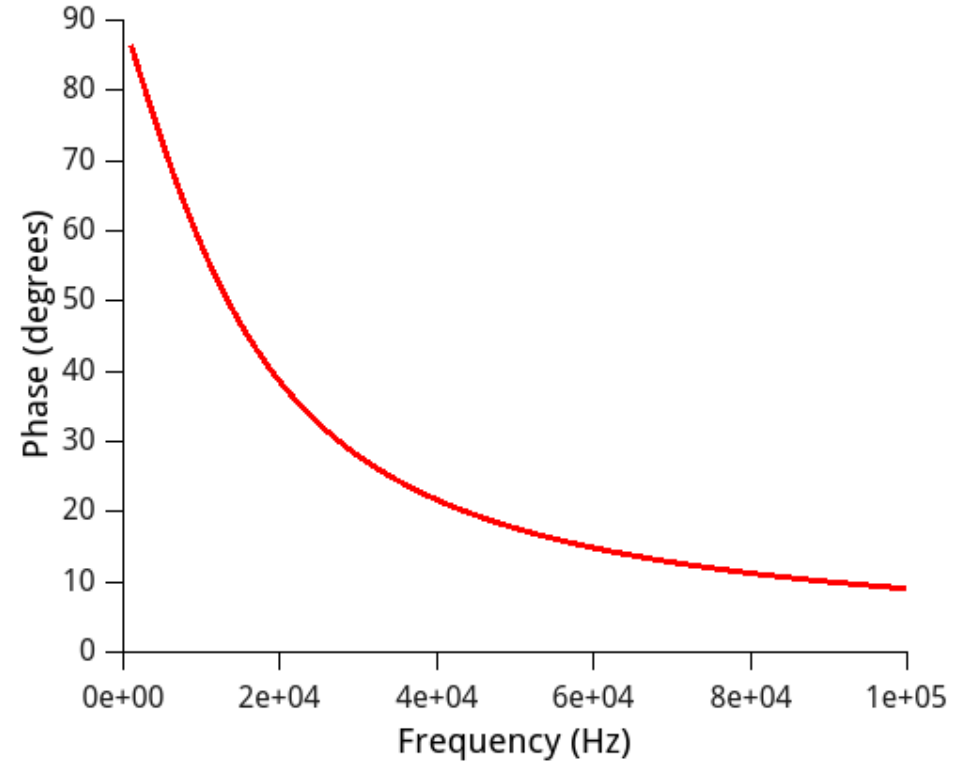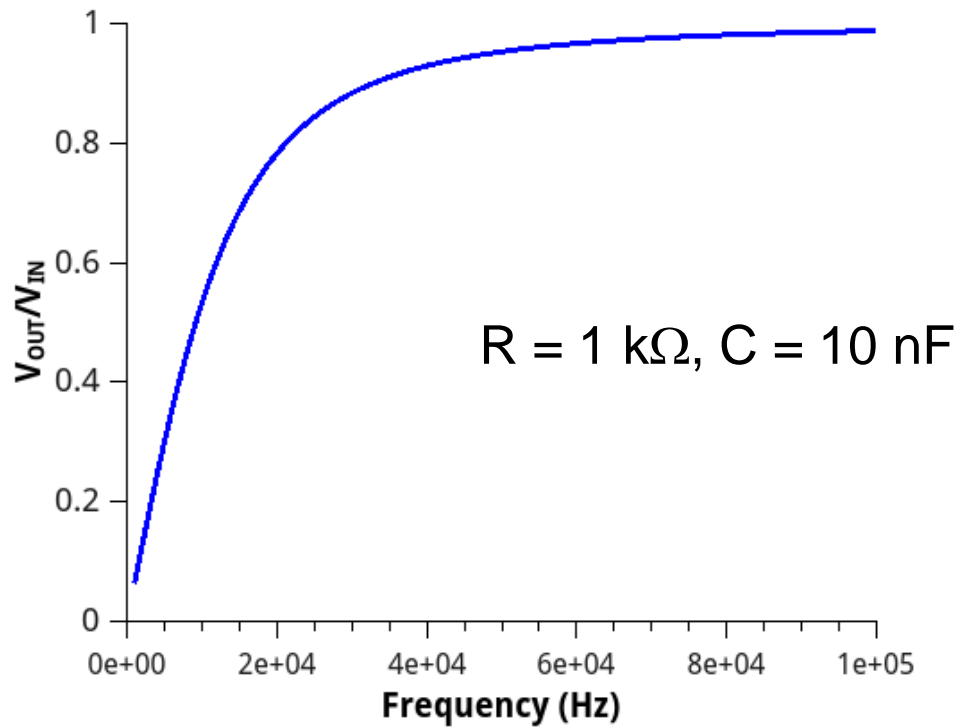
$$\frac{V_{OUT}(\omega)}{V_{IN}(\omega)} = \frac{R}{R + 1/j\omega C}$$




The Bode Plot for $|V_{out}/V_{in}|$



HW Bode
1905—1982
Bell Labs

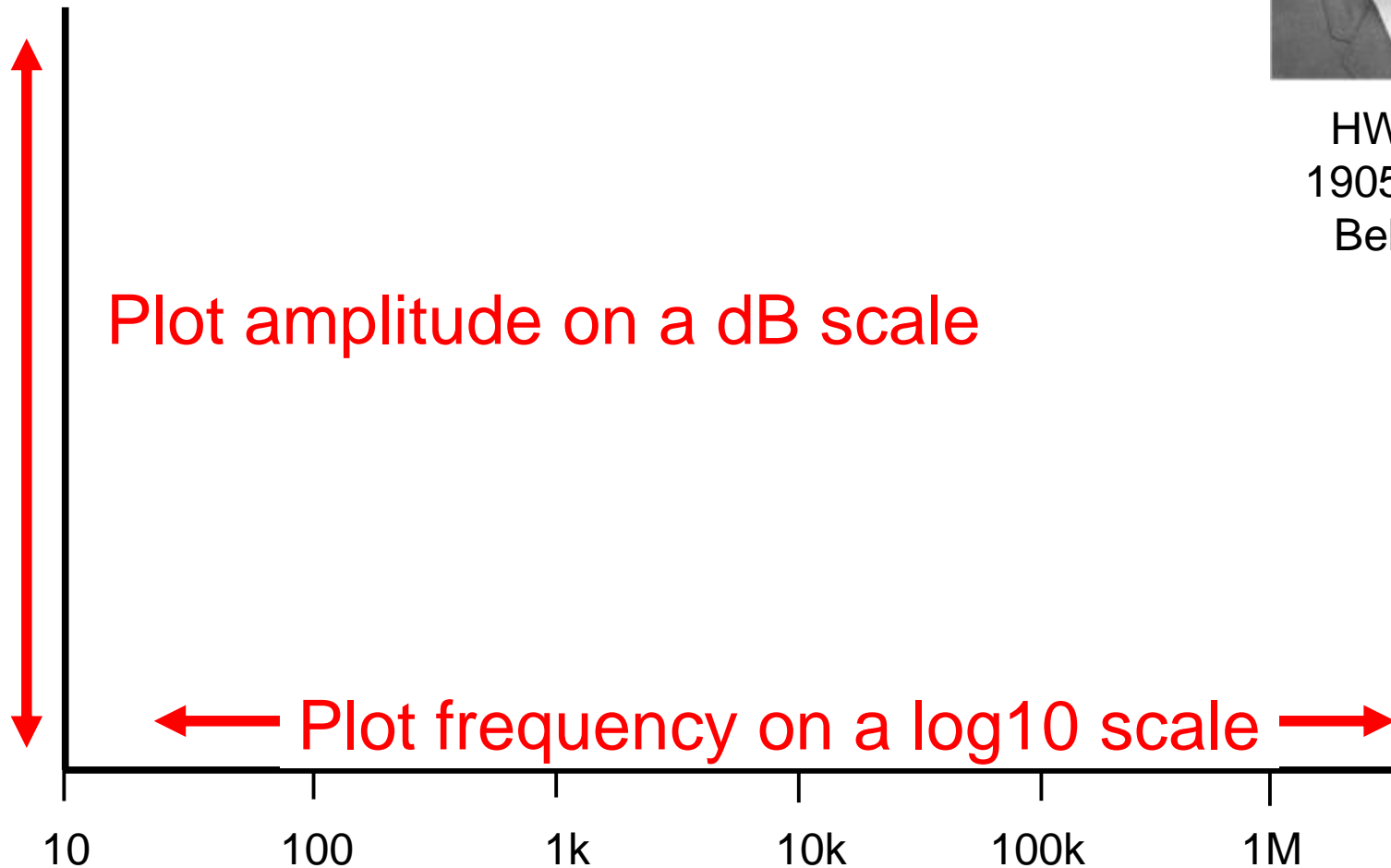

The Decibel: A Ratio

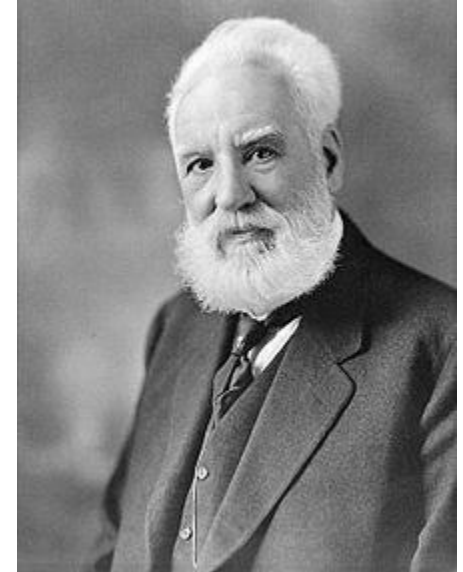


In honor of
Alexander Graham Bell

RATIO	POWER $10 \log_{10} \left\{ \frac{P_{\text{signal}}}{P_{\text{ref}}} \right\}$	FIELD $20 \log_{10} \left\{ \frac{A_{\text{signal}}}{A_{\text{ref}}} \right\}$
1	0 dB	0 dB
10	10 dB	20 dB
100	20 dB	40 dB
2	3 dB	6 dB
0.01	-20 dB	-40 dB

$$\text{dBm: } 10 \log_{10} \left\{ \frac{P_{\text{signal}}}{1 \text{ mW}} \right\}$$


$$0 \text{ dBm} = 1 \text{ mW}$$

AC circuit: High-pass

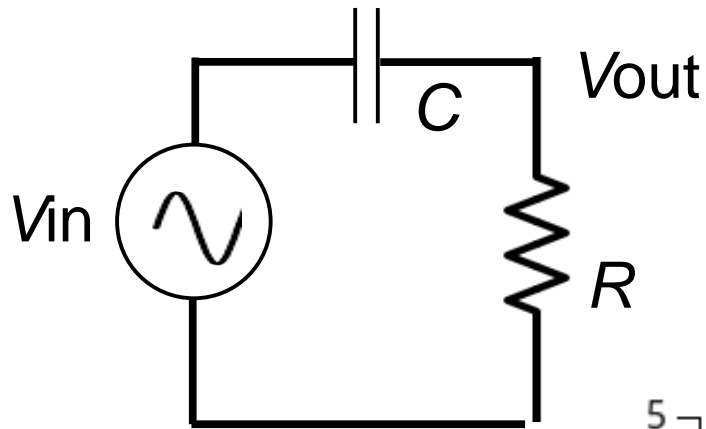


$$\frac{V_{OUT}(\omega)}{V_{IN}(\omega)} = \frac{R}{R + 1/j\omega C}$$

Bode Plot: AMPLITUDE RESPONSE

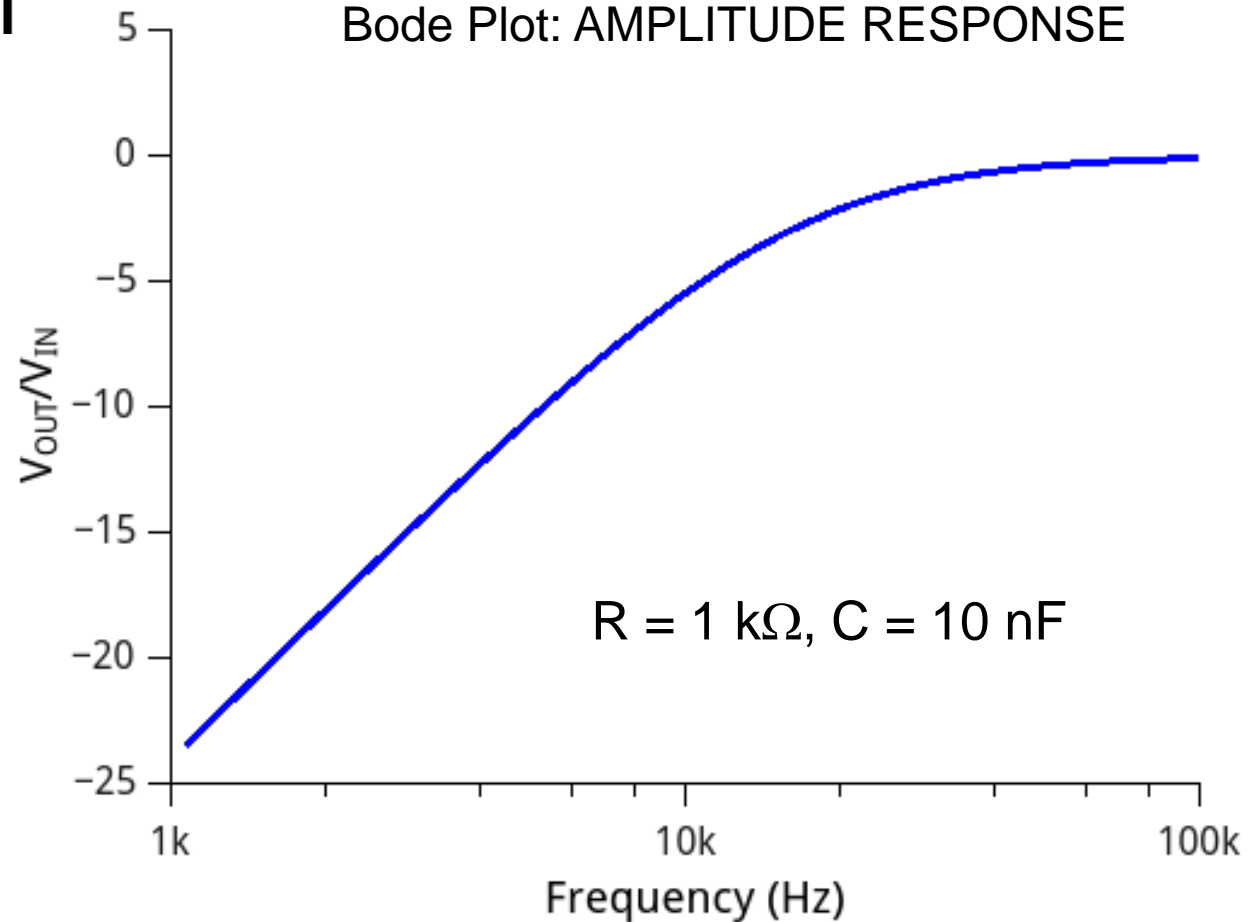


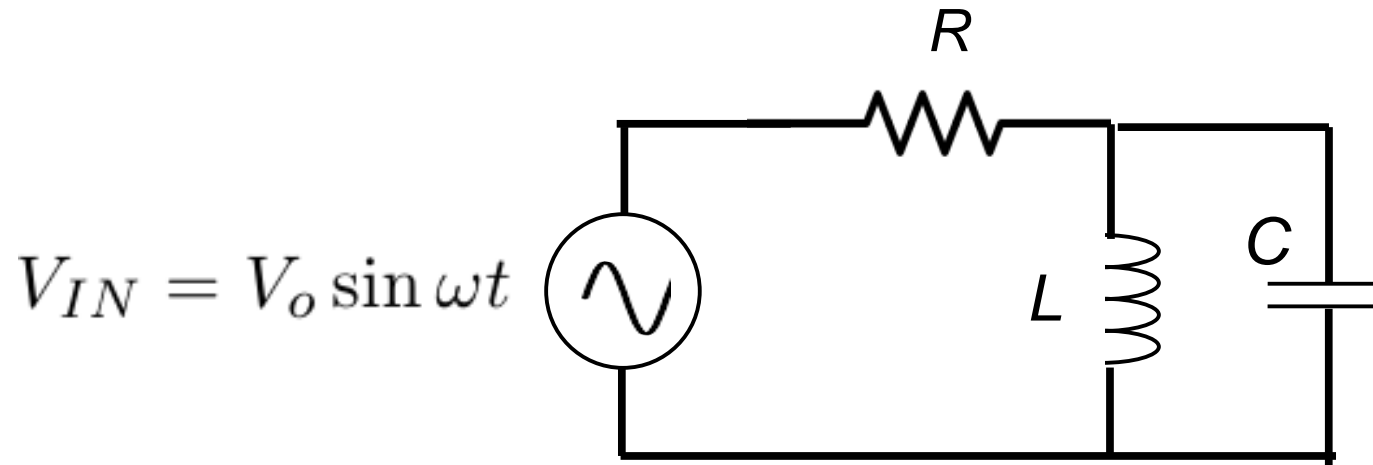Inductor-capacitor in AC circuit: Resonance




Parallel LC circuit

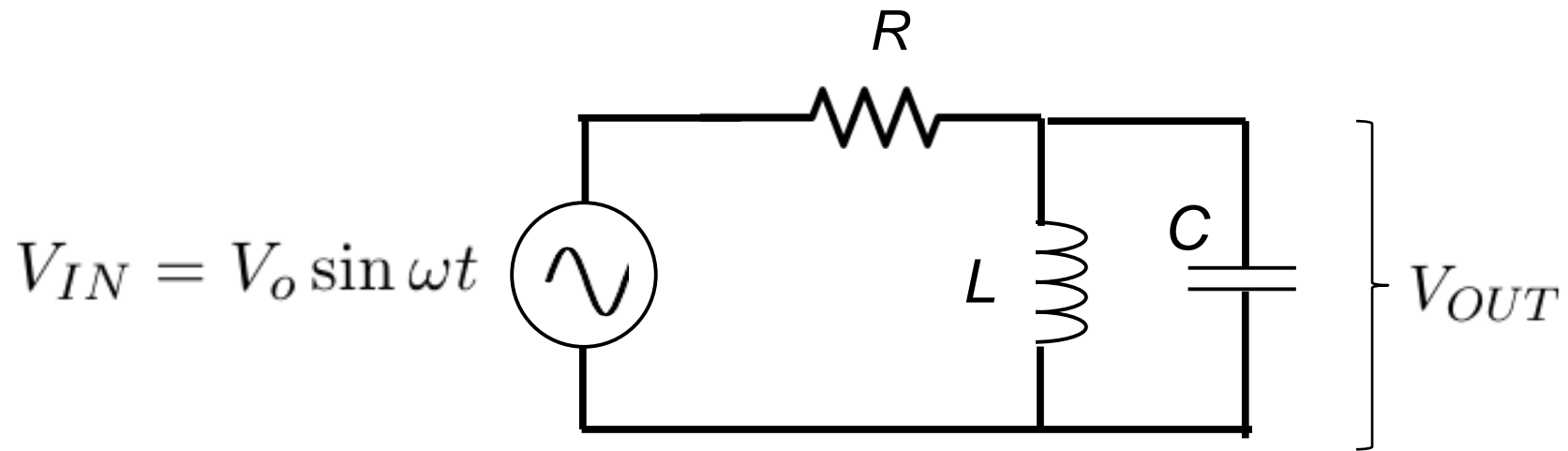Inductor-capacitor in AC circuit: Resonance



Parallel LC circuit

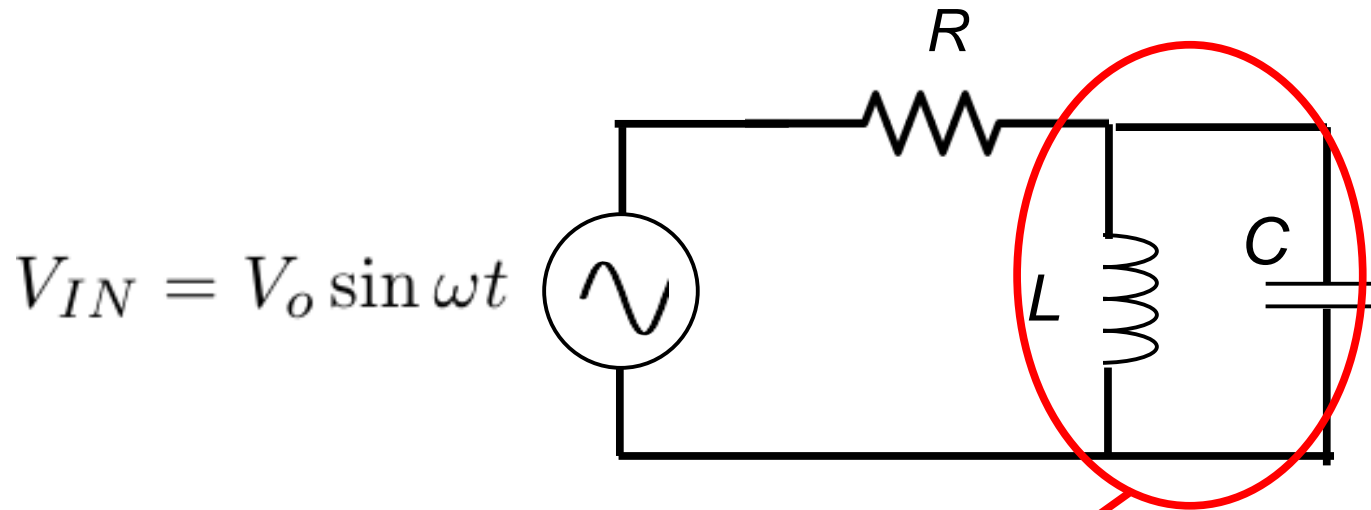
Inductor-capacitor in AC circuit: Resonance



$$Z_{parallel} = \frac{j\omega L}{1 - \omega^2 LC}$$


Resonance at: $f = \frac{1}{2\pi\sqrt{LC}}$

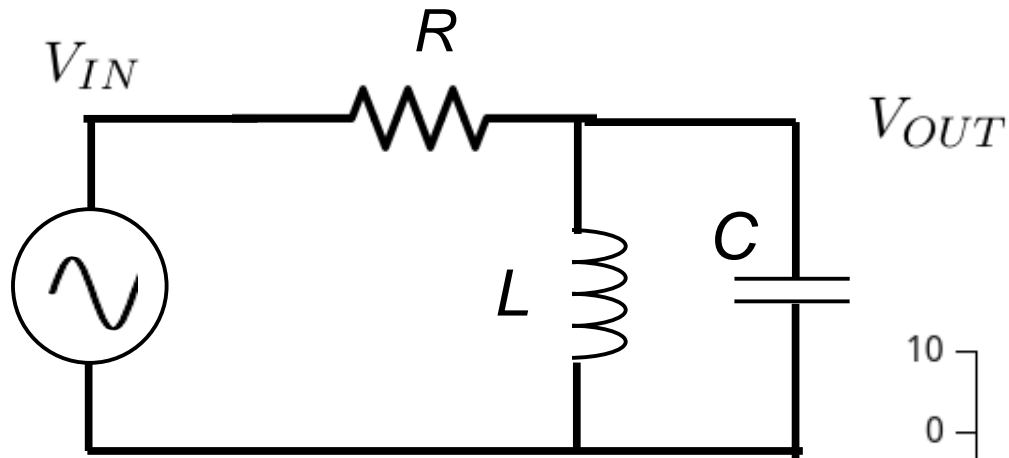Inductor-capacitor in AC circuit: Resonance




$C = 100 \text{ nF}$
 $L = 100 \text{ uH}$
 $f_{res} = 50.3 \text{ kHz}$

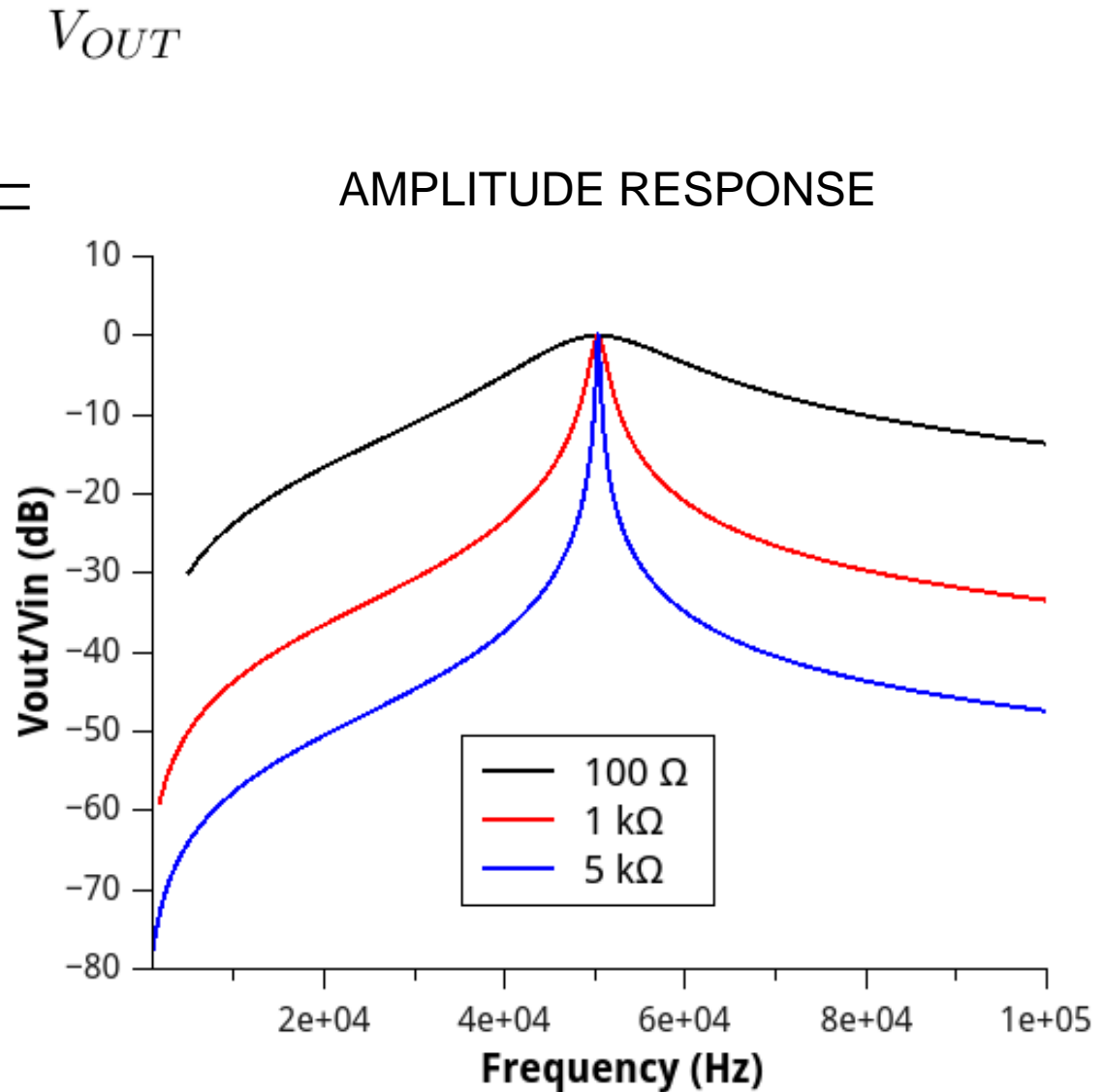$R = 100 \Omega, 1 \text{ k}\Omega, 5 \text{ k}\Omega$




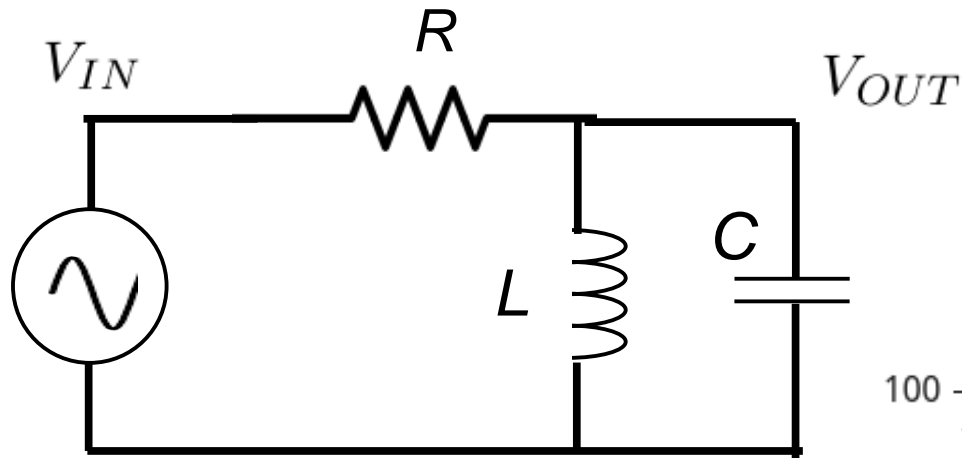Inductor-capacitor in AC circuit: Resonance



$C = 100 \text{ nF}$
 $L = 100 \text{ uH}$
 $f_{res} = 50.3 \text{ kHz}$

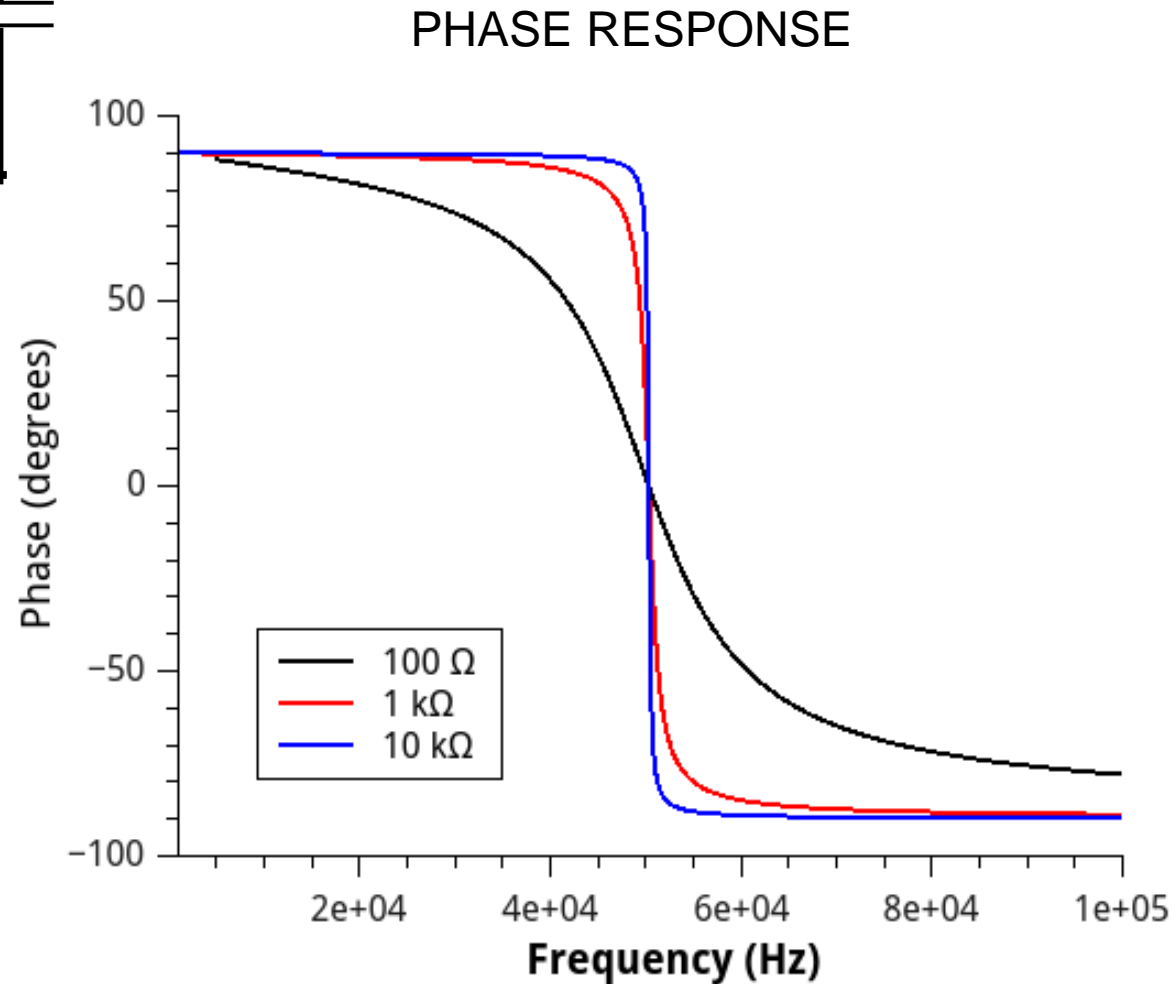$R = 100 \Omega, 1 \text{ k}\Omega, 5 \text{ k}\Omega$



Q-factor: Sharpness of Resonance

$$Q = \frac{\omega_0}{\Delta\omega} = \frac{f_0}{\Delta f} \quad \text{Sharper resonance} \rightarrow \text{Higher Q}$$

Δf = frequency range between the – 3 dB points

– 3 db \approx 0.707 of the peak


Q-factor: Sharpness of Resonance

Example RLC circuit:


R = 100 Ω , 1 k Ω , 5 k Ω

Q = 3.1, 31, 158

$$Q = R\sqrt{\frac{C}{L}}$$

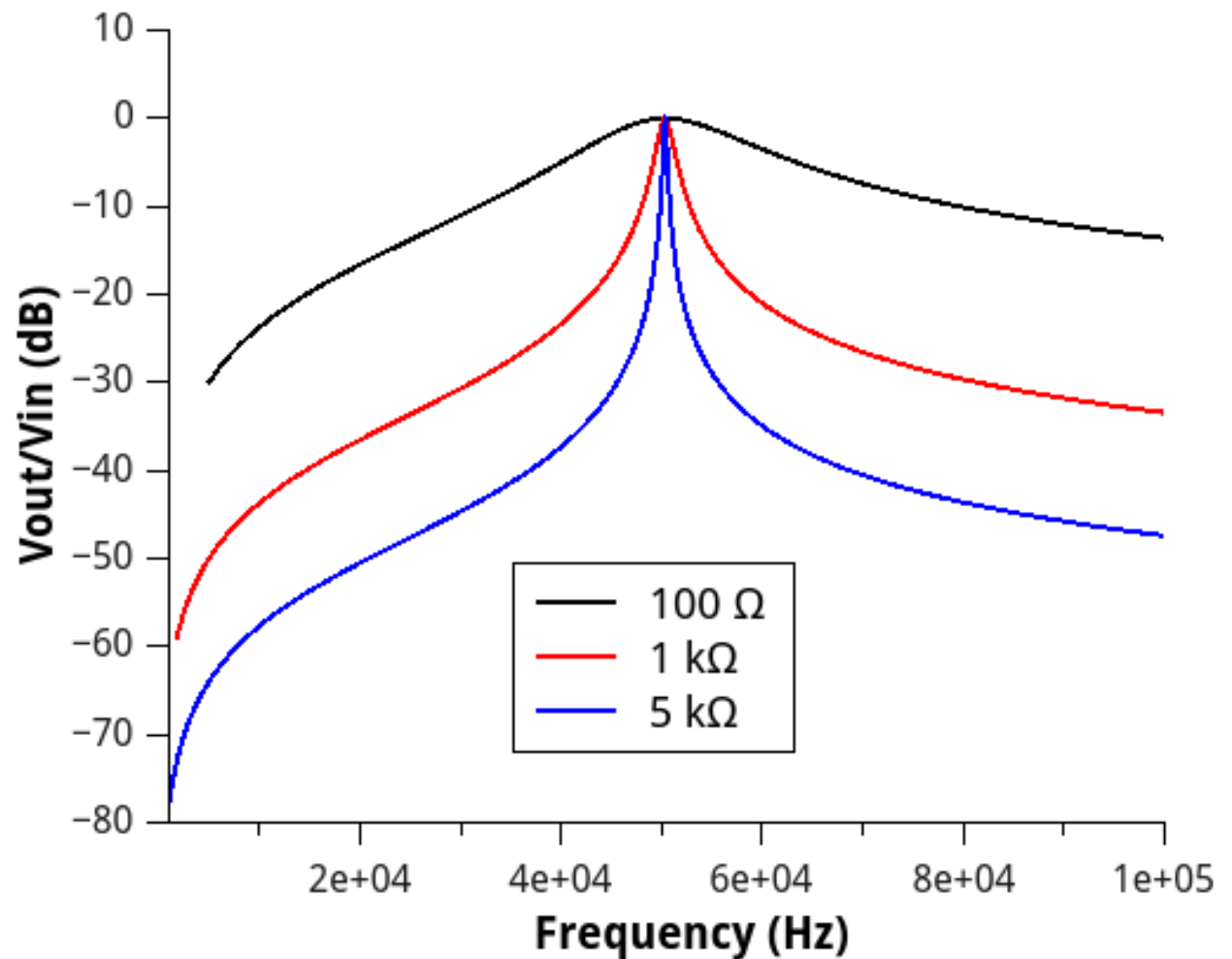


Resonance in series LC circuit

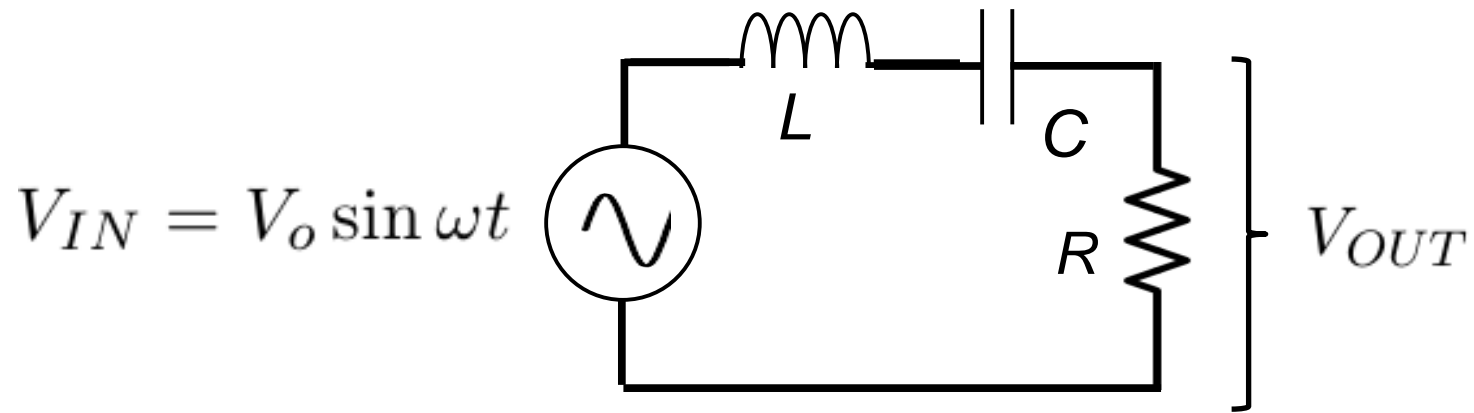

Series LC circuit


Resonance in series LC circuit

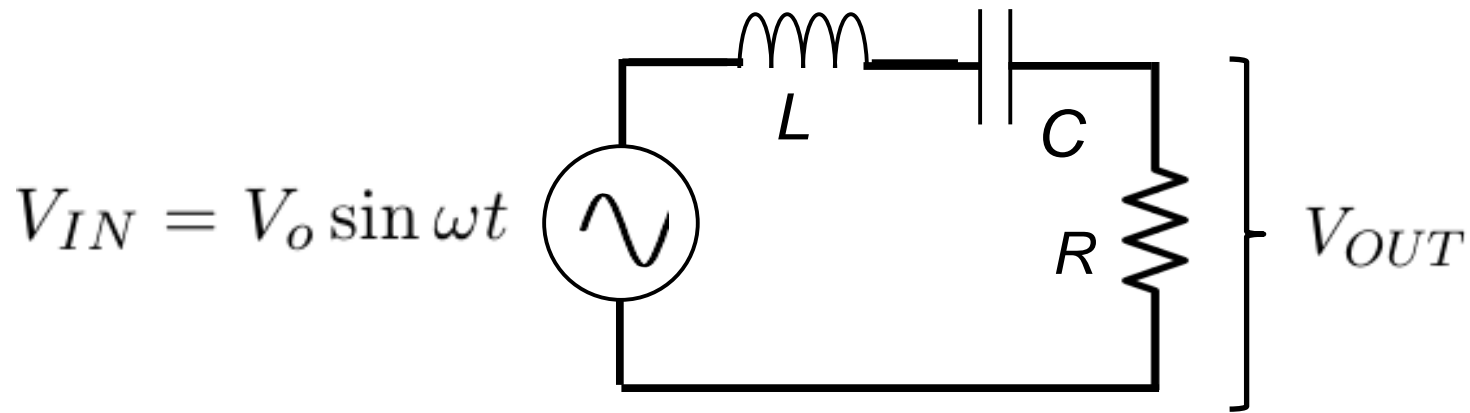

Series LC circuit

$$\frac{V_{OUT}}{V_{IN}} = \frac{R}{R + j\omega L + 1/j\omega C}$$


Resonance in series LC circuit

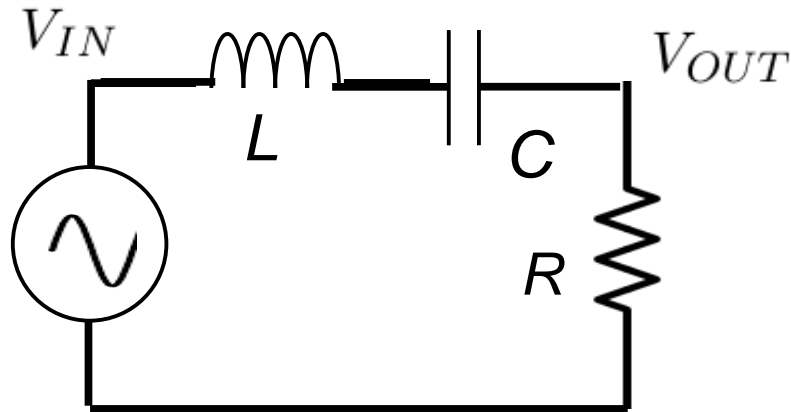


$C = 10 \text{ nF}$
 $L = 10 \text{ uH}$
 $f_{res} = 503 \text{ kHz}$

$R = 5 \Omega, 10 \Omega, 20 \Omega$
 $Q = 6.3, 3.1, 1.6$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

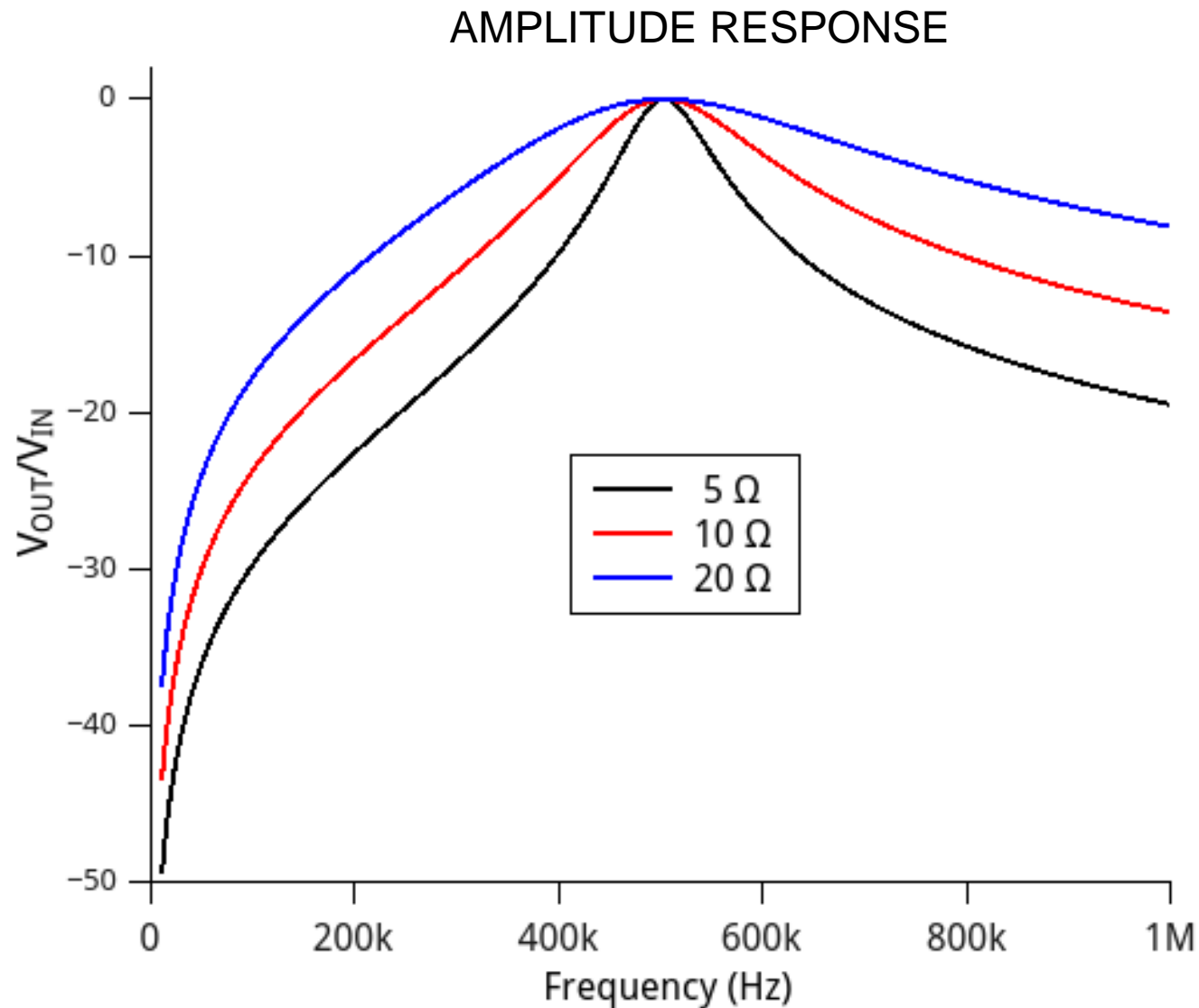

Resonance in series LC circuit

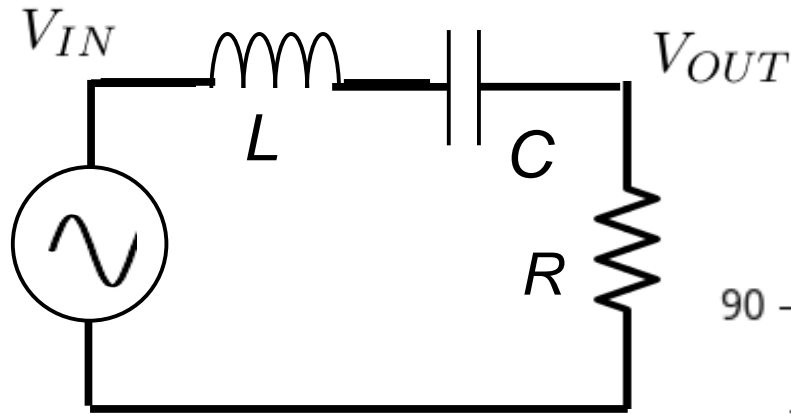

$C = 10 \text{ nF}$
 $L = 10 \text{ uH}$
 $f_{res} = 503 \text{ kHz}$

