

Lab 5: AC circuits (III)

Poles and Zeroes

$$\frac{V_{OUT}(\omega)}{V_{IN}(\omega)} = G(\omega) = \frac{N(\omega)}{D(\omega)}$$


Numerator: $N(\omega) = (\omega_{N1} + j\omega)(\omega_{N2} + j\omega) \times \dots (\omega_{Nm} + j\omega)$

Denominator: $D(\omega) = (\omega_{D1} + j\omega)(\omega_{D2} + j\omega) \times \dots (\omega_{Dm'} + j\omega)$


$$m \leq m'$$

Zeroes: Frequencies (ω_N) that make the numerator zero
Poles: Frequencies (ω_D) that make the denominator zero

The Bode Plot for $|G(\omega)|$

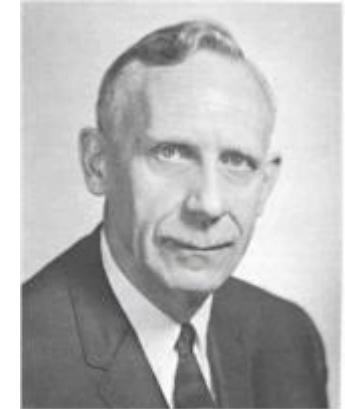

HW Bode
1905—1982
Bell Labs

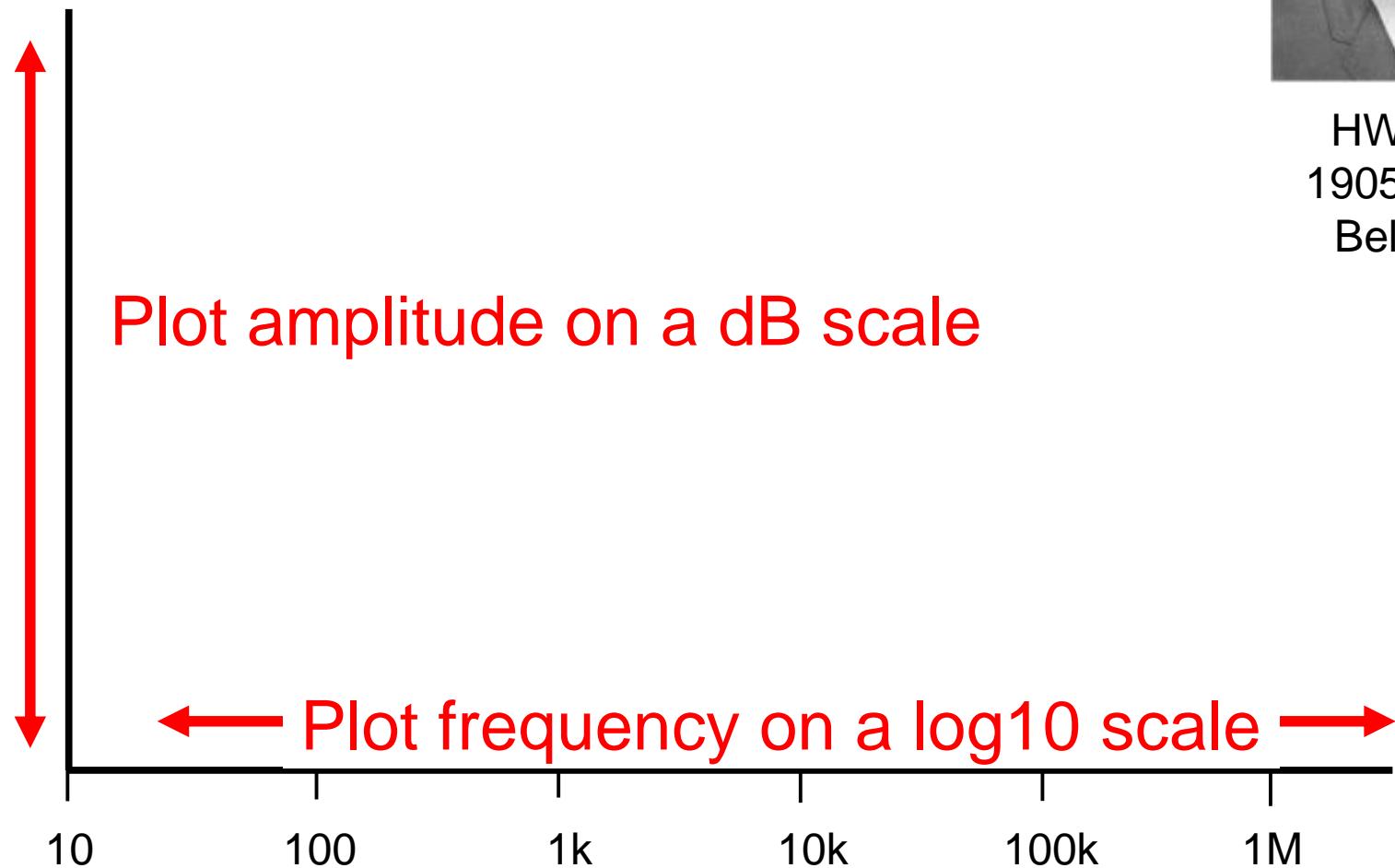

POLES and **ZEROES** change the slopes on the Bode Plot

Amplitude response

ZERO: + 20 dB/decade

POLE: – 20 dB/decade

Phase response


ZERO: + 45 deg/decade

POLE: – 45 deg/decade

POLES and **ZEROES** dramatically affect the shape of a Bode plot




HW Bode
1905—1982
Bell Labs

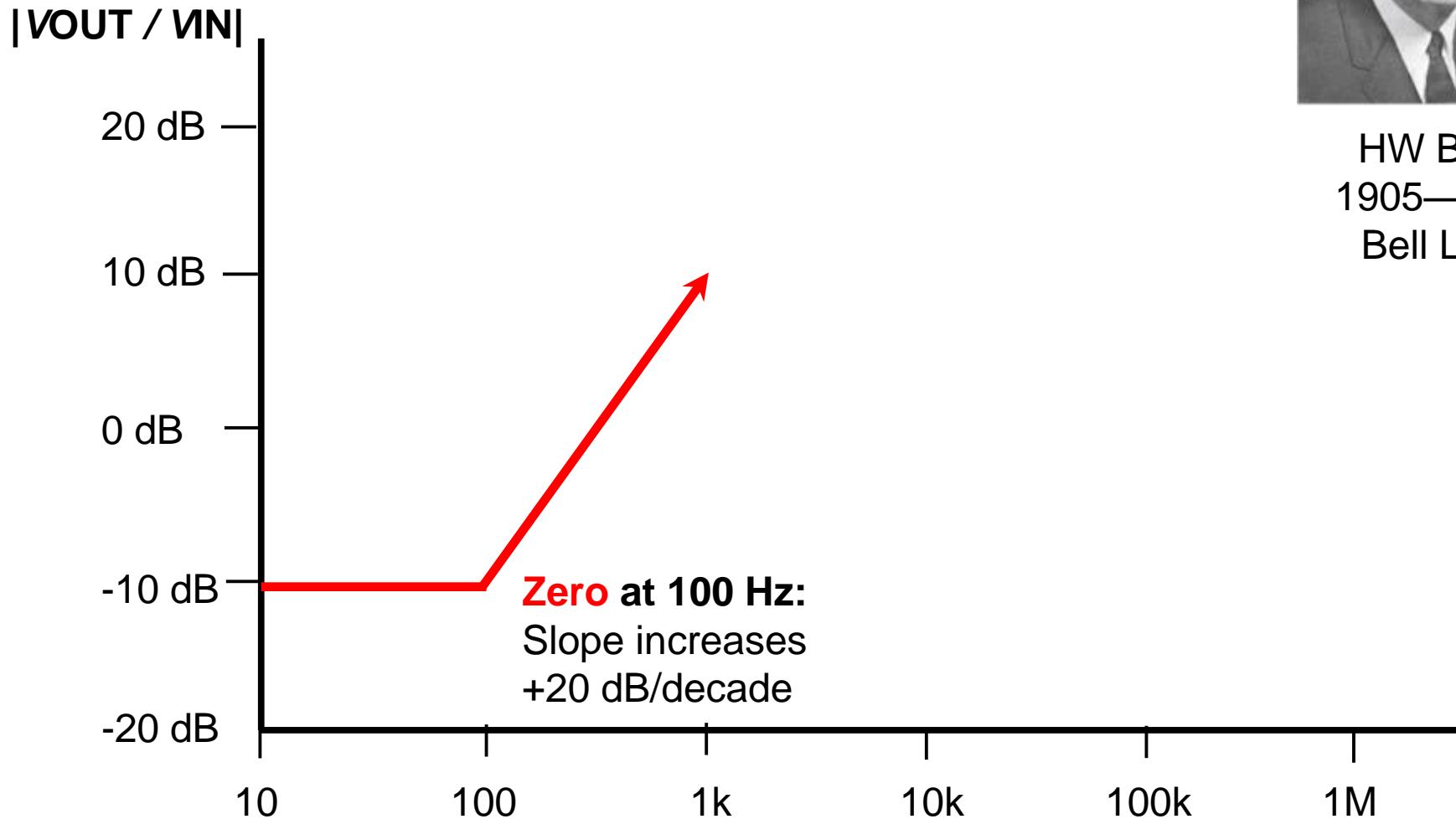

POLES and **ZEROES** dramatically affect the shape of a Bode plot




HW Bode
1905—1982
Bell Labs

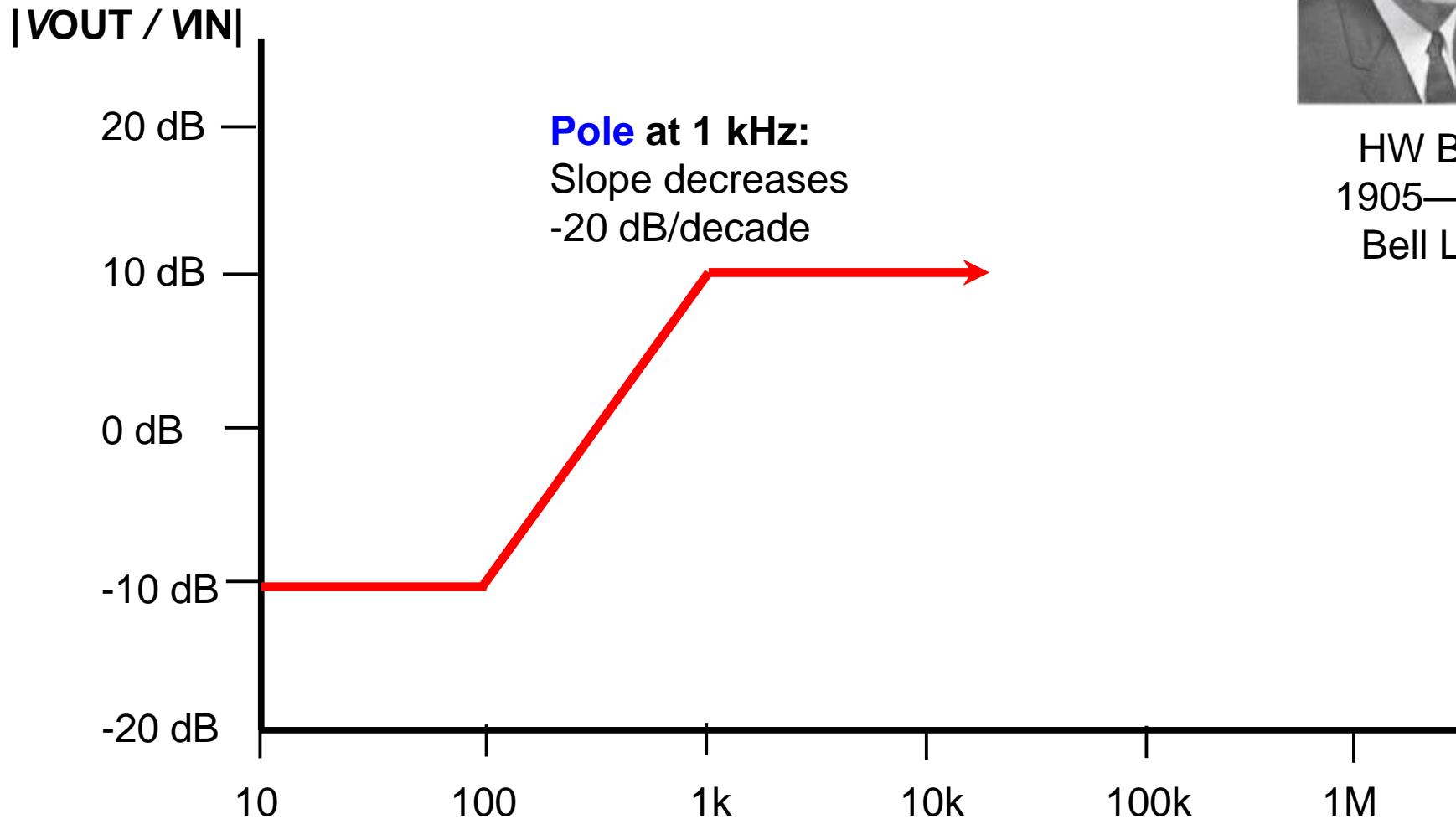


POLES and **ZEROES** dramatically affect the shape of a Bode plot



HW Bode
1905—1982
Bell Labs

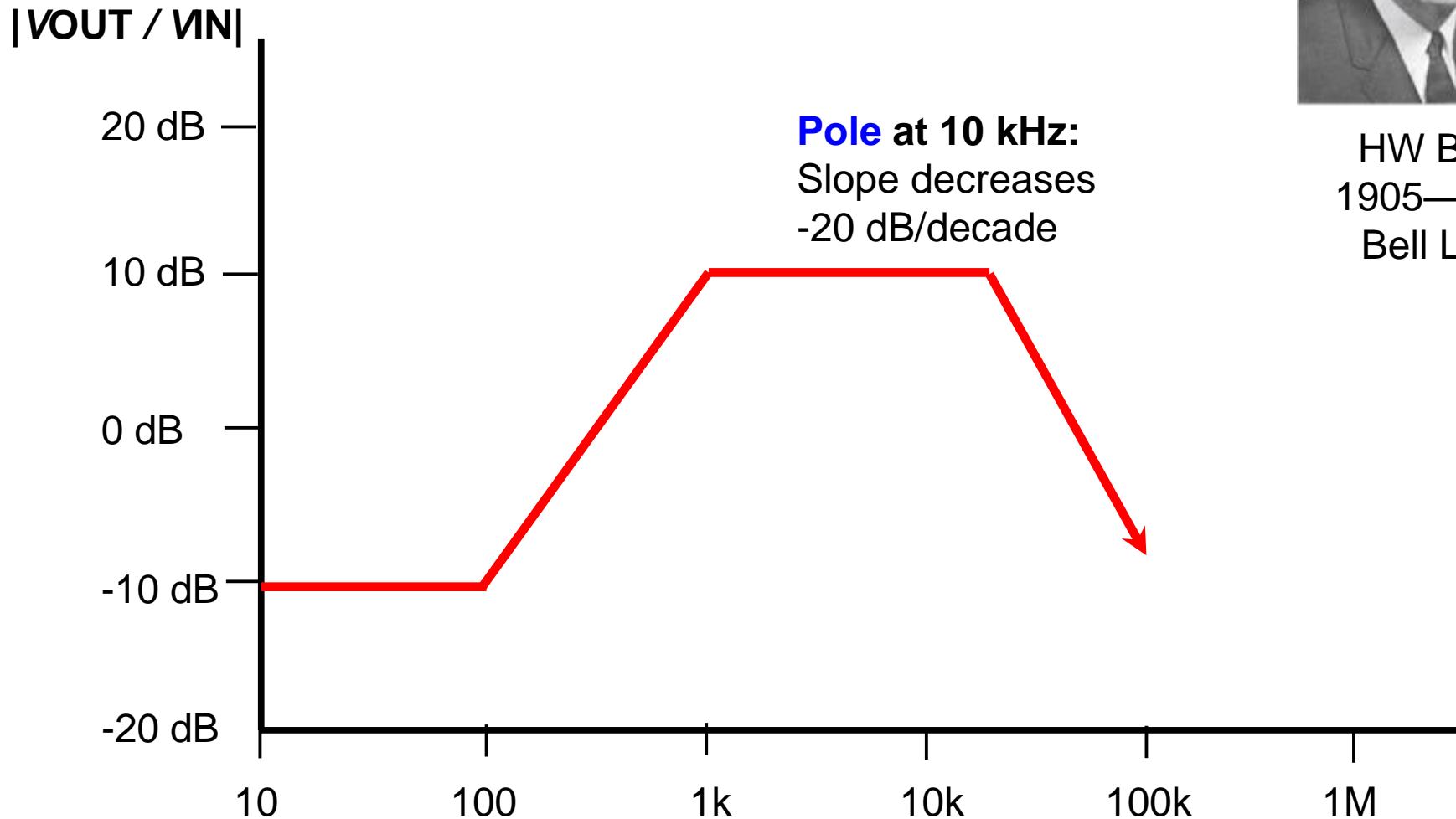


Example 1: Low-pass filter

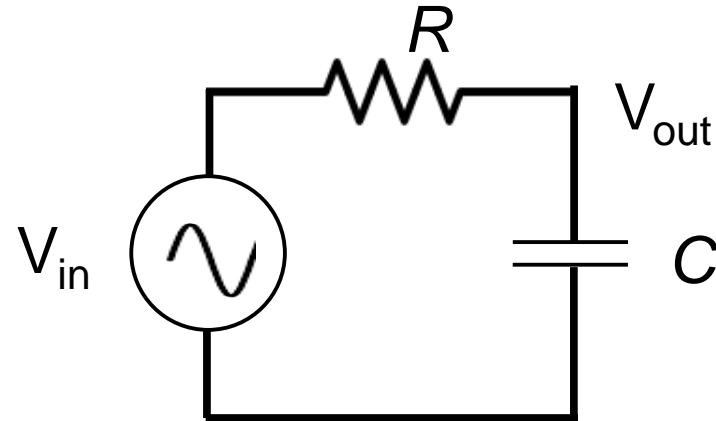



$$\frac{V_{out}}{V_{in}} = \frac{Z_C}{Z_R + Z_C} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC}$$

Pole in denominator

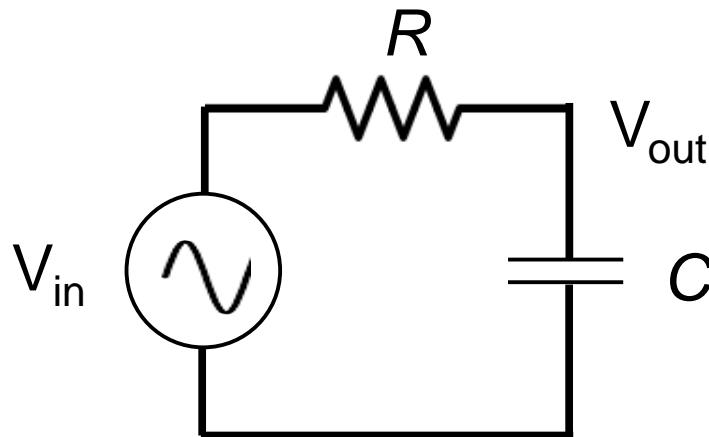


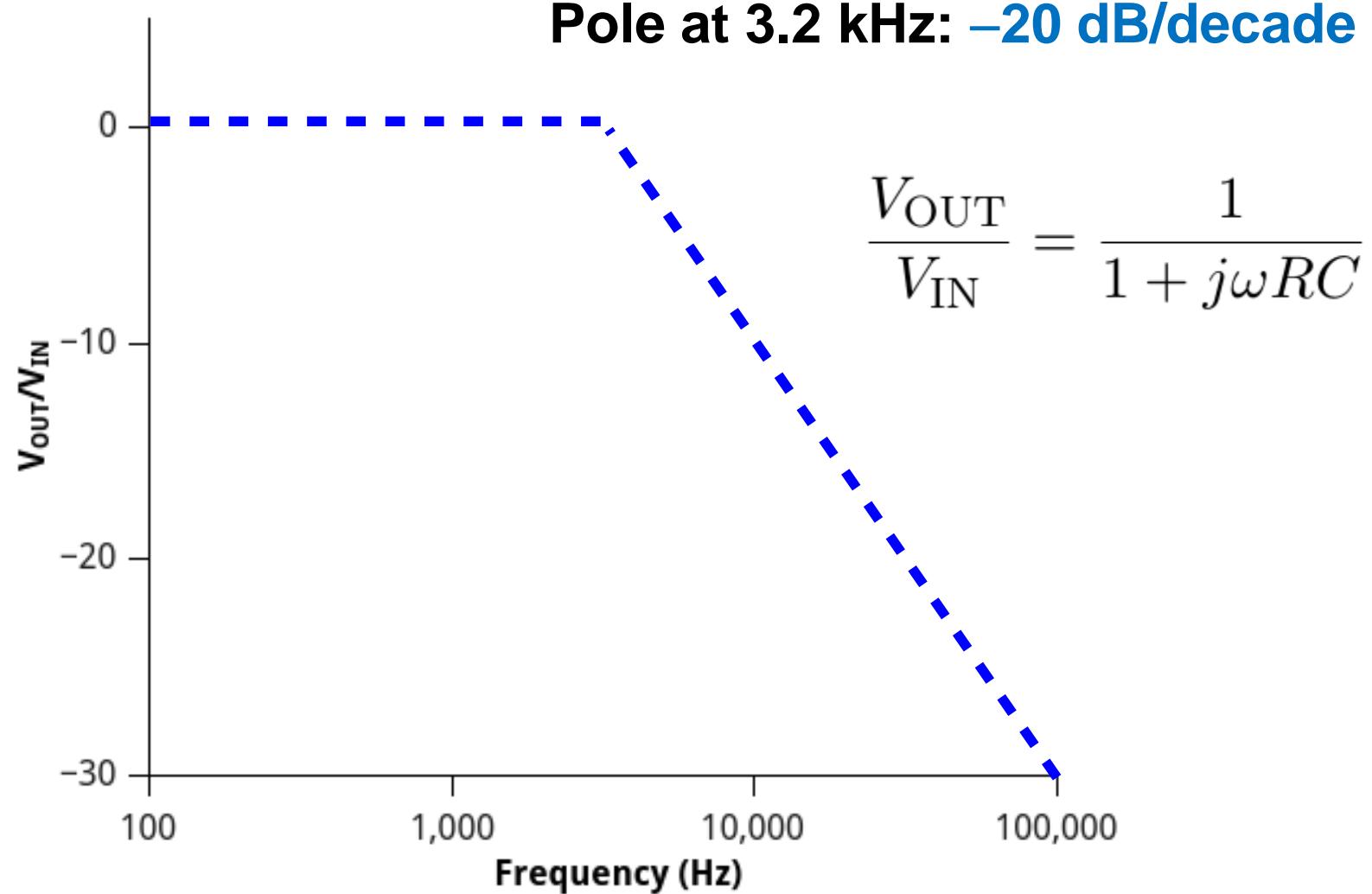
$$\begin{aligned}R &= 5000 \Omega \\C &= 10 \text{ nF} \\f &= 3.2 \text{ kHz}\end{aligned}$$



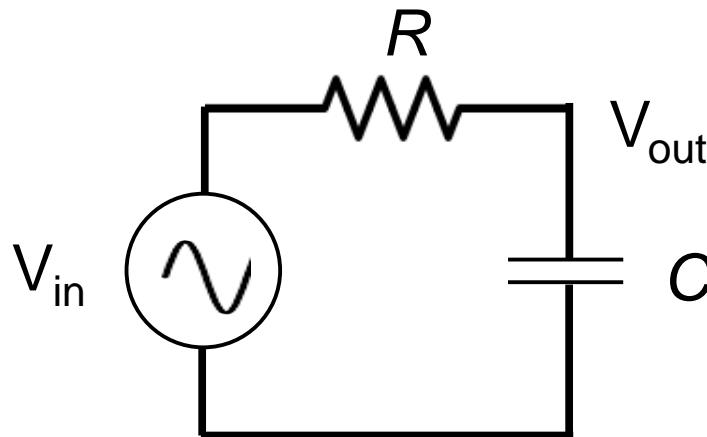
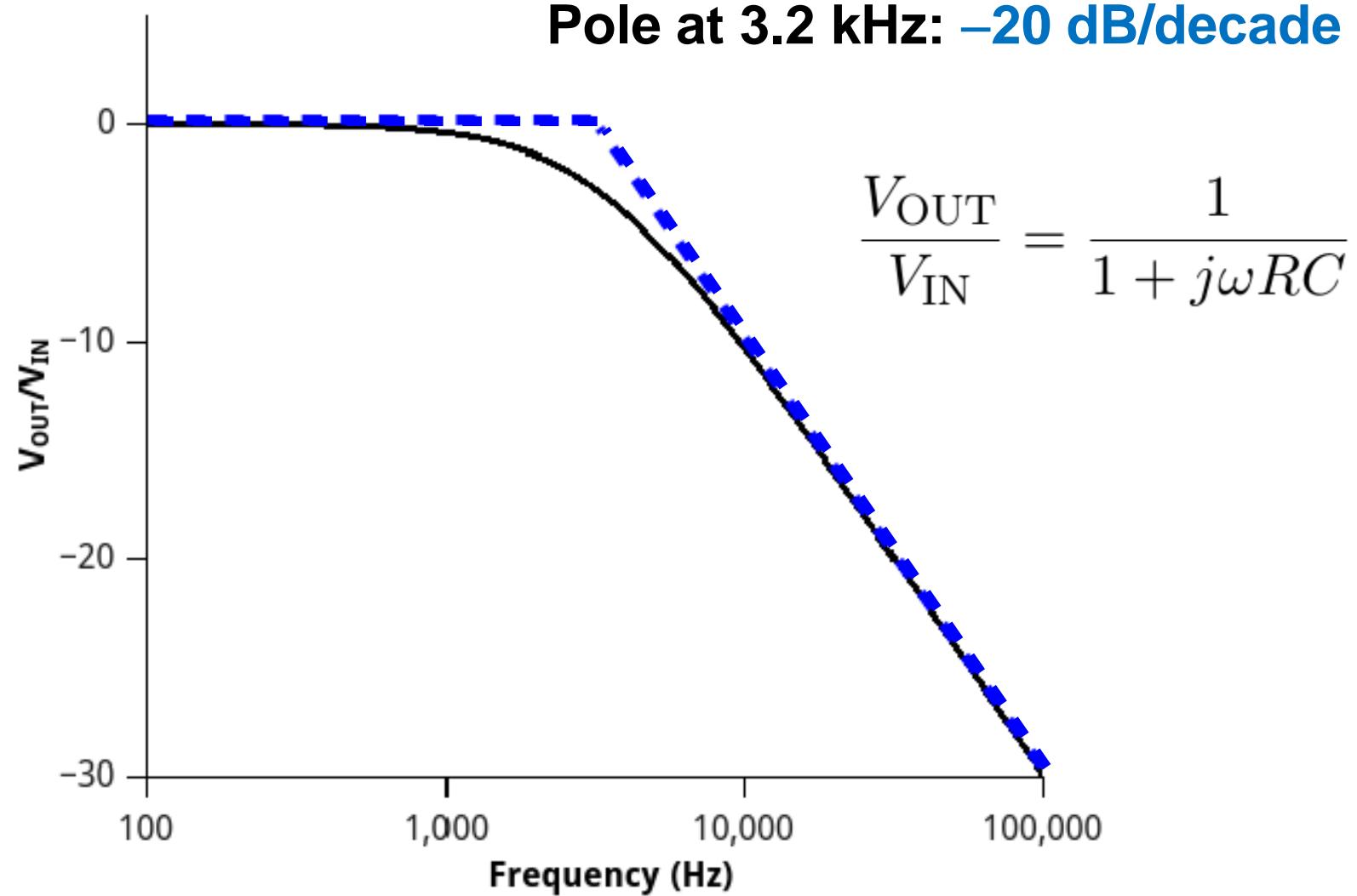
$$\begin{aligned}R &= 5000 \Omega \\C &= 10 \text{ nF} \\f &= 3.2 \text{ kHz}\end{aligned}$$



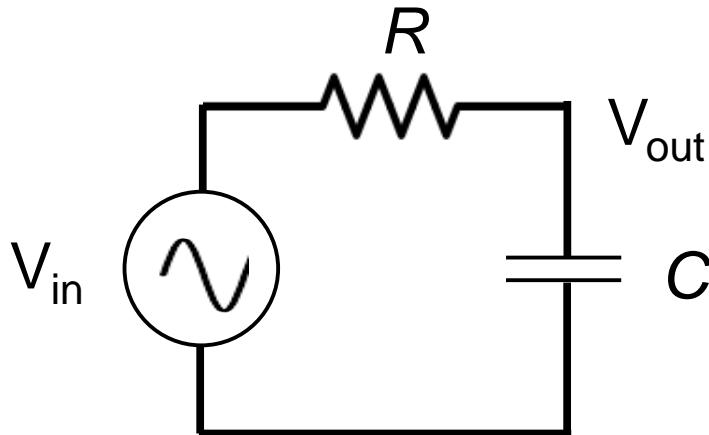


$$R = 5000 \Omega$$

$$C = 10 \text{ nF}$$


$$f = 3.2 \text{ kHz}$$

Pole at 3.2 kHz: **-45 deg/decade**

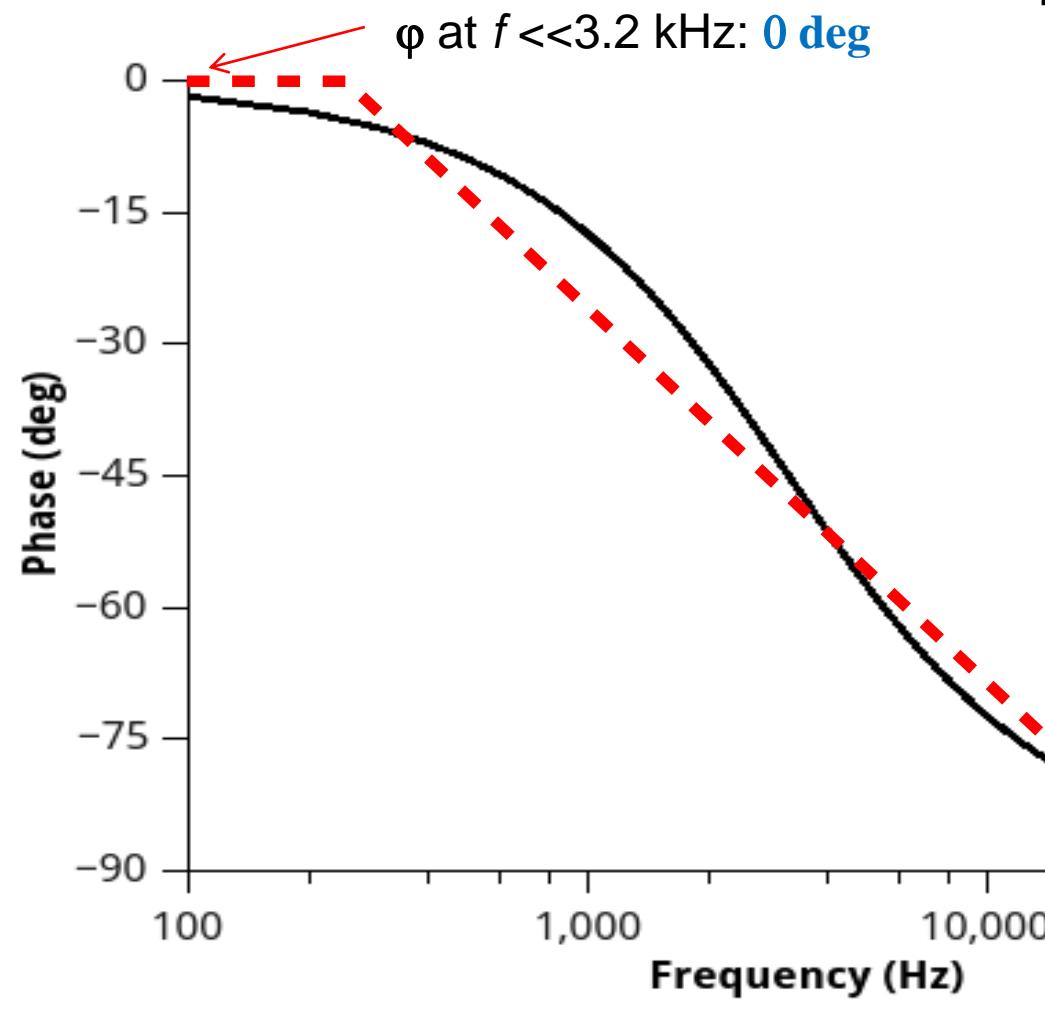


$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{1}{1 + j\omega RC}$$

$\phi = \tan^{-1}(b/a) = \tan^{-1}(-\omega RC/1)$

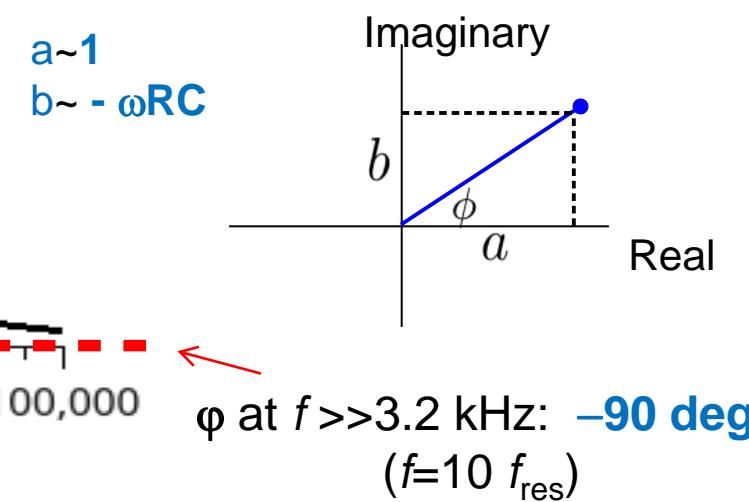


Example 2: 2-pole low-pass filter

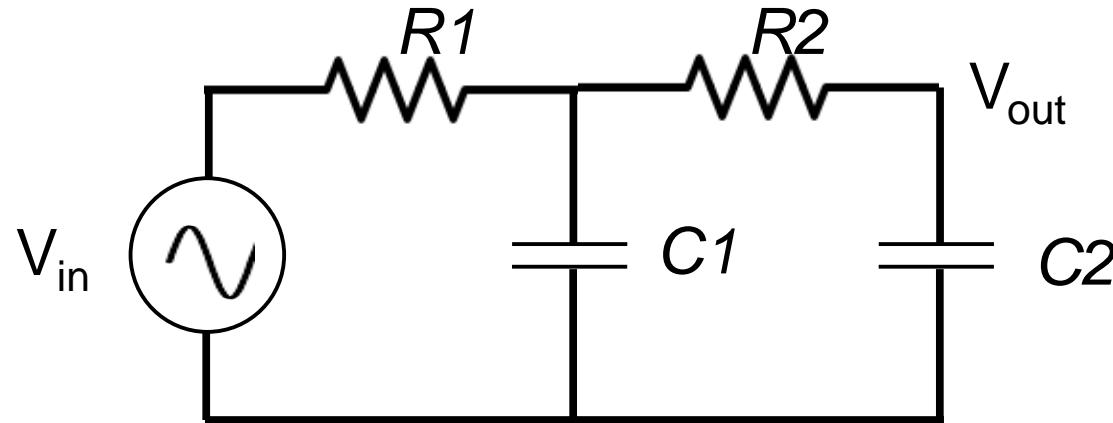



Assume “no loading”
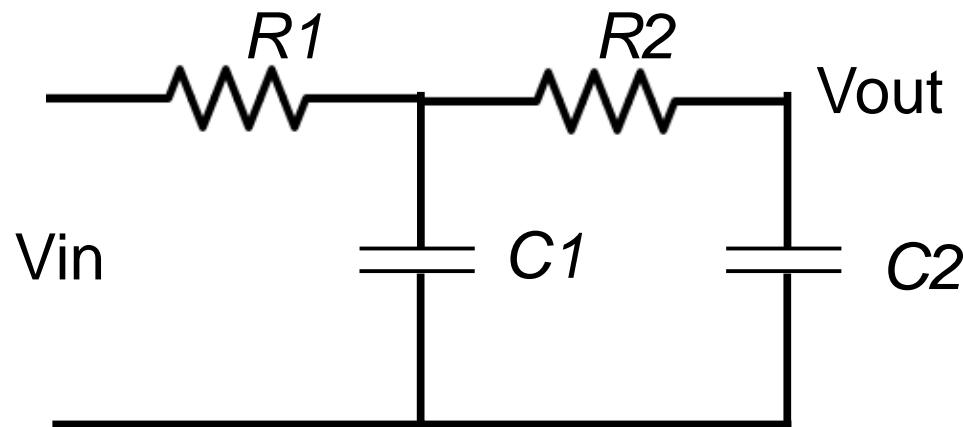
$$\frac{V_{OUT}}{V_{IN}} \approx \underbrace{\left[\frac{1}{1 + j\omega R_1 C_1} \right]}_{\text{1st pole}} \underbrace{\left[\frac{1}{1 + j\omega R_2 C_2} \right]}_{\text{2nd pole}}$$




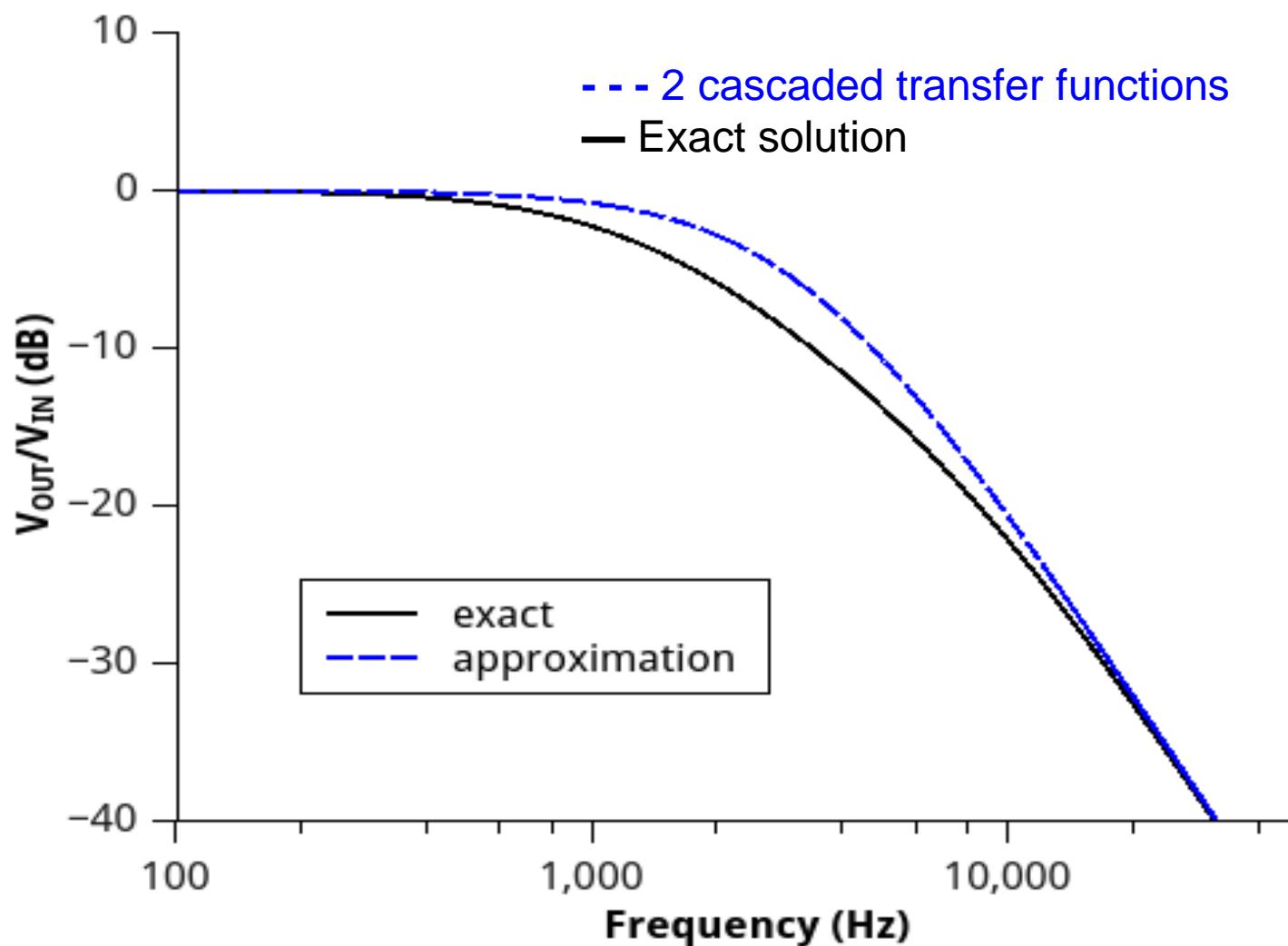
$R_1 = 5000 \Omega$ $R_2 = 500 \Omega$
 $C_1 = 10 \text{ nF}$ $C_2 = 3 \text{ nF}$
 $f = 3.2 \text{ kHz}$ $f = 10.6 \text{ kHz}$



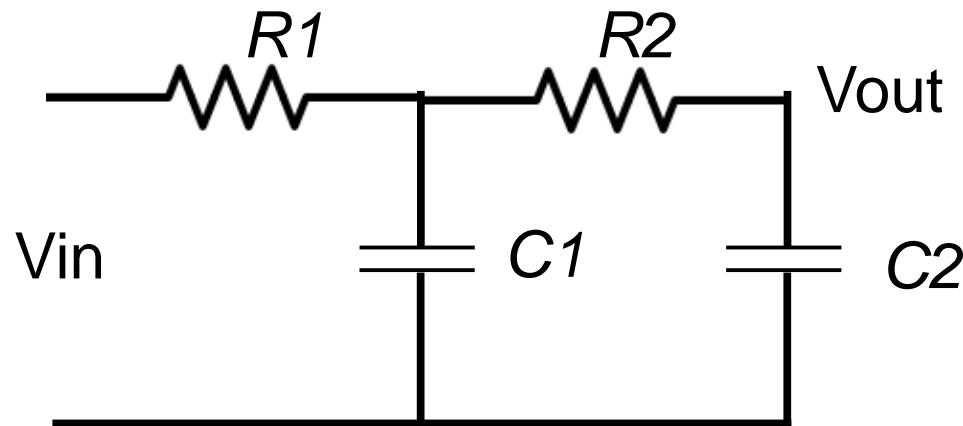


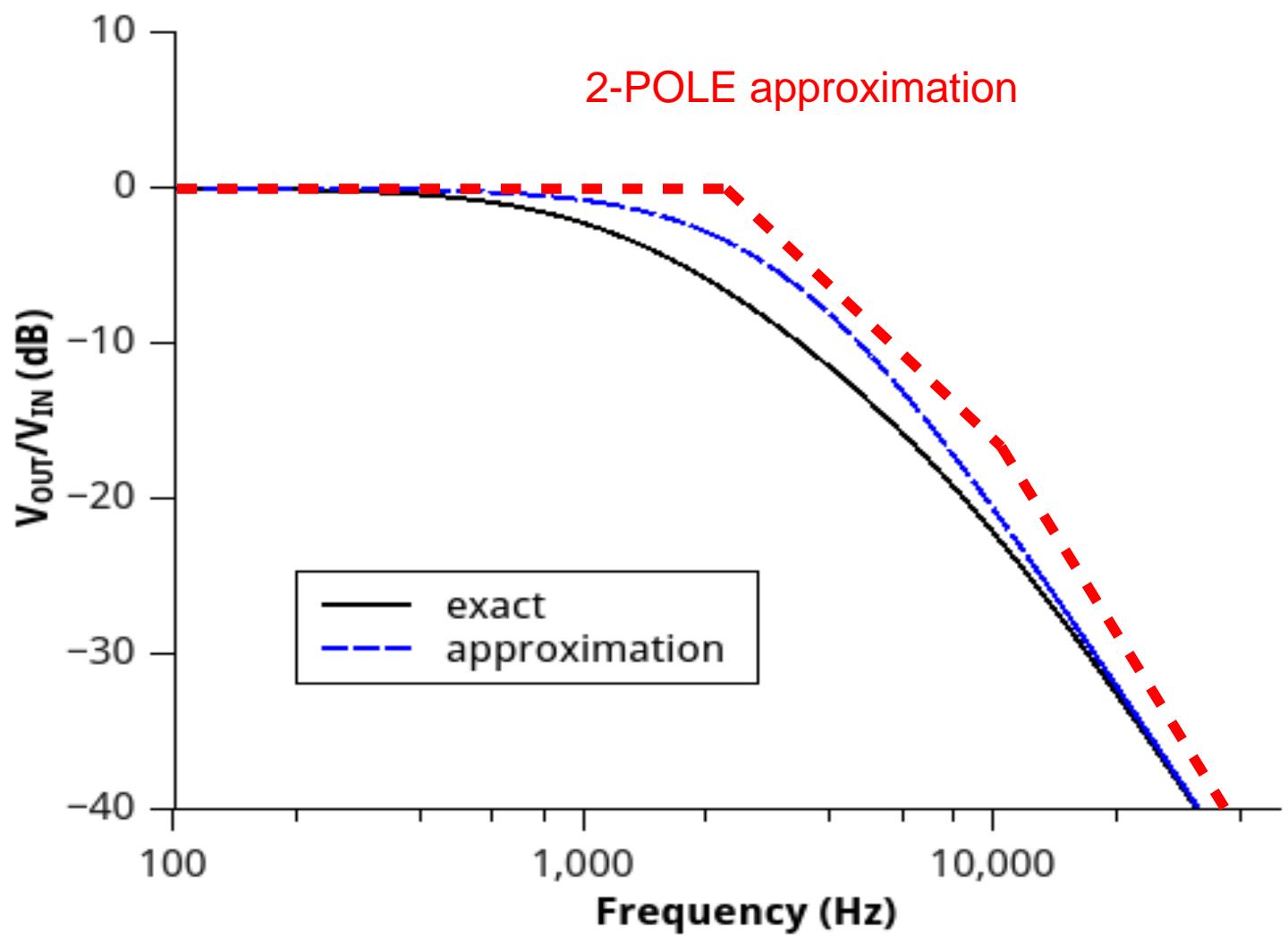$R1 = 5000 \Omega$ $R2 = 500 \Omega$
 $C1 = 10 \text{ nF}$ $C2 = 3 \text{ nF}$
 $f = 3.2 \text{ kHz}$ $f = 10.6 \text{ kHz}$




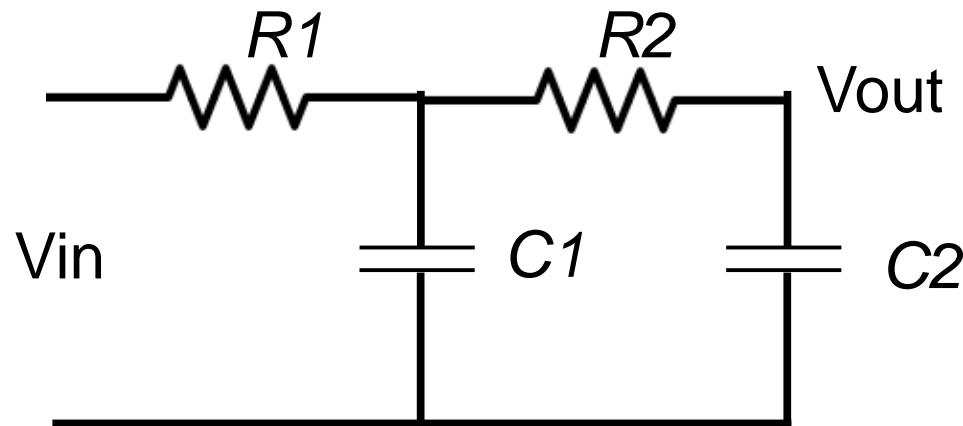

$R_1 = 5000 \Omega$	$R_2 = 500 \Omega$
$C_1 = 10 \text{ nF}$	$C_2 = 3 \text{ nF}$
$f = 3.2 \text{ kHz}$	$f = 10.6 \text{ kHz}$

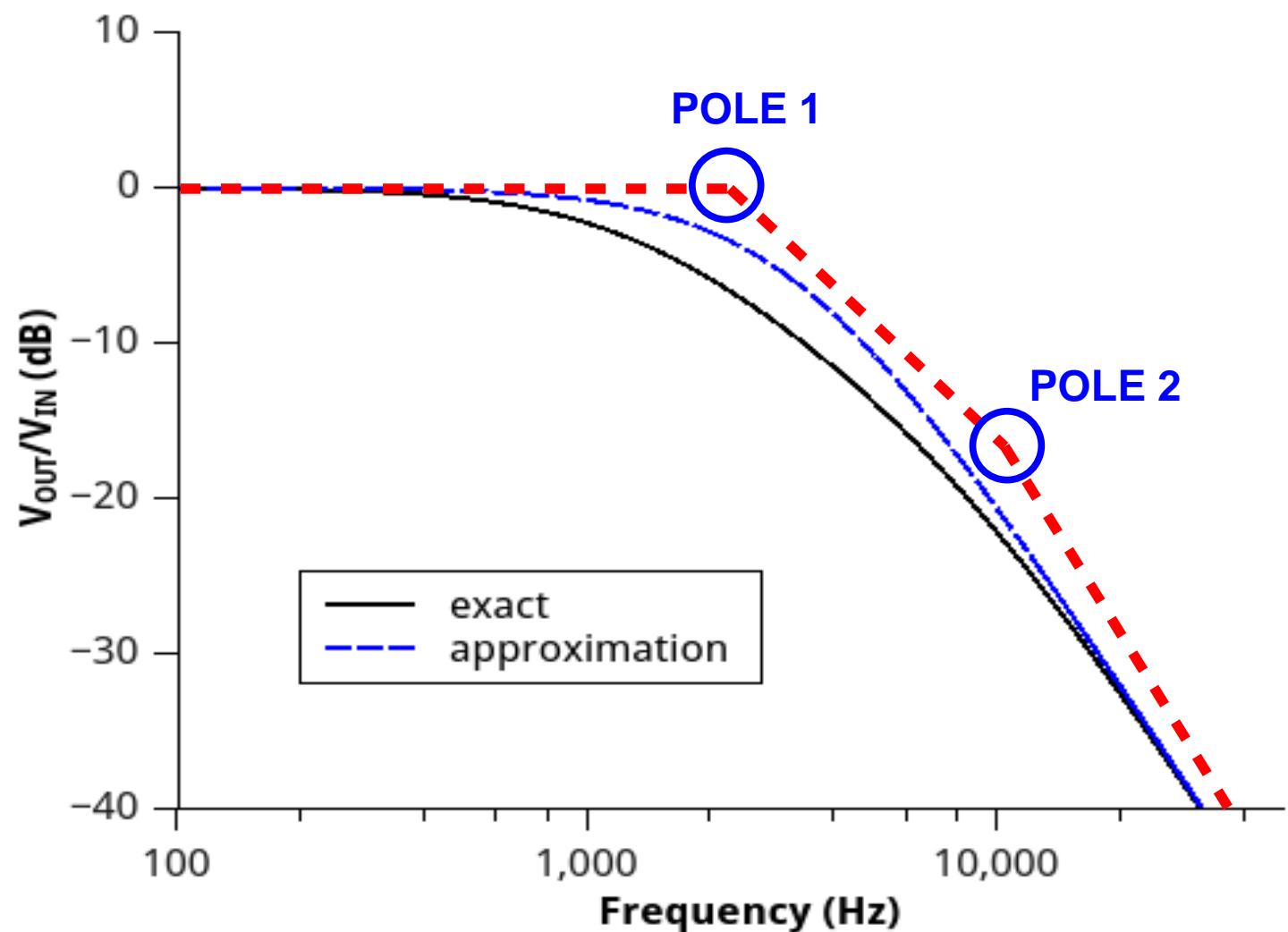

Example 3: 2-pole low-pass filter

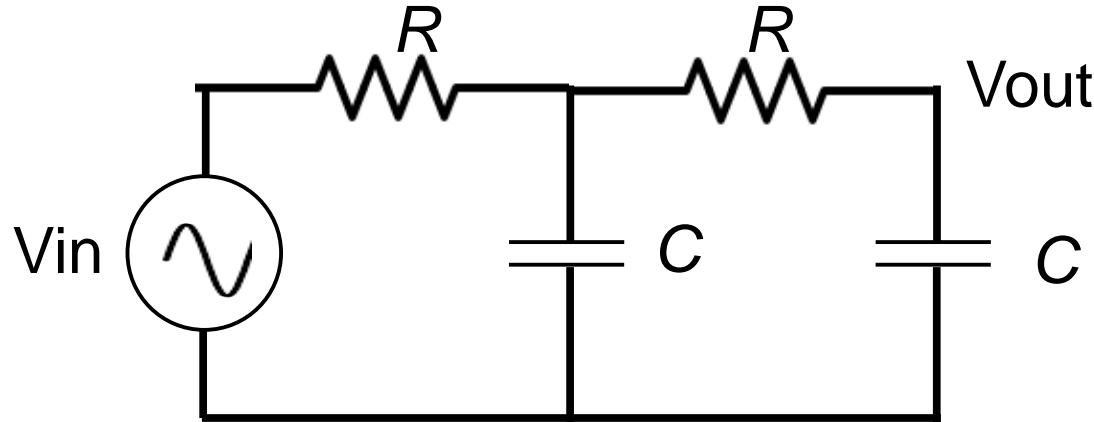


$$\begin{aligned}R &= 5000 \Omega \\C &= 10 \text{ nF} \\f &= 3.2 \text{ kHz}\end{aligned}$$

Assume “no loading”


$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} \approx \underbrace{\left[\frac{1}{1 + j\omega RC} \right]}^2$$

2 identical poles

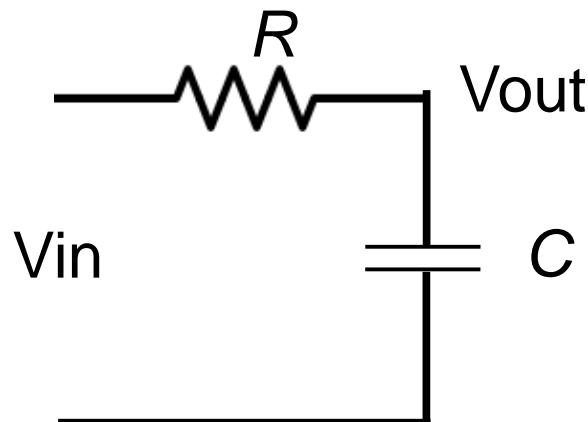



1-pole

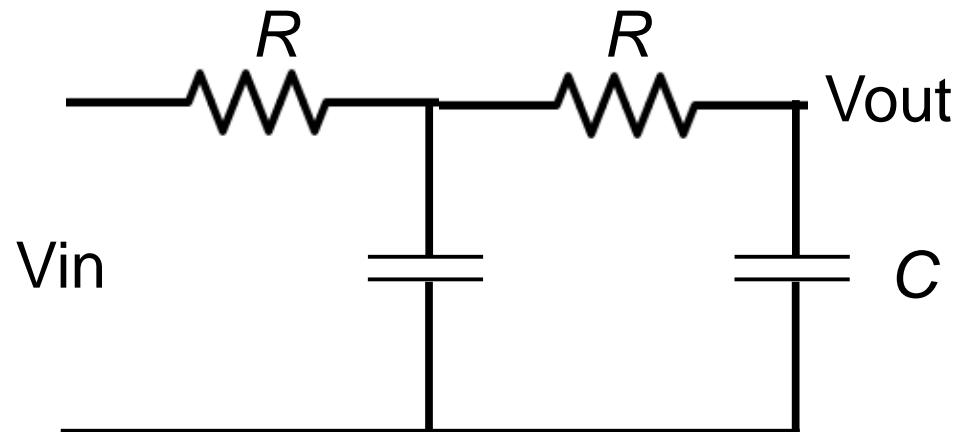$R = 5000 \Omega$
 $C = 10 \text{ nF}$
 $f = 3.2 \text{ kHz}$




2-identical poles

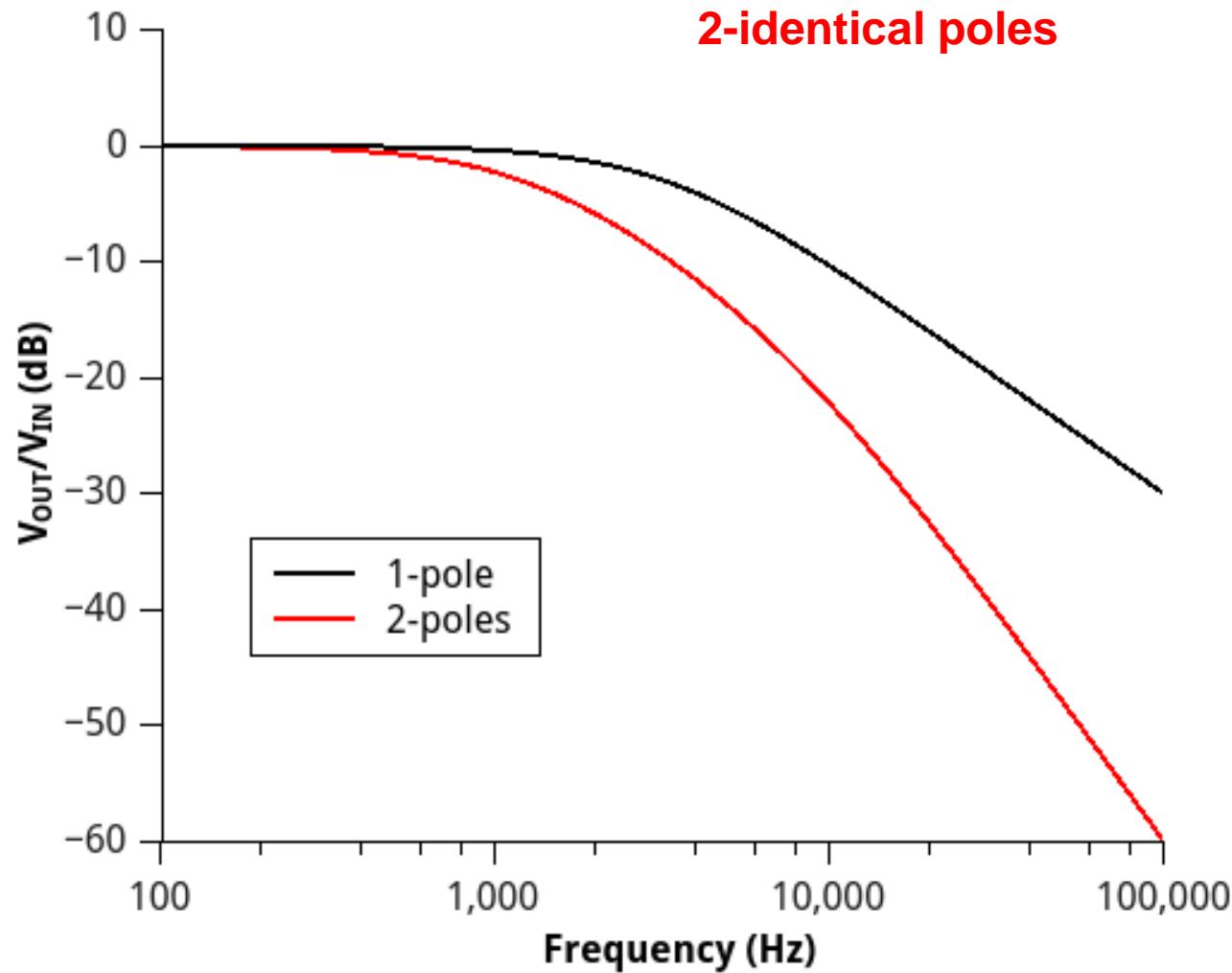

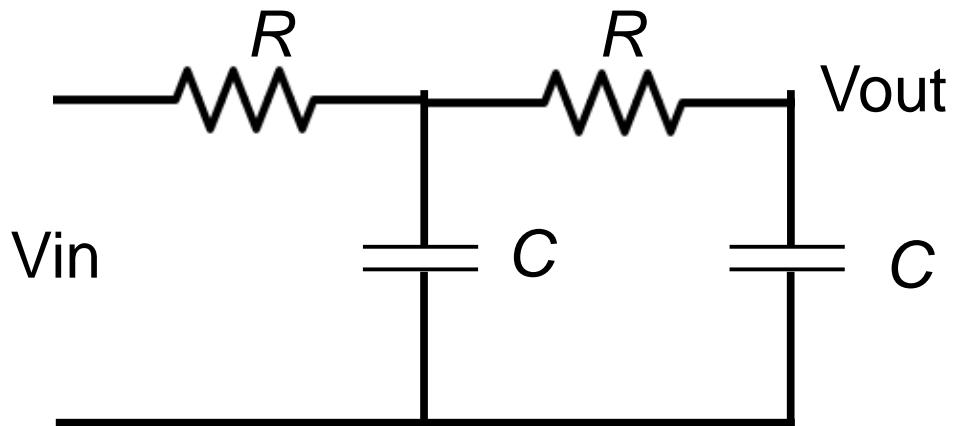

2 identical poles

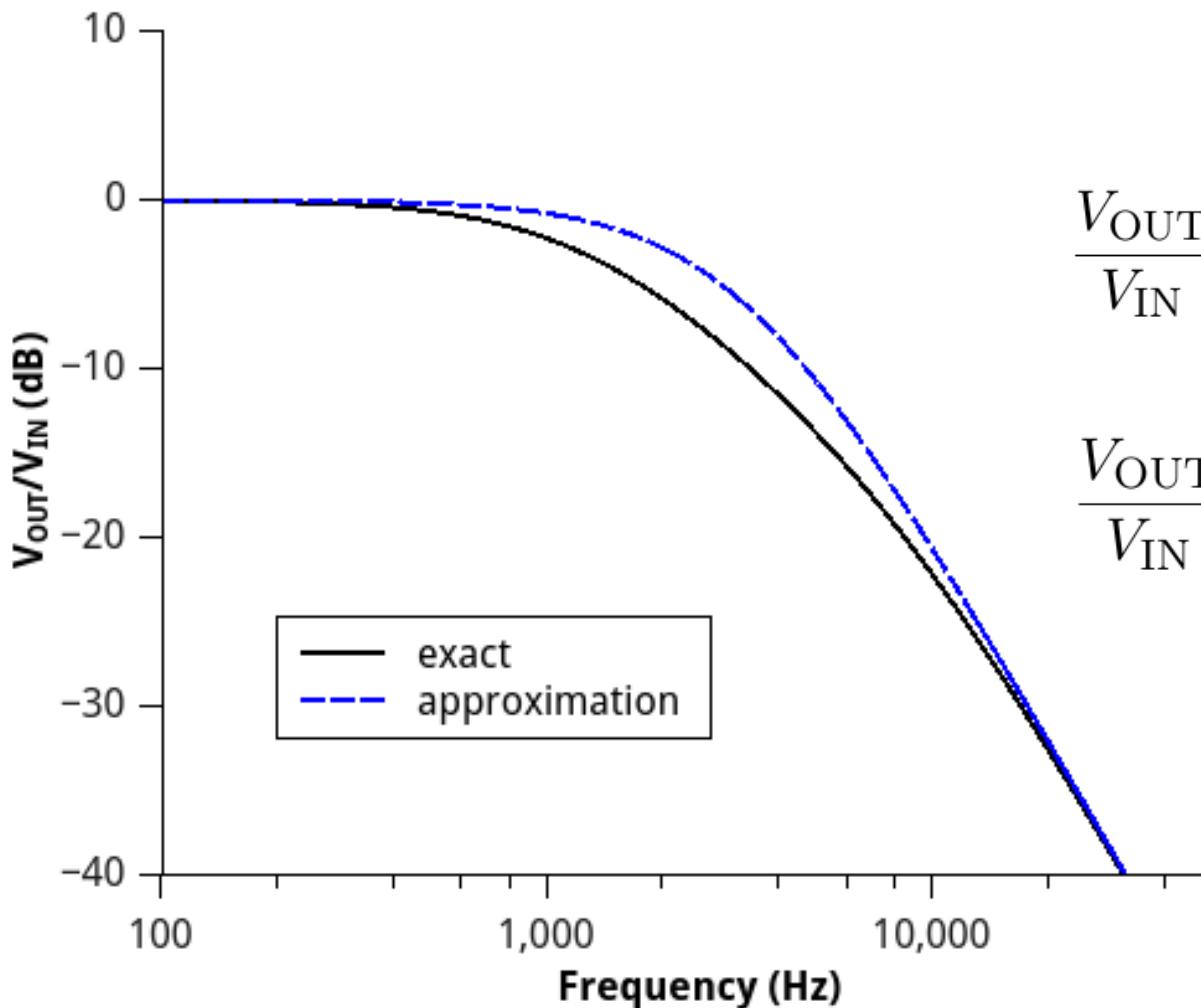
- Effect of Loading
- Analyze as uncoupled stages



$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{1}{1 - (\omega RC)^2 + j\omega 3RC}$$

$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} \approx \left[\frac{1}{1 + j\omega RC} \right]^2$$


Example 4: 1-pole + 1-zero

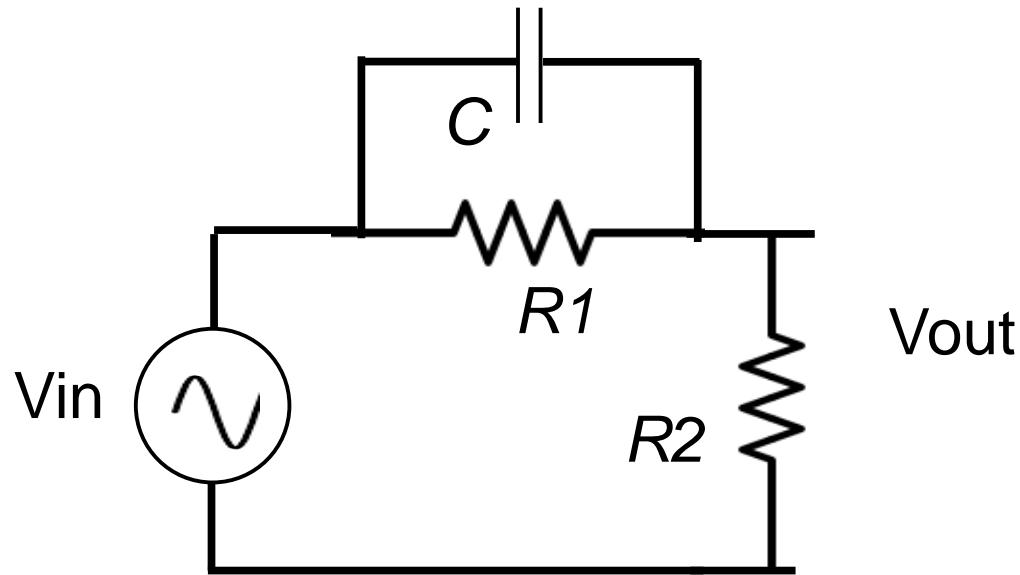


ZERO in numerator


$$\frac{V_{OUT}}{V_{IN}} = \left[\frac{R_2}{R_1 + R_2} \right] \left[\frac{1 + j\omega R_1 C}{1 + j\omega C \frac{R_1 R_2}{R_1 + R_2}} \right]$$

POLE in denominator

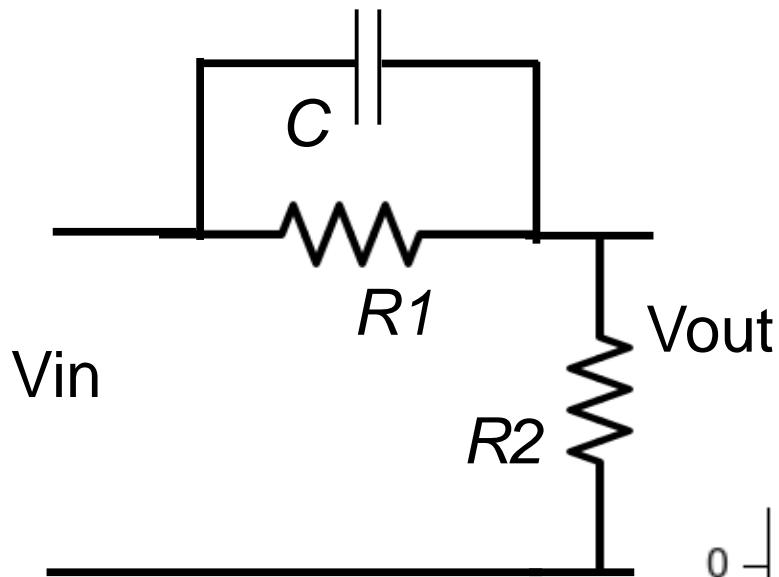

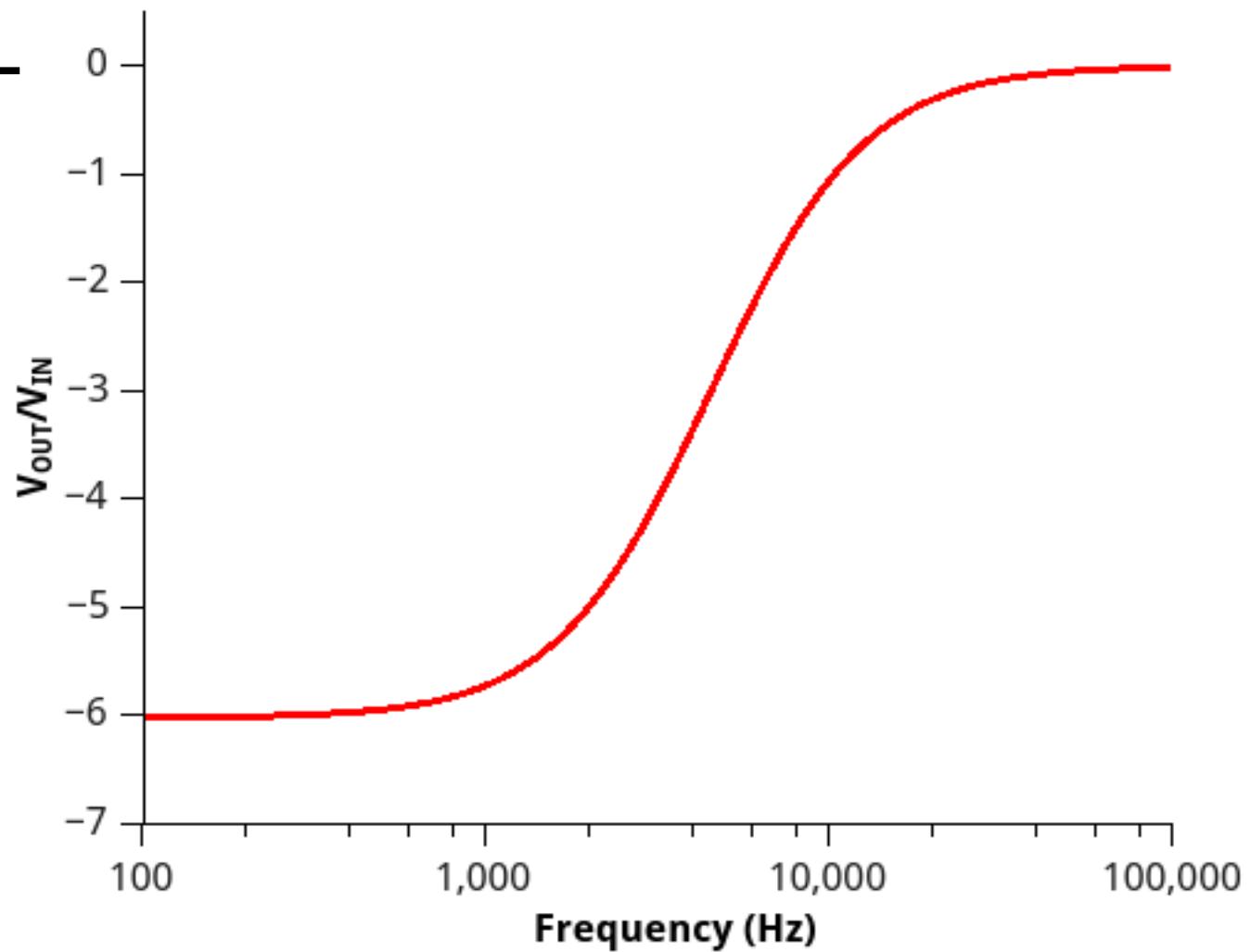$R_1 = R_2 = 500 \Omega$
 $C = 100 \text{ nF}$
 $f_{\text{ZERO}} = 3.2 \text{ kHz}$
 $f_{\text{POLE}} = 6.4 \text{ kHz}$



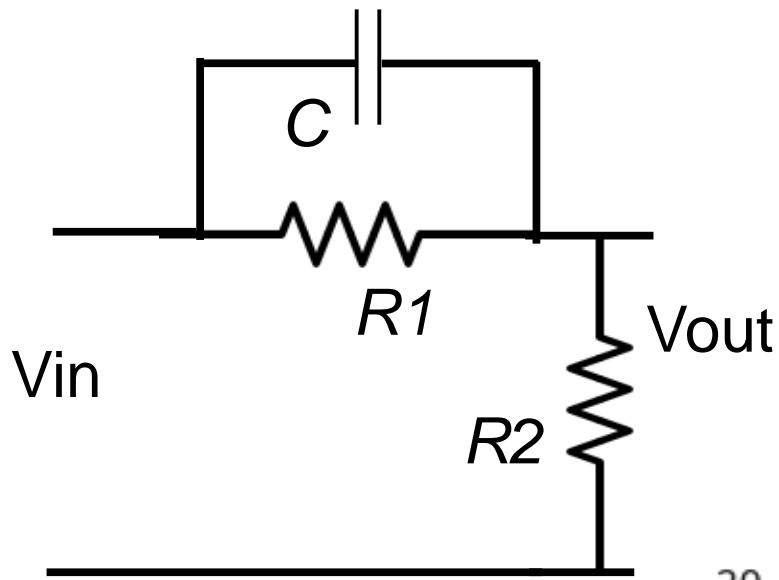

$R_1 = R_2 = 500 \Omega$
 $C = 100 \text{ nF}$
 $f_{\text{ZERO}} = 3.2 \text{ kHz}$
 $f_{\text{POLE}} = 6.4 \text{ kHz}$

