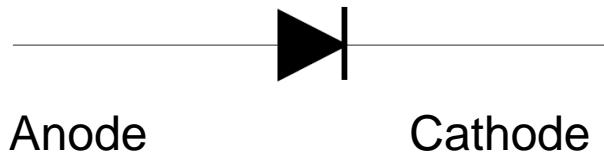



Lab 6: Diodes

Ideal Diode



Ideal Diode

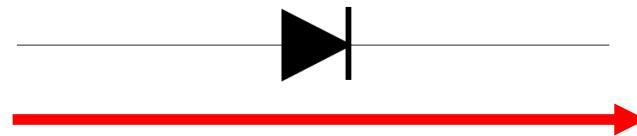
$$V_{\text{Anode}} > V_{\text{Cathode}}$$



Current flows without resistance

Ideal Diode


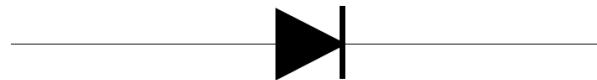
$$V_{\text{Anode}} < V_{\text{Cathode}}$$



No current flow

Current only flows in one direction

Vacuum tube diode

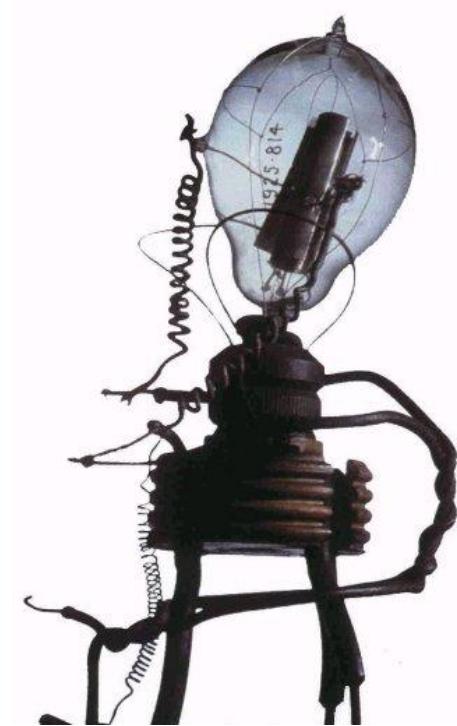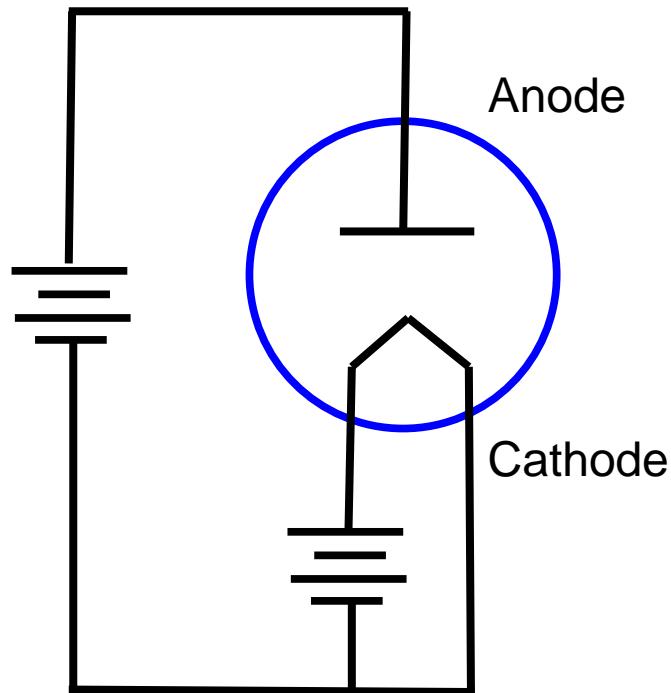


Fleming valve (1904)




J.A. Fleming


Vacuum tube diode

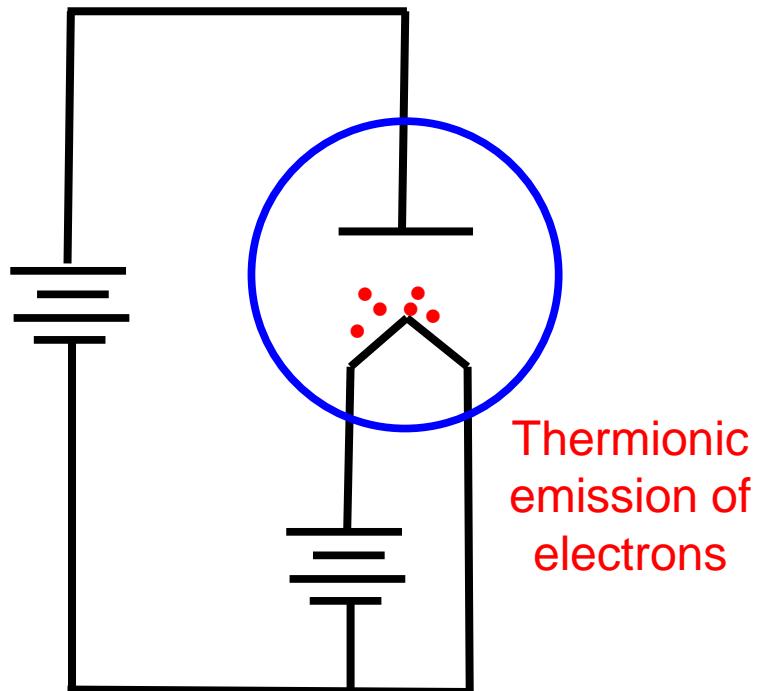


Vacuum tube diode

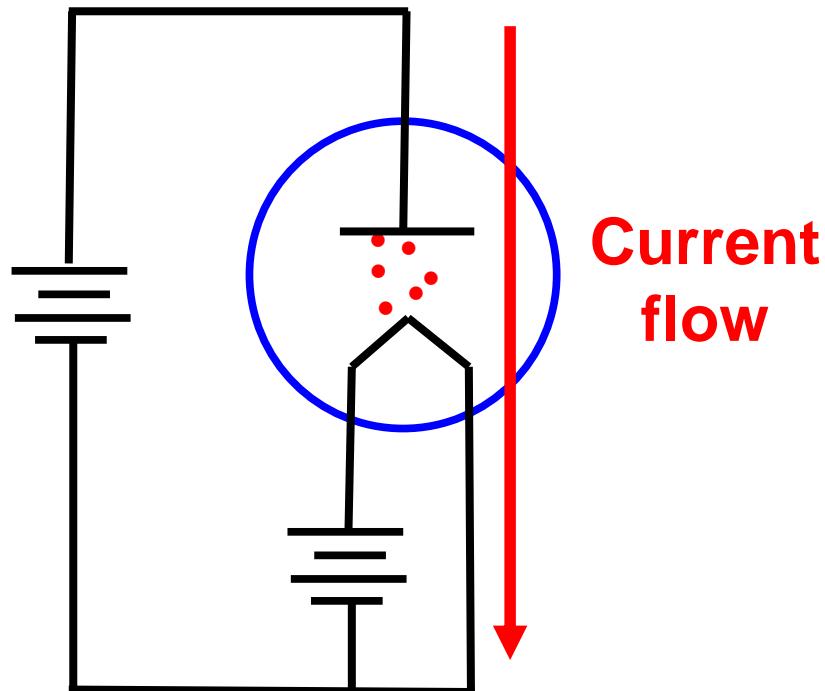

Vacuum tube diode

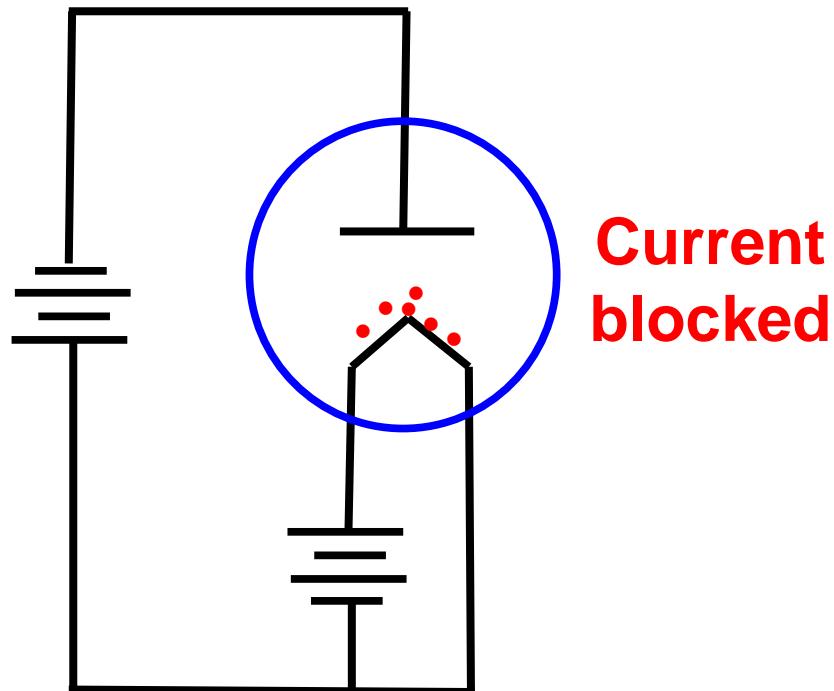


Semiconductor p-n junction


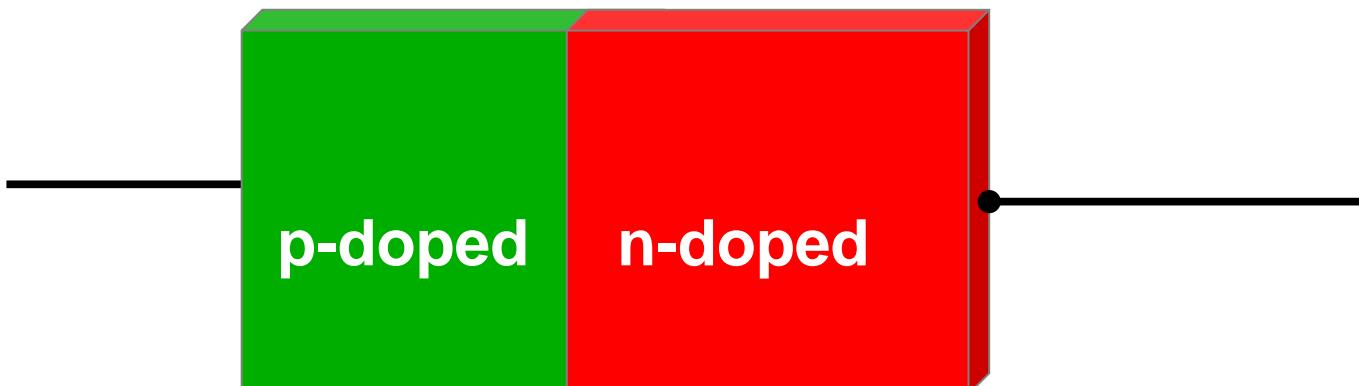


Voltage controlled alignment
of quantum mechanical energy levels


Russel Ohl (1939)

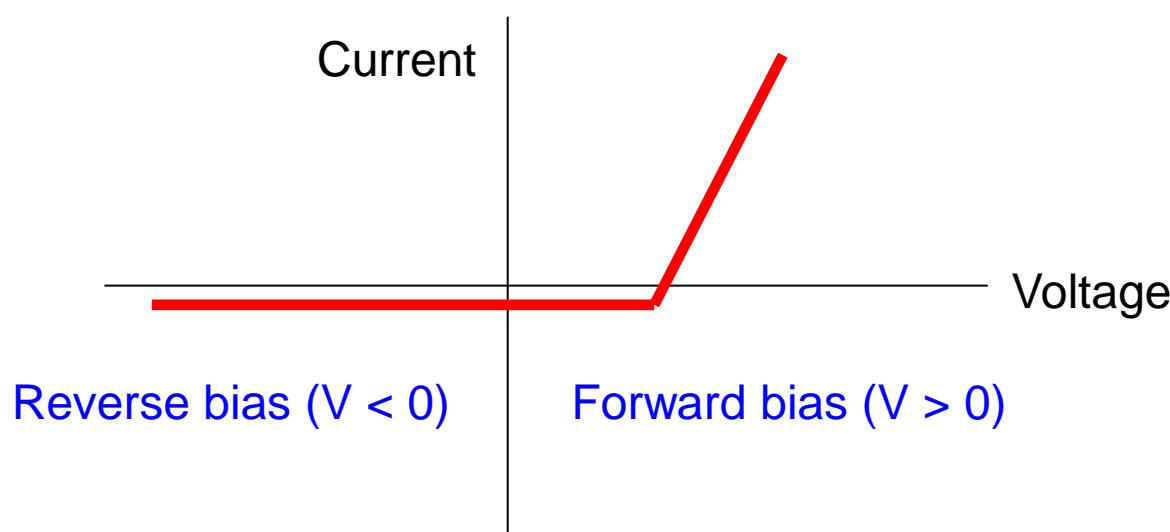


Semiconductor p-n junction

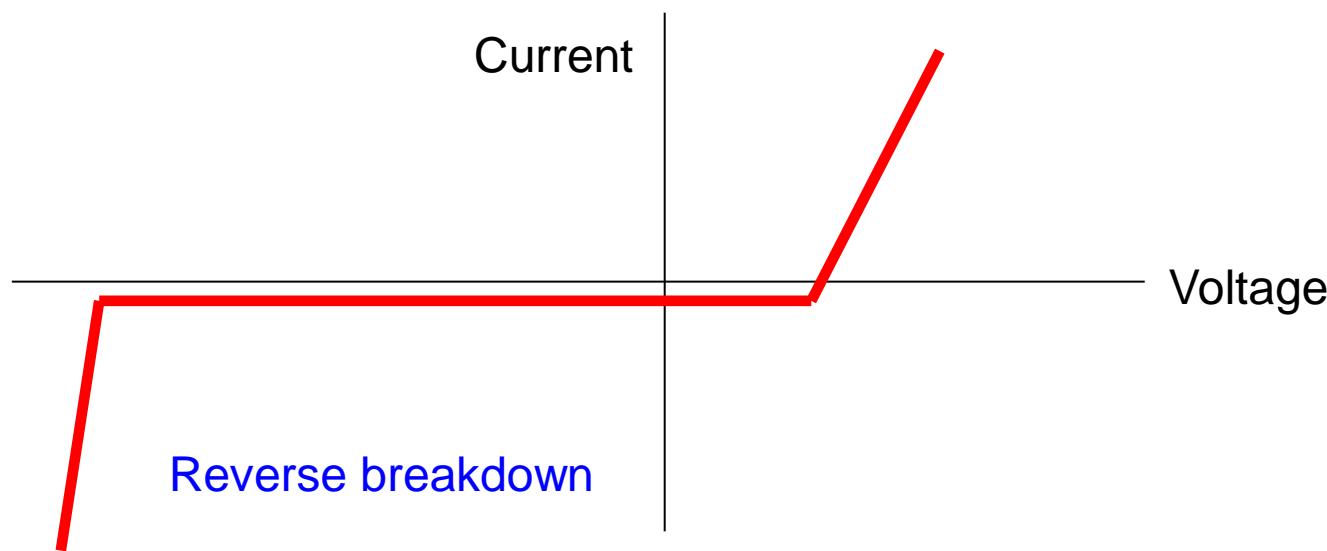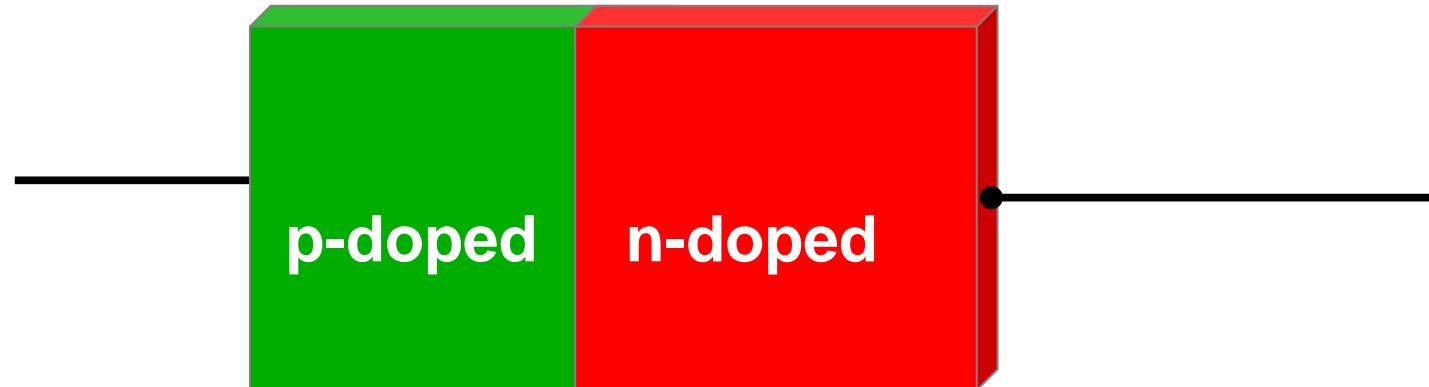


RECTIFICATION: Half-wave rectifier

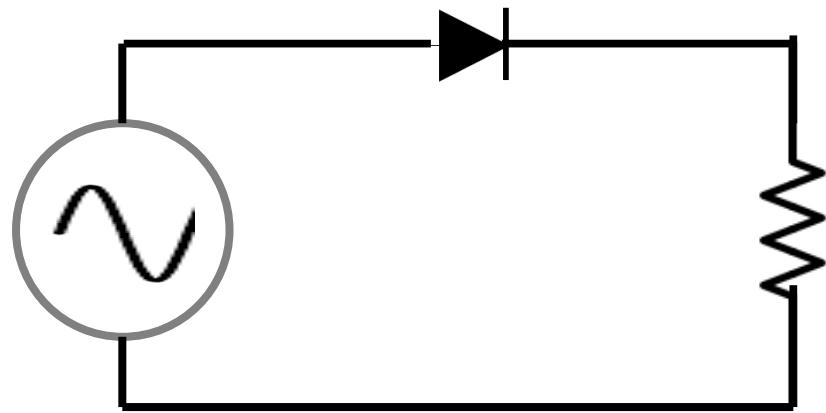


RECTIFICATION: Half-wave rectifier

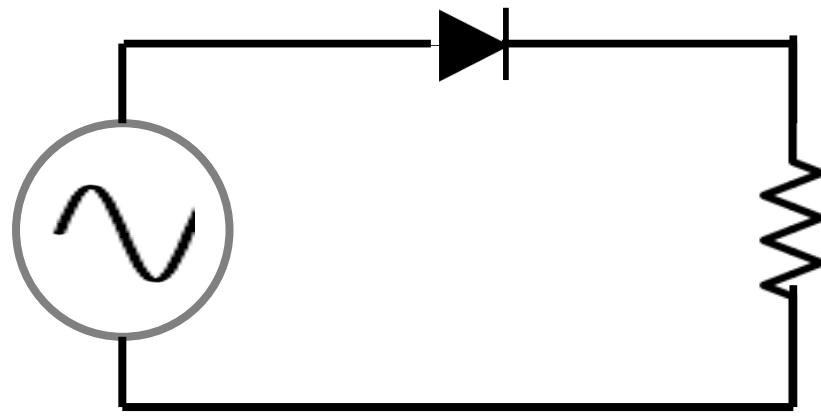


Input current

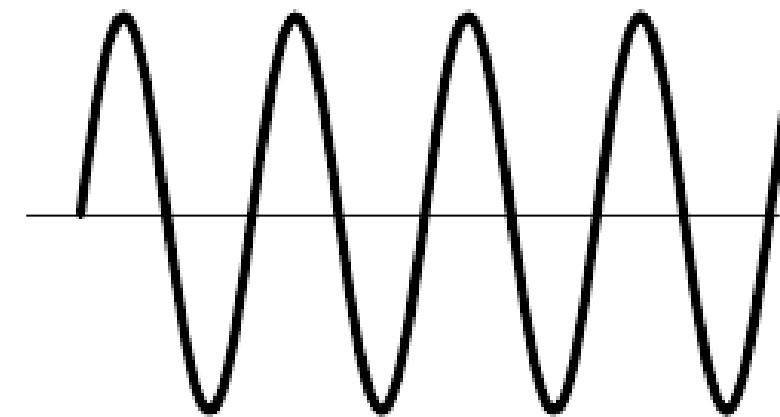


Resistor (output) current

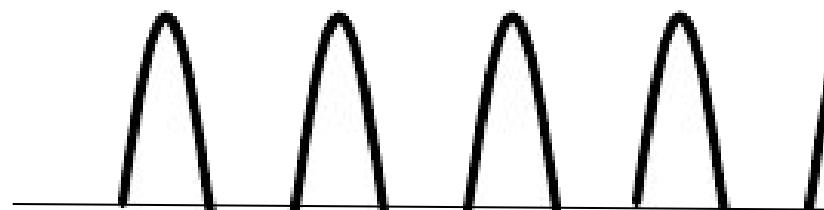


RECTIFICATION: Bridge rectifier

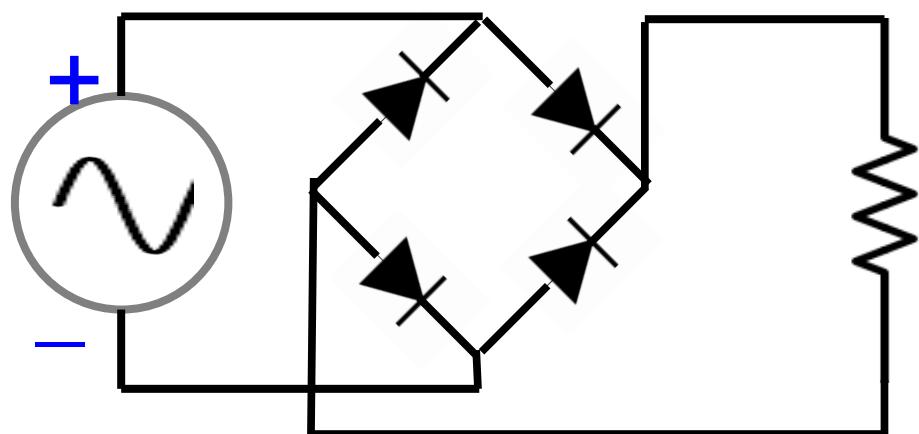


RECTIFICATION: Bridge rectifier

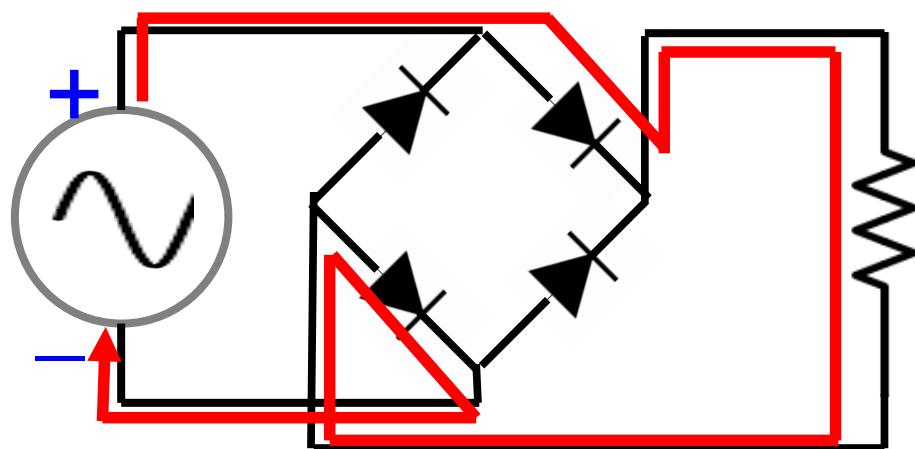


RECTIFICATION: Bridge rectifier

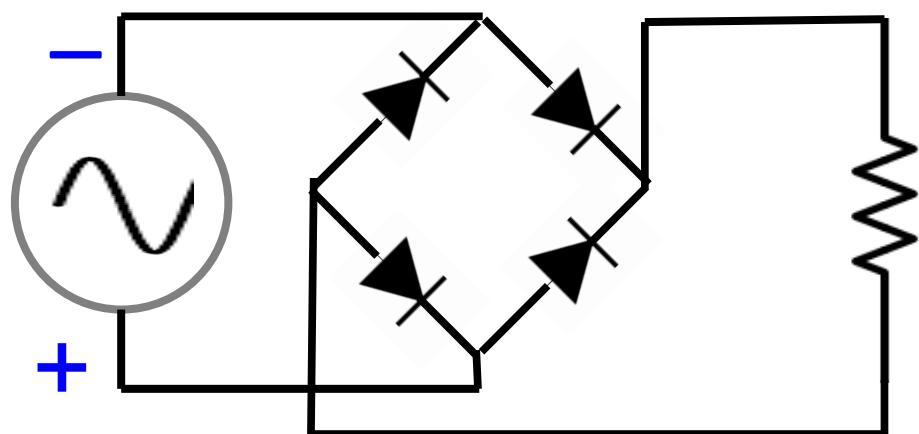


RECTIFICATION: Bridge rectifier

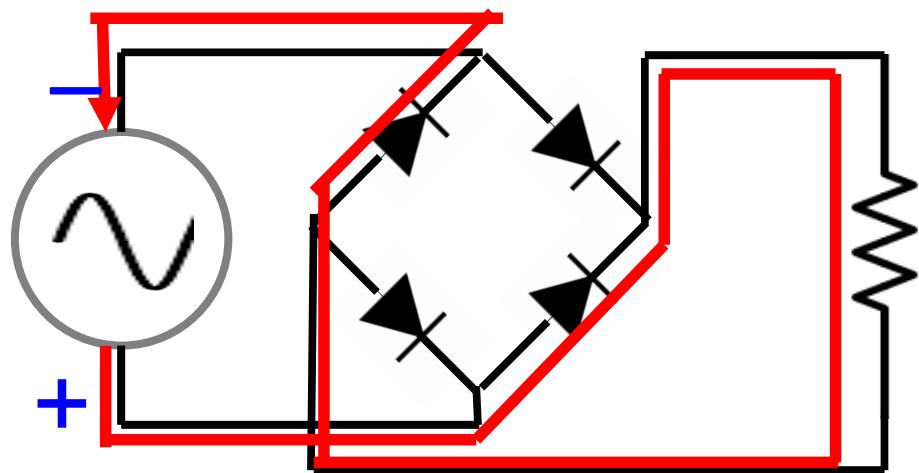

RECTIFICATION: Bridge rectifier

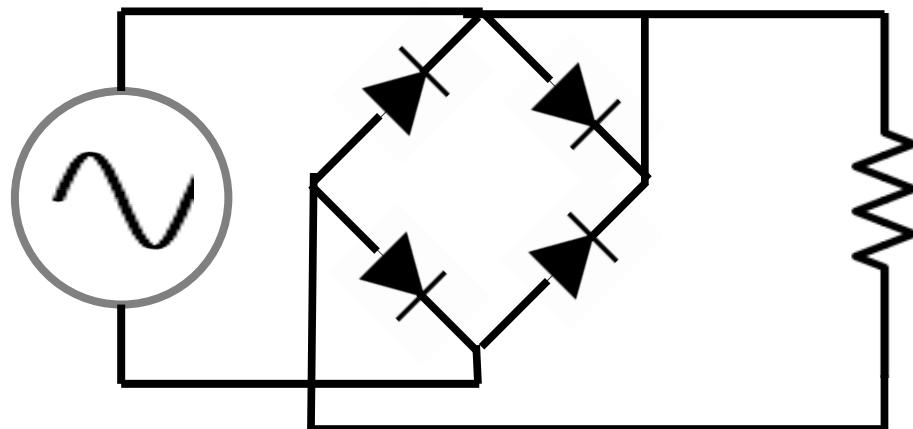


Input current

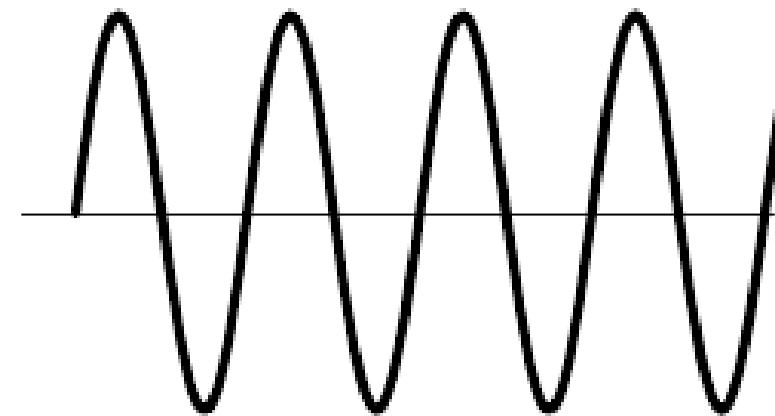


Resistor (output) current



FILTERED RECTIFICATION

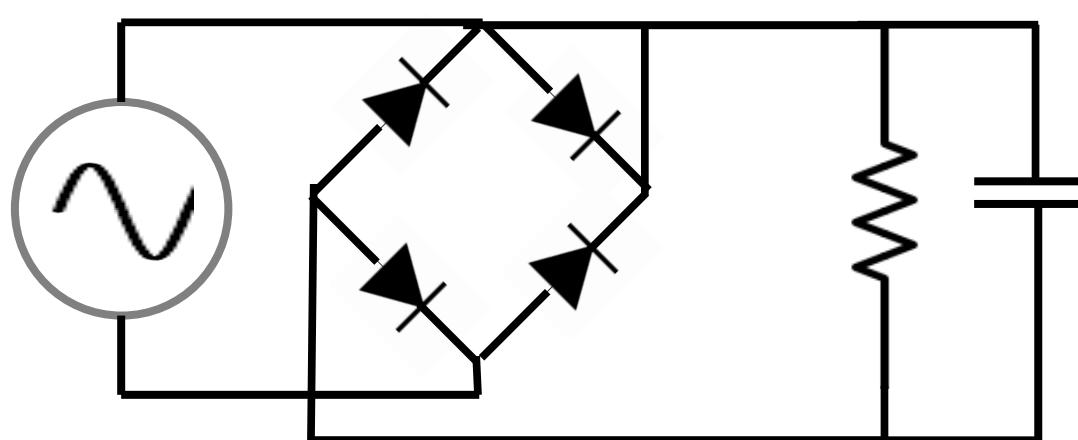

Input current

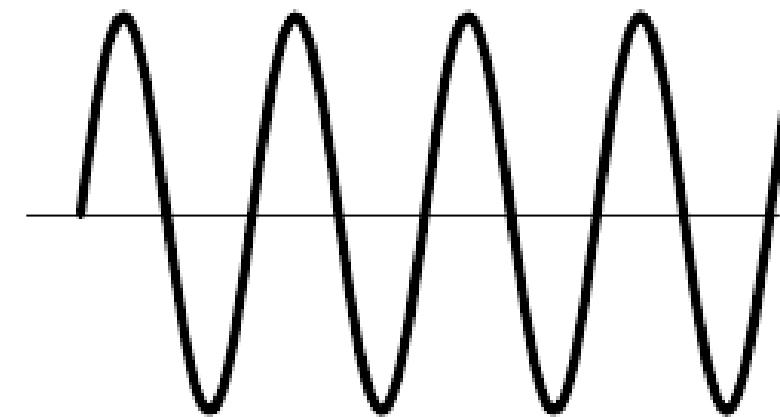

Resistor (output) current

VOLTAGE RIPPLE

