

HW#9 Solutions

25.1

$$I = \frac{V}{R} \quad R_T = R_{Cu} + R_{Ag}$$

$$R_{Cu} = \frac{\rho L}{A} = \frac{(1.72 \times 10^{-9})(0.8)}{\pi \left(\frac{6 \times 10^{-4}}{2}\right)^2} = 0.049 \Omega$$

$$R_{Ag} = \frac{\rho L}{A} = \frac{(1.47 \times 10^{-9})(1.2)}{\pi \left(\frac{6 \times 10^{-4}}{2}\right)^2} = 0.062 \Omega$$

$$I = \frac{V}{R_{Cu} + R_{Ag}} = \frac{5}{0.049 + 0.062} = 45 \text{ A}$$

a. + b.) Conservation of charge requires the charge is the same in both sections

$$\Rightarrow 45 \text{ A}$$

$$c.) E = \rho J = \frac{\rho I}{A} = \frac{IR}{L} \Rightarrow E_{Cu} = \frac{45(0.049)}{0.8} = \boxed{2.76 \text{ V/m}}$$

$$d.) E_{Ag} = \frac{45(0.062)}{1.2} = \boxed{2.33 \text{ V/m}}$$

$$e.) V_{Ag} = IR_{Ag} = (45)(0.062) = \boxed{2.79 \text{ V}}$$

25.2



$$dR = \frac{\rho dx}{A}$$

a.)

$$R = \int P \frac{dx}{A} = \int_0^L (a + bx^2) \frac{dx}{\pi r^2} = \frac{aL + \frac{bL^3}{3}}{\pi r^2}$$

$$\text{at } L=0 \quad f(0) = a + b(0)^2 = a = 2.25 \times 10^{-8}$$

$$\text{@ } L=1.5 \quad f(1.5) = (2.25 \times 10^{-8}) + b(1.5)^2 = 8.5 \times 10^{-8} \\ \Rightarrow b = 2.78 \times 10^{-8}$$

$$\Rightarrow R = \frac{(2.25 \times 10^{-8})(1.5) + \frac{(2.78 \times 10^{-8})(1.5)^3}{3}}{\pi (0.011)^2} = \boxed{1.71 \times 10^{-4} \Omega}$$

$$\text{b.) } E = \frac{\rho I}{\pi r^2} = \frac{[2.25 \times 10^{-8} + 2.78 \times 10^{-8} (.75)^2](1.75)}{\pi (0.011)^2}$$

$$\downarrow \boxed{1.76 \times 10^{-4} \frac{V}{m}}$$

$$\text{c.) } R_1 = \int_0^{L/2} (a + bx^2) \frac{dx}{\pi r^2} = \left[a\left(\frac{L}{2}\right) + b\left(\frac{L}{2}\right)^2 \frac{1}{3} \right] \cdot \frac{1}{\pi r^2} \\ = \boxed{5.47 \times 10^{-5} \Omega}$$

$$R_2 = R_T - R_1 = (1.71 \times 10^{-4}) - (5.47 \times 10^{-5}) = \boxed{1.16 \times 10^{-4} \Omega}$$

25.3

$$a.) V_{c1} = \frac{Q}{C_1} = \frac{18 \mu\text{C}}{2 \mu\text{F}} = 9 \text{ V}$$

$$V_{c1} = V_{c2} = \frac{Q_2}{C_2} = \frac{Q_2}{7 \mu\text{F}} \Rightarrow Q_2 = (9 \text{ V})(7 \mu\text{F}) = \boxed{63 \mu\text{C}}$$

b.) No current flows to the capacitors when they are fully charged so...

$$\mathcal{E} = IR_1 + IR_2$$

$$V_{R2} = V_{c1} = 9 \text{ V} \quad I = \frac{V_{R2}}{R_2} = \frac{9}{3} = 3 \text{ A}$$

$$R_1 = \frac{\mathcal{E} - IR_2}{I} = \frac{62 \text{ V} - 9 \text{ V}}{3 \text{ A}} = \boxed{17.67 \Omega}$$

$$V = \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4} = V$$

(1) $\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$
 $\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$

with each exchange, # of each species is halved
as time passes

$$AS = \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4} \quad VP = \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$$

$$\frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4} \quad \frac{1}{2} \cdot \frac{1}{2} = \frac{1}{4}$$

1000