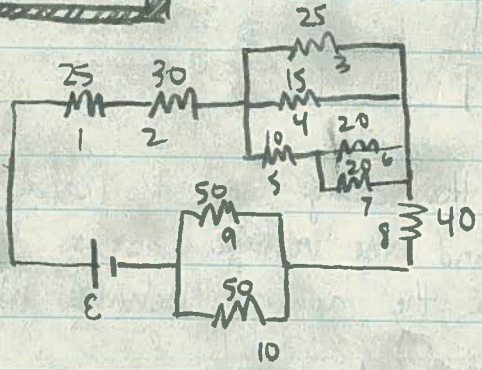


# HW#10 Solutions

26.1




need to find most  $R_{eq}$ :  $R_{9,10}: \frac{1}{R_{eq}} = \frac{1}{R_9} + \frac{1}{R_{10}} = \frac{2}{50}$

$$\frac{1}{R_{6,7}} = \frac{1}{20} + \frac{1}{20} \Rightarrow R_{6,7} = 10 \Omega$$

$$R_{5,6,7} = 20 \Omega$$
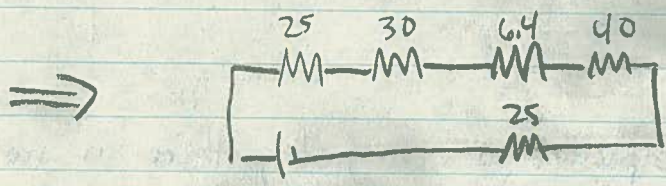
$$\frac{1}{R_{3,4,5,6,7}} = \frac{1}{25} + \frac{1}{15} + \frac{1}{20} = 6.4 \Omega$$




$R=40\Omega$  is the largest resistance so it will limit the max current

$$P = I^2 R \Rightarrow 2.5 = I^2 (40) \Rightarrow I = 0.25 \text{ A}$$

$$E_{max} = IR = (0.25)(25 + 30 + 6.4 + 40 + 25) = 31.6 \text{ V}$$

26.2

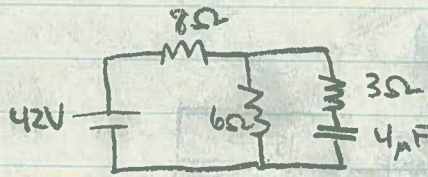

- a.) Initially the charge on the capacitor is  $\emptyset$  and the voltage across it is also  $\emptyset$ .  
→ So the capacitor behaves like a wire.

$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{3} = \frac{3}{6} \Rightarrow R_{eq} = 2\Omega$$

$$42V = I(2+8) \Rightarrow I = \frac{42}{10} = 4.2A$$

$$I_{R8} = 4.2A$$

$$I_{R3} = 2.8A$$

$$I_{R6} = 1.4A$$


- b.) Once the capacitor is charged there is no current through it or  $R = 3\Omega$ .

$$R_{eq} = 8+6 = 14\Omega$$

$$\epsilon = IR \Rightarrow 42 = I(14) \rightarrow \frac{42}{14} = I = 3A$$

↳ the voltage drop across the capacitor and  $R = 6\Omega$  is  $V = (3)(6) = 18V$
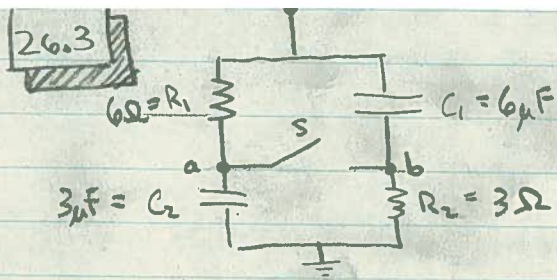
$$Q = VC = (18)(4 \times 10^{-6}) = 7.2 \times 10^{-5} C$$



a.) When  $S$  is open we have a parallel circuit. When the capacitors are fully charged no current flows

$$\Rightarrow V_a = V_b = 18V$$

b.) Point  $a$  is directly connected to the positive terminal so it is at a higher potential.

c.) when  $S$  is closed

$$V = IR \rightarrow I = \frac{18}{(6+3)} = 2A$$

$$\Rightarrow V_b = (2)(3) = 6V$$

d.) Initial values:

$$Q_1 = C_1 V = (6\mu F)(18) = 1.08 \times 10^{-4} C$$

$$Q_2 = C_2 V = (3\mu F)(18) = 5.4 \times 10^{-5} C$$

Final values:

$$Q_1 = C_1 (V_i - V_f) = (6\mu F)(18 - 6) = 7.2 \times 10^{-5} C$$

$$Q_2 = C_2 (V_i - V_f) = (3\mu F)(18 - 2.6) = 1.8 \times 10^{-5} C$$

$$Q_{2i} - Q_{2f} = 3.6 \times 10^{-5} C$$

$$Q_{1i} - Q_{1f} = 3.6 \times 10^{-5} C$$

