

Physics 161.002  
Clicker Quiz: March 6, 2007

4. Four wires meet at a junction. The first carries 4A into the junction, the second carries 5A out of the junction, and the third carries 2A out of the junction. The fourth carries:
- A) 7A out of the junction  
 B) 7A into the junction  
 C) 3A out of the junction  
 D) 3A into the junction  
 E) 1A into the junction
- $\sum I_i = 0$   
 $4 - 5 - 2 + I_4 = 0$   
 $\therefore I_4 = 3A$  into junction.

8. A battery is connected across a series combination of two identical resistors. If the potential difference across the terminals is V and the current in the battery is i, then:
- A) the potential difference across each resistor is V and the current in each resistor is i  
 B) the potential difference across each resistor is V/2 and the current in each resistor is i/2  
 C) the potential difference across each resistor is V and the current in each resistor is i/2  
 D) the potential difference across each resistor is V/2 and the current in each resistor is i  
 E) none of the above are true


9. A battery is connected across a parallel combination of two identical resistors. If the potential difference across the terminals is V and the current in the battery is i, then:
- A) the potential difference across each resistor is V and the current in each resistor is i  
 B) the potential difference across each resistor is V/2 and the current in each resistor is i/2  
 C) the potential difference across each resistor is V and the current in each resistor is i/2  
 D) the potential difference across each resistor is V/2 and the current in each resistor is i  
 E) none of the above are true

16. Nine identical wires, each of diameter d and length L, are connected in parallel. The combination has the same resistance as a single similar wire of length L but whose diameter is:
- A) 3d  
 B) 9d  
 C) d/3  
 D) d/9  
 E) d/81
- $R = \frac{\rho L}{A} = \frac{\rho L}{\pi (d/2)^2}$   
 $R_{11} = R/9 = \frac{\rho L}{\pi (D/2)^2}$   
 $\therefore D = 3d$

19. Two wires made of the same material have the same length but different diameter. They are connected in series to a battery. The quantity that is the same for the wires is:
- A) the end-to-end potential difference  
 B) the current  
 C) the current density  
 D) the electric field  
 E) the electron drift velocity


26. The emf of a battery is equal to its terminal potential difference: under all conditions
- A) only when the battery is being charged  
 B) only when a large current is in the battery  
 C) only when there is no current in the battery  
 D) only when there is no current in the battery  
 E) under no conditions
- $V_{terminal} = \mathcal{E} - I r_{internal}$

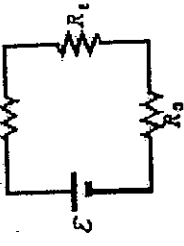30. In the diagram  $R_1 > R_2 > R_3$ . Rank the three resistors according to the current in them, least to greatest.



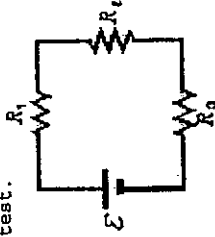- A) 1, 2, 3  
 B) 3, 2, 1  
 C) 1, 3, 2  
 D) 3, 1, 2  
 E) All are the same

- 30P. In the diagram  $R_1 > R_2 > R_3$ . Rank the three resistors according to the voltage drops across them, least to greatest.



- A) 1, 2, 3  
 B) 3, 2, 1  
 C) 1, 3, 2  
 D) 3, 1, 2  
 E) All are the same


$V_i = I R_i$

46. In an antique automobile, a 6-V battery supplies a total of 48 W to two identical headlights in parallel. The resistance (in ohms) of each bulb is:

- A) 0.67  
 B) 1.5  
 C) 3  
 D) 4  
 E) 8

$Power = 2 \times \frac{V^2}{R}$   
 $\therefore R = \frac{2 \times V^2}{Power} = \frac{2 \times (6V)^2}{48W} = 1.5 \Omega$   
 #lights  $\rightarrow R$

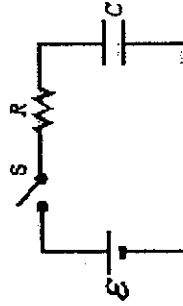59. Four circuits have the form shown in the diagram. The capacitor is initially uncharged and the switch S is open.



The values of the emf, resistance 'R', and capacitance 'C' for each of the circuits are


- circuit 1: emf = 18 V, R = 3 ohms, C = 1 microF  
 circuit 2: emf = 18 V, R = 6 ohms, C = 9 microF  
 circuit 3: emf = 12 V, R = 1 ohms, C = 7 microF  
 circuit 4: emf = 10 V, R = 5 ohms, C = 7 microF

Rank the circuits according to the current just after switch S is closed least to greatest.

- A) 1, 2, 3, 4  
 B) 4, 3, 2, 1  
 C) 4, 2, 3, 1  
 D) 4, 2, 1, 3  
 E) 3, 1, 2, 4

because at  $t=0$  voltage across the capacitor = 0 (C=0) = 0

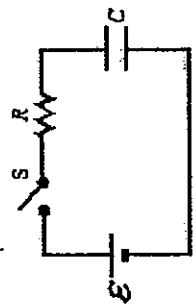60. Four circuits have the form shown in the diagram. The capacitor is initially uncharged and the switch S is open.



The values of the emf, resistance 'R', and capacitance 'C' for each for the circuits are

- circuit 1: emf = 18 V, R = 3 ohms, C = 1 microF
- circuit 2: emf = 18 V, R = 6 ohms, C = 9 microF
- circuit 3: emf = 12 V, R = 1 ohms, C = 7 microF
- circuit 4: emf = 10 V, R = 5 ohms, C = 7 microF

$$RC = 3 \times 10^{-6} \times 1 = 3 \mu s$$

$$= 6 \times 9 \times 10^{-6} = 54 \mu s$$

$$= 1 \times 7 \times 10^{-6} = 7 \mu s$$

$$= 5 \times 7 \times 10^{-6} = 35 \mu s$$

Rank the circuits according to the time after the switch 'S' is closed for the capacitor to reach half their final charge, least to greatest.

- A) 1, 2, 3, 4
- B) 4, 3, 2, 1
- C) 1, 3, 4, 2
- D) 4, 2, 1, 3
- E) 3, 1, 2, 4

→ depends on  $\tau = RC$