


HWWS solutions

29.36 a)  $j_D = \frac{i}{A} = \frac{0.28 \text{ A}}{\pi (0.04 \text{ m})^2} = 55.7 \text{ A/m}^2$

b)  $j_D = \epsilon_0 \frac{dE}{dt}$  so  $\frac{dE}{dt} = 6.3 \times 10^{12} \text{ V/m.s}$

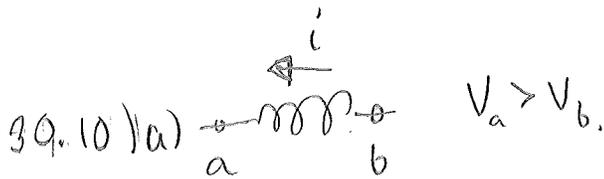c)  $\oint \vec{B} \cdot d\vec{l} = \mu_0 \epsilon_0 \frac{dE}{dt} = \mu_0 j_D A = \mu_0 j_D \pi r^2$


$B \cdot 2\pi r = \mu_0 j_D \pi r^2 \quad B = \frac{\mu_0 j_D r}{2} = 7 \times 10^{-7} \text{ T}$



looks like:  so current must be decreasing.

b)  $V = 1.04 \text{ V} = L \frac{di}{dt}$  with  $L = 0.26 \text{ H}$ ,  $\left| \frac{di}{dt} \right| = 4 \text{ A/s}$

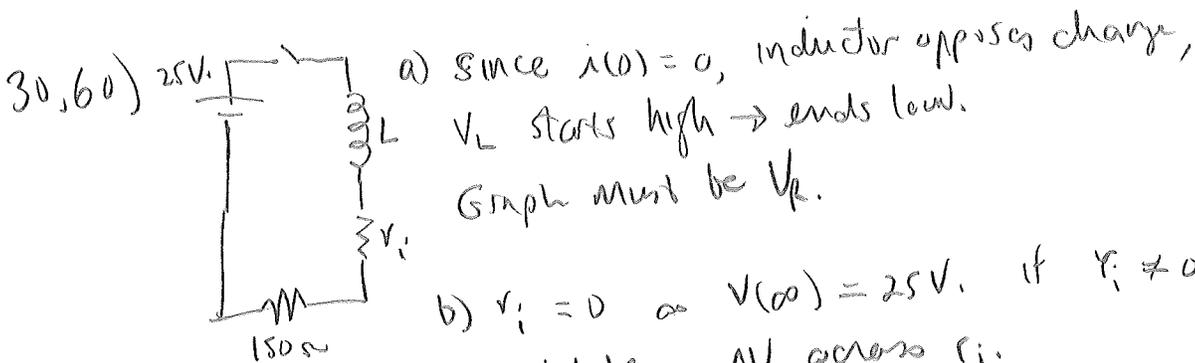Current after 2 seconds =  $12 \text{ A} - 4.2 \text{ A} = 7.8 \text{ A}$



b)  $r_i = 0 \Rightarrow V(\infty) = 25 \text{ V}$ . if  $r_i \neq 0$ , there would be a  $\Delta V$  across  $r_i$ .

$V_R = V_{\text{max}} (1 - e^{-t/\tau})$  At  $t = \tau$ ,  $V_R \approx 0.63 V_{\text{max}} = 16 \text{ V}$ .

so  $\tau = 0.5 \text{ ms} = L/R = L/150 \Omega \quad L = 0.075 \text{ H}$

