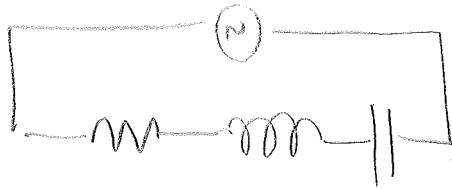


31.42.



	X_{200}	X_{1000}	
R	200	200	} mΩ
L	80	400	
C	833	167	

$V = IX$

$X_L = \omega L$

$X_C = \frac{1}{\omega C}$

$V_1 = V_R$


$V_2 = V_L$

$V_3 = V_C$

$V_4 = \vec{V}_L + \vec{V}_C$

$V_5 = \text{EMF}$

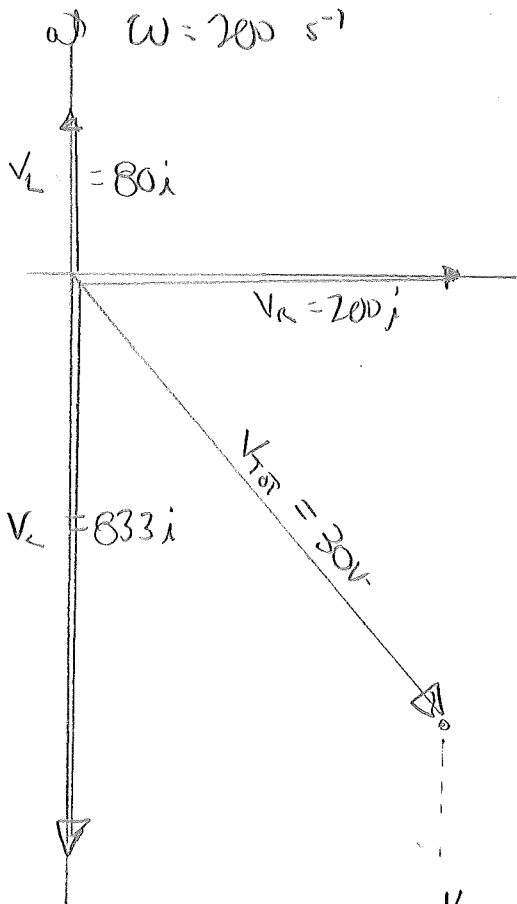$V_{5, \text{RMS}} = \frac{30}{\sqrt{2}}$ always
 $= 21.2 \text{ V}$




$V_{TOT} = ((833-80)^2 + 200^2)^{1/2} i$
 $i = 38.5 \text{ mA}$

$V_{1, \text{RMS}} = \frac{iR}{\sqrt{2}} = 5.44 \text{ V}$

$V_{2, \text{RMS}} = \frac{iX_L}{\sqrt{2}} = 2.18 \text{ V}$

$V_{3, \text{RMS}} = \frac{iX_C}{\sqrt{2}} = 22.7 \text{ V}$

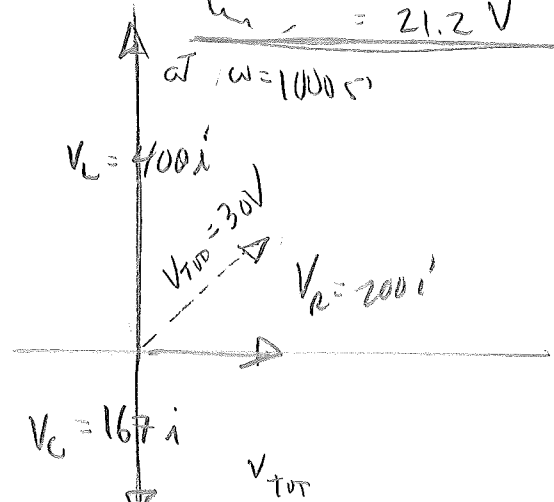$V_{4, \text{RMS}} = \frac{i(833-80)}{\sqrt{2}} = 20.5 \text{ V}$



$V_{TOT} = ((400-167)^2 + 200^2)^{1/2} i$
 $i = 98 \text{ mA}$


$V_{1, \text{RMS}} = \frac{iR}{\sqrt{2}} = 13.8 \text{ V}$

$V_{2, \text{RMS}} = \frac{iX_L}{\sqrt{2}} = 27.7 \text{ V}$

$V_{3, \text{RMS}} = 11.6 \text{ V}$

$V_{4, \text{RMS}} = 16.1 \text{ V}$

31.51. a)

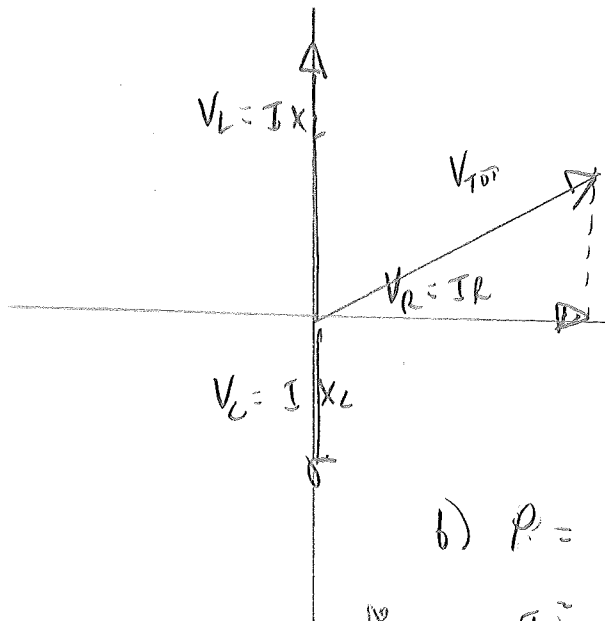

$$V_{TOT} = [(I X_L - I X_C)^2 + (I R)^2]^{1/2}$$

$$V_{TOT} = I (X_L - X_C)^2 + R^2)^{1/2}$$

$$I = \frac{V}{\sqrt{(X_L - X_C)^2 + R^2}}$$

Q.E.D. ω ,
 $X_L = \omega L$
 $X_C = \frac{1}{\omega C}$

b) $P = I^2 R$ where $I = I_{RMS}$!


$$P = \left(\frac{I}{R}\right)^2 R = \frac{V^2 R / R^2}{R^2 + (X_L - X_C)^2}$$

c) Both maximize with smallest denominator, at $X_L = X_C$.


$$\frac{1}{\omega C} = \omega L \quad \text{or} \quad \omega = 1/\sqrt{LC}$$

d)
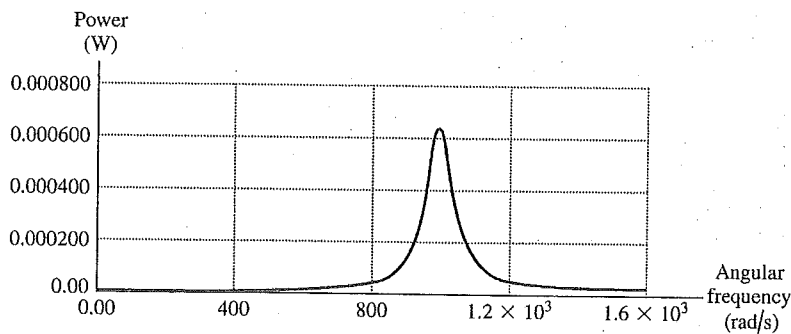
$$(d) P_{av} = \frac{(100 \text{ V})^2 (200 \Omega) / 2}{(200 \Omega)^2 + (\omega(2.00 \text{ H}) - 1/[\omega(0.500 \times 10^{-6} \text{ F})])^2} = \frac{25\omega^2}{40,000\omega^2 + (2\omega^2 - 2,000,000)^2}$$




31.54:

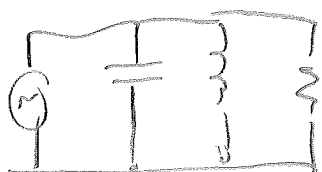

in parallel $V_L = V_C = V_R = \mathcal{E}$

$$I_L + I_C + I_R = I$$

31.54 continued (b, c)

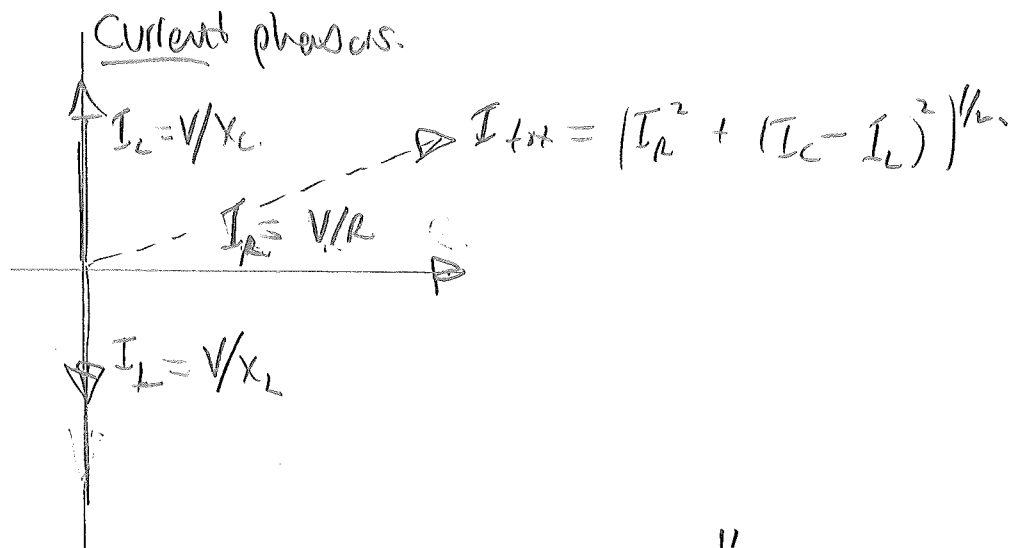

$$(d) \quad I_{tot} = \left[\frac{V^2}{R^2} + \left(\frac{V}{X_C} - \frac{V}{X_L} \right)^2 \right]^{1/2}$$
$$= V \cdot \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L} \right)^2}$$