

36

AC Circuits

36.1 AC Sources and Phasors


1. The figure shows emf phasors A, B, and C.

a. What is the instantaneous value of the emf?

A _____ B _____ C _____

b. At this instant, is the magnitude of the emf increasing, decreasing, or holding constant?

A _____ B _____ C _____



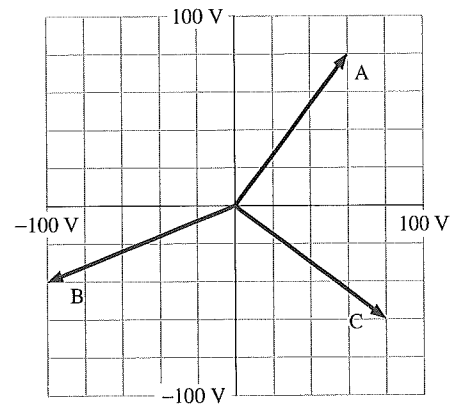


2. Draw a phasor diagram for the following emfs.

a. $(100 \text{ V}) \cos \omega t$ at $\omega t = 240^\circ$

b. $(400 \text{ V}) \cos \omega t$ at $t = \frac{1}{3}T$

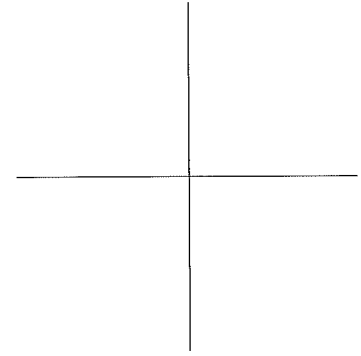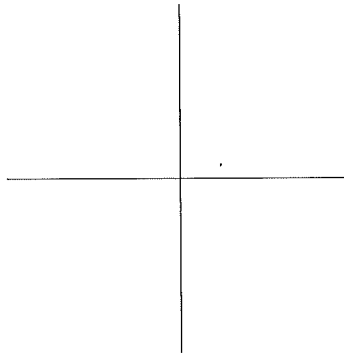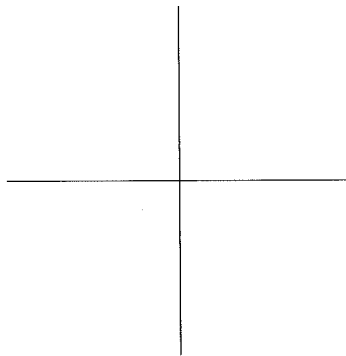
c. $(200 \text{ V}) \cos \omega t$ at $t = 0$



3. The current phasor is shown for a 10Ω resistor.

a. What is the instantaneous resistor voltage v_R ?

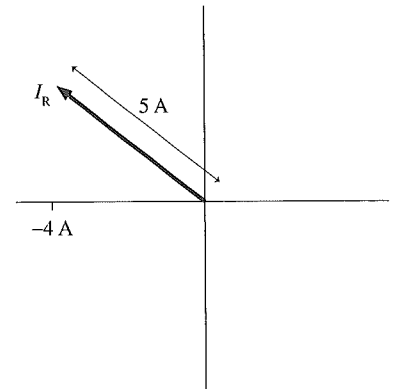b. What is the peak resistor voltage V_R ?



4. The peak current through a resistor is 4.0 A. What is the peak current if:

a. The resistance R is doubled?

b. The peak emf \mathcal{E}_0 is doubled?

c. The frequency ω is doubled?

36.2 Capacitor Circuits

5. The peak current through a capacitor is 4.0 A. What is the peak current if:

a. The peak emf \mathcal{E}_0 is doubled?


b. The capacitance C is doubled?

c. The frequency ω is doubled?


6. Current and voltage graphs are shown for a capacitor circuit with $\omega = 1000$ rad/s.

a. What is the capacitive reactance X_C ?


b. What is the capacitance C ?

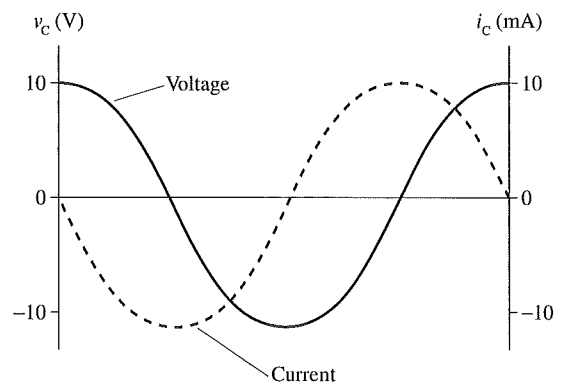

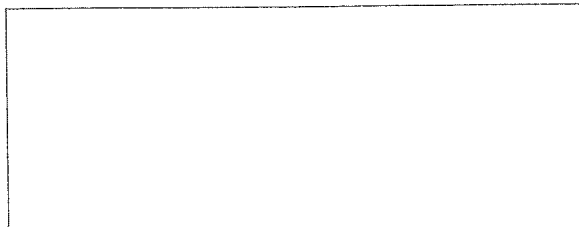7. A $13 \mu\text{F}$ capacitor is connected to a $5.5 \text{ V}/250 \text{ Hz}$ oscillator. What is the instantaneous capacitor current i_C when $\mathcal{E} = -5.5 \text{ V}$?



8. Consider these three circuits.

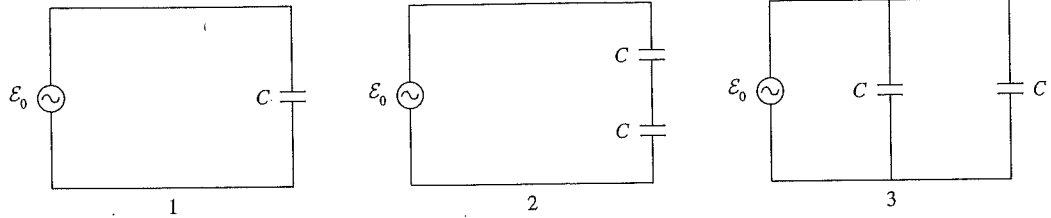


- Rank in order, from largest to smallest, the peak currents $(I_C)_1$ to $(I_C)_3$ provided by the emf.

Order:

Explanation:


9. Consider these four circuits.

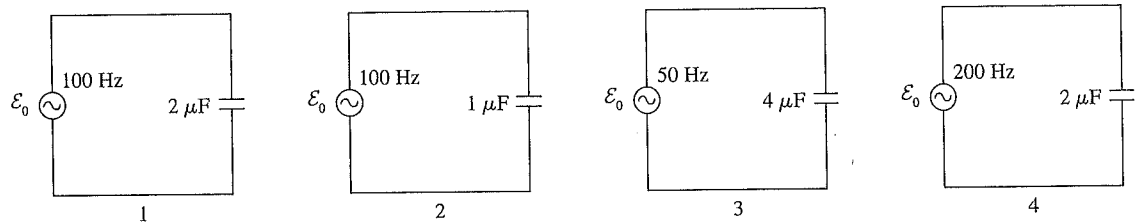

- Rank in order, from largest to smallest, the capacitive reactances $(X_C)_1$ to $(X_C)_4$.

Order:

Explanation:

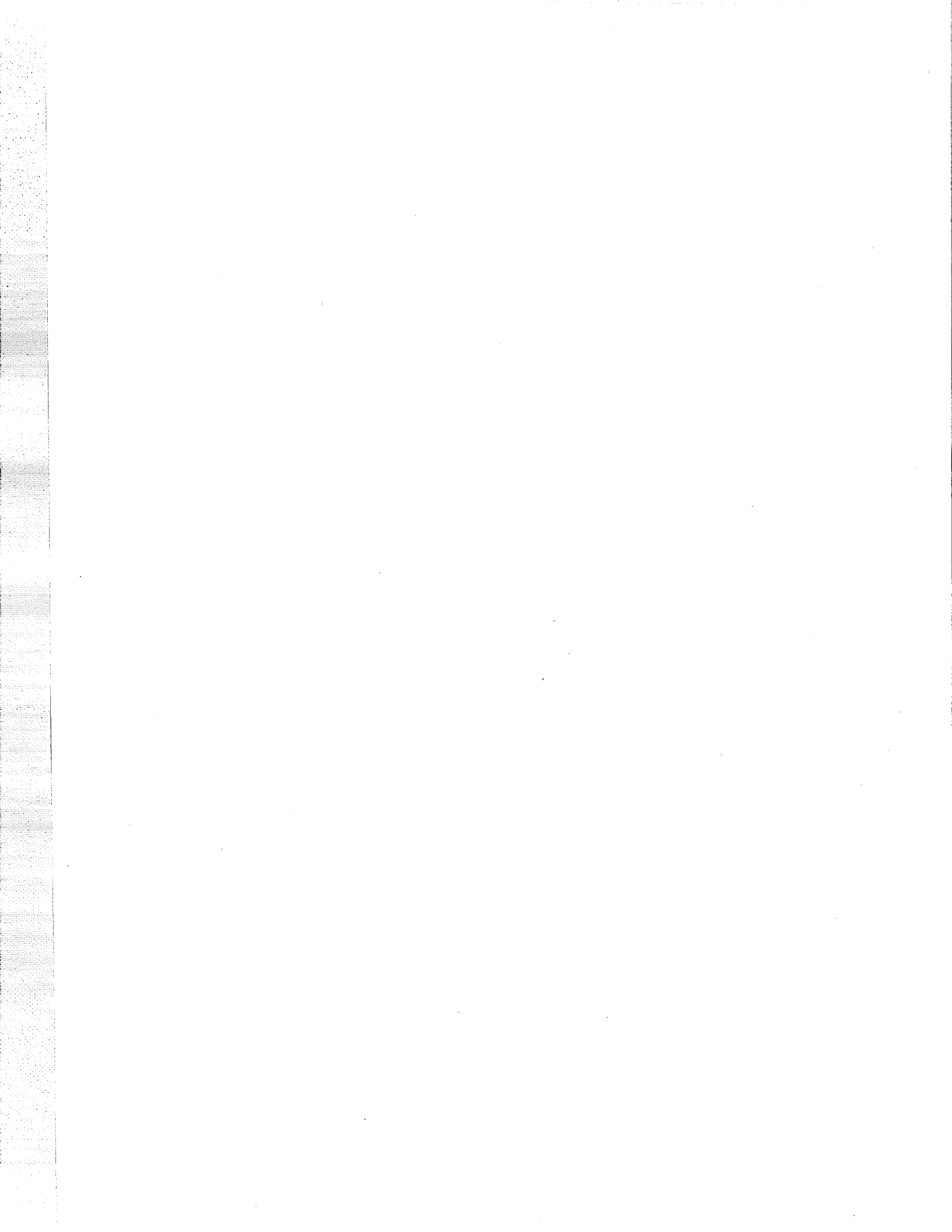

36.4 Inductor Circuits

14. The peak current passing through an inductor is 4.0 A. What is the peak current if:

a. The peak emf \mathcal{E}_0 is doubled?


b. The inductance L is doubled?

c. The frequency ω is doubled?





15. Current and voltage graphs are shown for an inductor circuit with $\omega = 1000$ rad/s.

a. What is the inductive reactance X_L ?

b. What is the inductance L ?

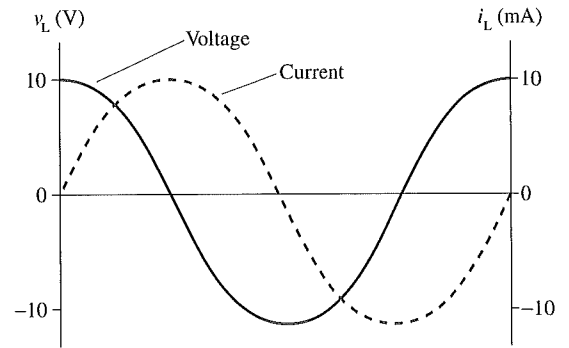

16. Consider these four circuits.

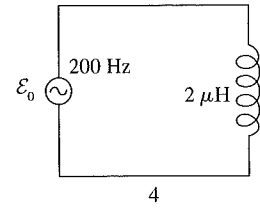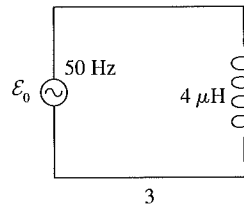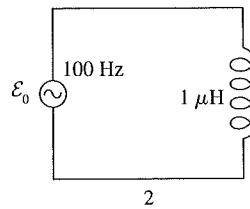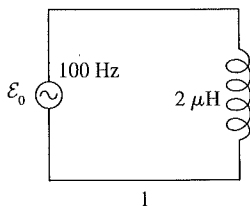

Rank in order, from largest to smallest, the inductive reactances $(X_L)_1$ to $(X_L)_4$.

Order:

Explanation:

36.5 The Series *RLC* Circuit

17. The resonance frequency of a series *RLC* circuit is 1000 Hz. What is the resonance frequency if:

a. The resistance R is doubled?

b. The inductance L is doubled?

c. The capacitance C is doubled?


d. The peak emf \mathcal{E}_0 is doubled?

e. The frequency ω is doubled?

18. For these combinations of resistance and reactance, is a series *RLC* circuit in resonance (Yes or No)? Does the current lead the emf, lag the emf, or is it in phase with the emf?


R	X_L	X_C	Resonance?	Current?
100 Ω	100 Ω	50 Ω	_____	_____
100 Ω	50 Ω	100 Ω	_____	_____
100 Ω	75 Ω	75 Ω	_____	_____

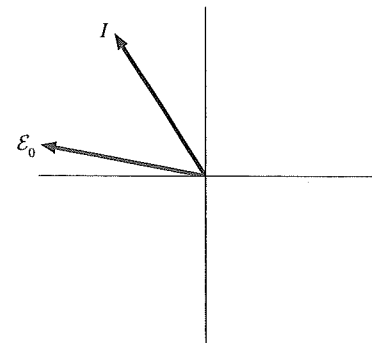19. In this series *RLC* circuit, is the emf frequency less than, equal to, or greater than the resonance frequency ω_0 ? Explain.



20. The resonance frequency of a series *RLC* circuit is greater than the emf frequency. Does the current lead or lag the emf? Explain.

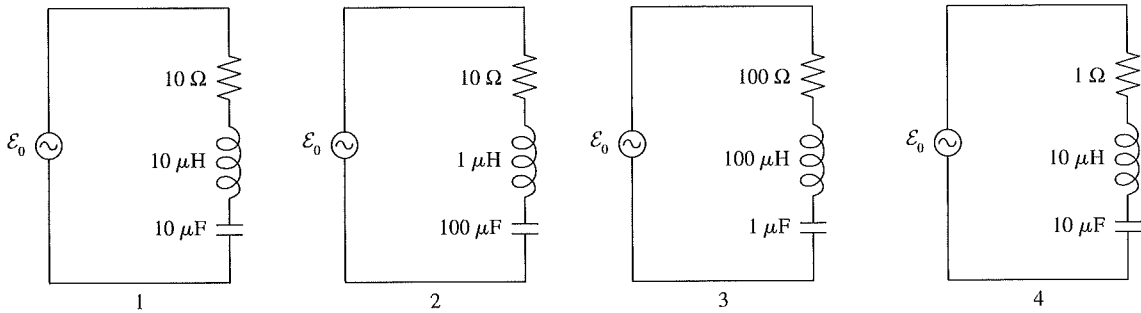21. Consider these four circuits. They all have the same resonance frequency ω_0 .



Rank in order, from largest to smallest, the maximum currents $(I_{\max})_1$ to $(I_{\max})_4$.

Order:

Explanation:

22. The current in a series *RLC* circuit lags the emf by 20° . You cannot change the emf. What two different things could you do to the circuit that would increase the power delivered to the circuit by the emf?

36.6 Power in AC Circuits




23. An average power dissipated by a resistor is 4.0 W. What is P_{avg} if:

a. The resistance R is doubled?

b. The peak emf \mathcal{E}_0 is doubled?

c. Both are doubled simultaneously?

24. Consider these three circuits.

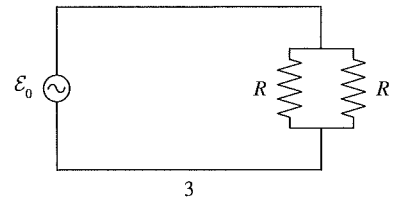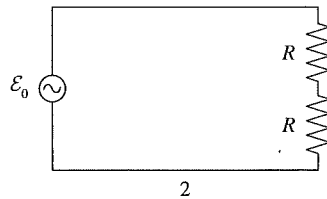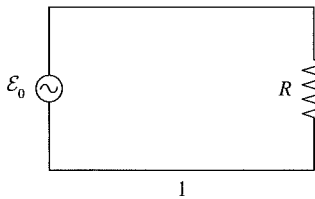

Rank in order, from largest to smallest, the average powers P_1 to P_3 delivered by the three emfs.

Order:

Explanation:
