

36 AC Circuits

36.1 AC Sources and Phasors


1. The figure shows emf phasors A, B, and C.

a. What is the instantaneous value of the emf? *x-axis proj.*

A 60V B -100V C 80V

b. At this instant, is the magnitude of the emf increasing, decreasing, or holding constant?

A dec. B dec. C incr.



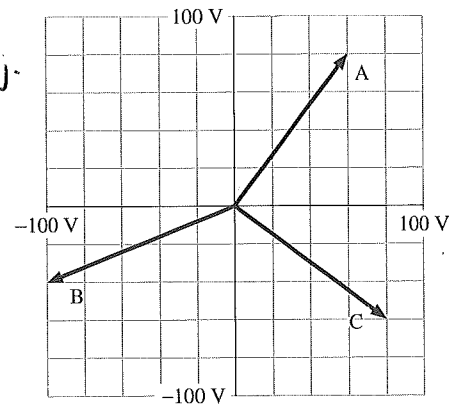


2. Draw a phasor diagram for the following emfs.

a. $(100 \text{ V}) \cos \omega t$ at $\omega t = 240^\circ$

b. $(400 \text{ V}) \cos \omega t$ at $t = \frac{1}{3}T$

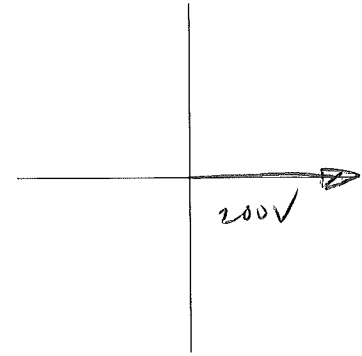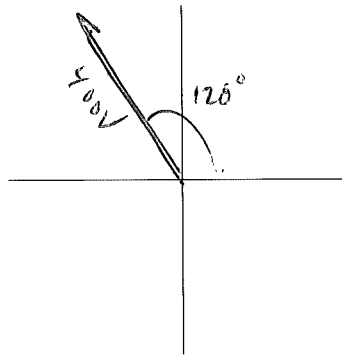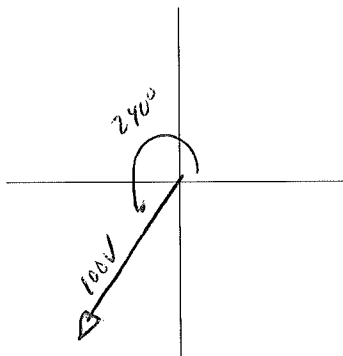c. $(200 \text{ V}) \cos \omega t$ at $t = 0$




3. The current phasor is shown for a 10Ω resistor.

a. What is the instantaneous resistor voltage v_R ?

$$i = -4 \text{ A} \quad V = iR = 40 \text{ V}$$

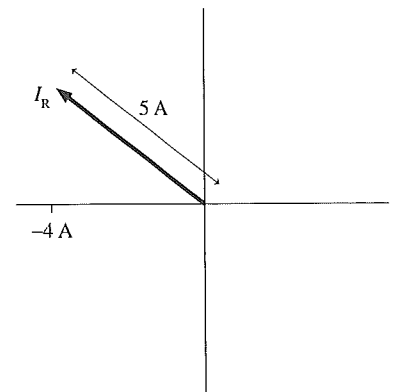b. What is the peak resistor voltage V_R ?

$$i_p = 5 \text{ A} \quad V = iR = 50 \text{ V}$$



4. The peak current through a resistor is 4.0 A. What is the peak current if:

a. The resistance R is doubled?

$$V = IR \quad R \uparrow 2x \quad I \downarrow 2x \quad (2A)$$

b. The peak emf \mathcal{E}_0 is doubled?

$$I \uparrow 2x \quad (8A)$$

c. The frequency ω is doubled?

$$(4A) \quad \text{No effect.}$$

36.2 Capacitor Circuits

5. The peak current through a capacitor is 4.0 A. What is the peak current if:

a. The peak emf \mathcal{E}_0 is doubled?

$$V = IX \quad X = \frac{1}{\omega C} \quad \mathcal{E} = V = \frac{I}{\omega C} \quad \mathcal{E} \uparrow 2x \Rightarrow I \uparrow 2x \quad (8A)$$

b. The capacitance C is doubled?

$$C \uparrow 2x \Rightarrow I \uparrow 2x \quad (8A)$$

c. The frequency ω is doubled?

$$\omega \uparrow 2x \Rightarrow I \uparrow 2x \quad (8A)$$

6. Current and voltage graphs are shown for a capacitor circuit with $\omega = 1000$ rad/s.


a. What is the capacitive reactance X_C ?

$$V = iX_C \quad X_C = \frac{10V}{10mA} = 1k\Omega$$


b. What is the capacitance C ?

$$X_C = \frac{1}{\omega C} = 1k\Omega$$




$$C = 10^{-6} F = 1 \mu F$$

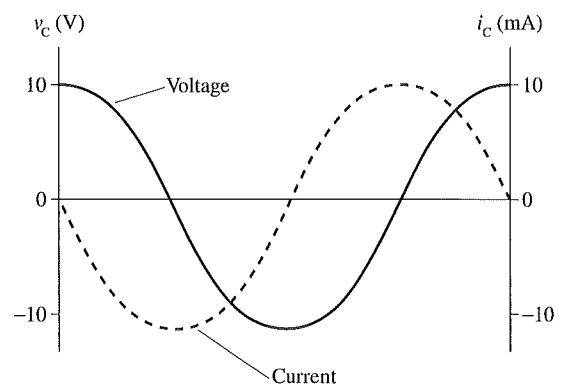

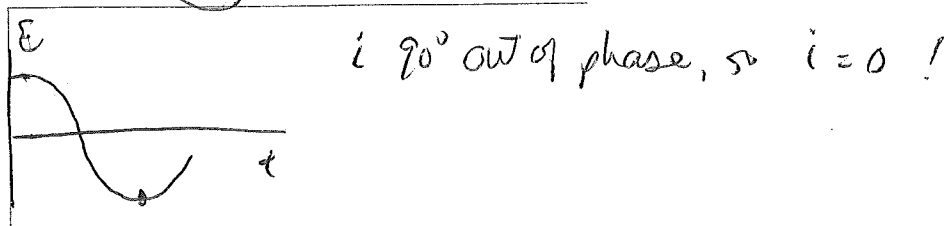7. A $13 \mu\text{F}$ capacitor is connected to a $(5.5 \text{ V})/250 \text{ Hz}$ oscillator. What is the instantaneous capacitor current i_C when $\mathcal{E} = -5.5 \text{ V}$?







8. Consider these three circuits.

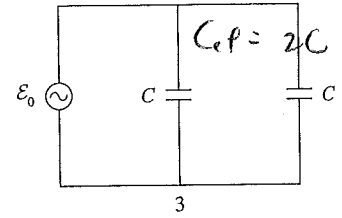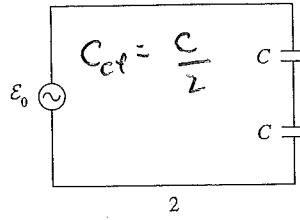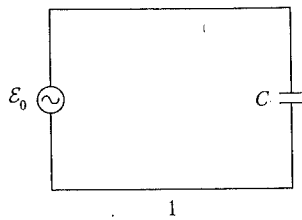

Rank in order, from largest to smallest, the peak currents $(I_C)_1$ to $(I_C)_3$ provided by the emf.

Order: 3, 1, 2
 Explanation:


9. Consider these four circuits.

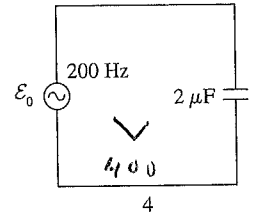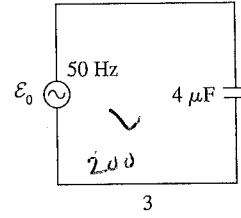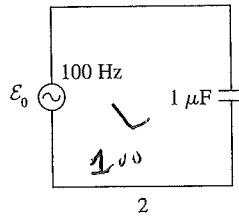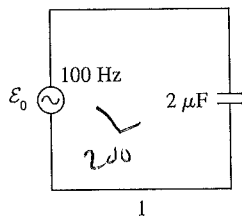

Rank in order, from largest to smallest, the capacitive reactances $(X_C)_1$ to $(X_C)_4$.

Order: 2, 1=3, 4
 Explanation:

$$X_C = \frac{1}{\omega C}$$

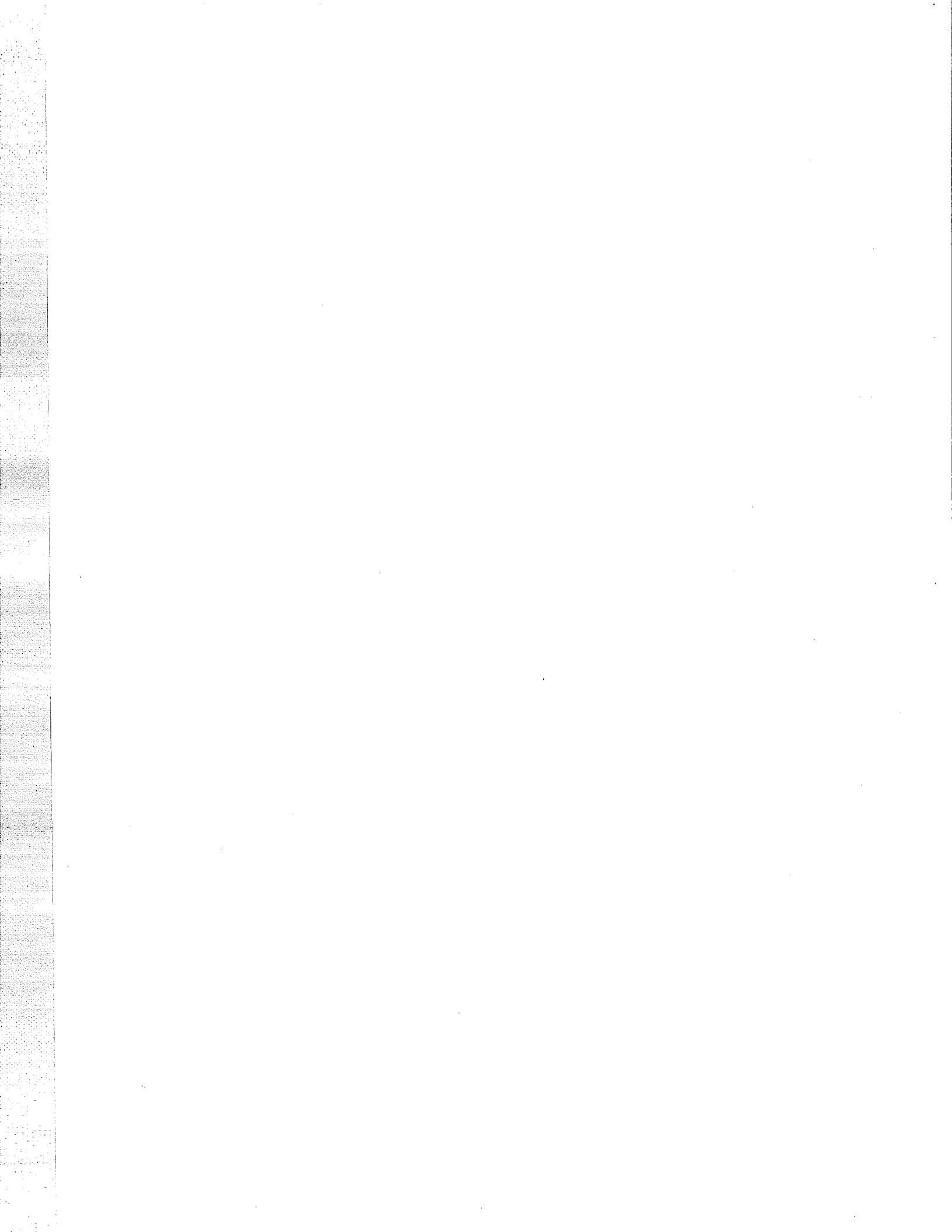

36.4 Inductor Circuits

14. The peak current passing through an inductor is 4.0 A. What is the peak current if:
 a. The peak emf \mathcal{E}_0 is doubled?

8 A. $V = IX_L$ $X_L = \omega L$
 $V = I\omega L$

- b. The inductance L is doubled?

$L \uparrow 2x$ $I \downarrow 2x$ (2 A)


- c. The frequency ω is doubled?

$\omega \uparrow 2x$ $I \downarrow 2x$ (2 A)

15. Current and voltage graphs are shown for an inductor circuit with $\omega = 1000$ rad/s.

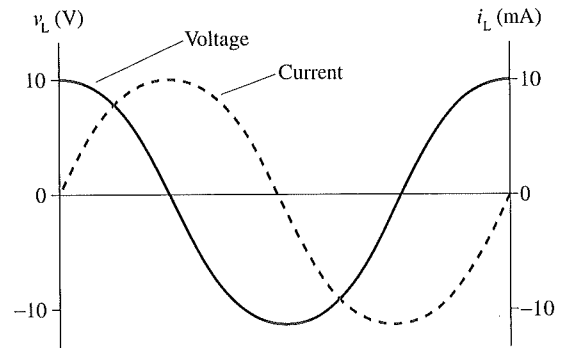- a. What is the inductive reactance X_L ?


$X_L = \frac{V}{I} = \frac{10V}{10mA} = 1k\Omega$



- b. What is the inductance L ?

$X_L = \omega L = 1000 \text{ s}^{-1} \cdot k \cdot L$
 $L = 1 \text{ H}$

16. Consider these four circuits.

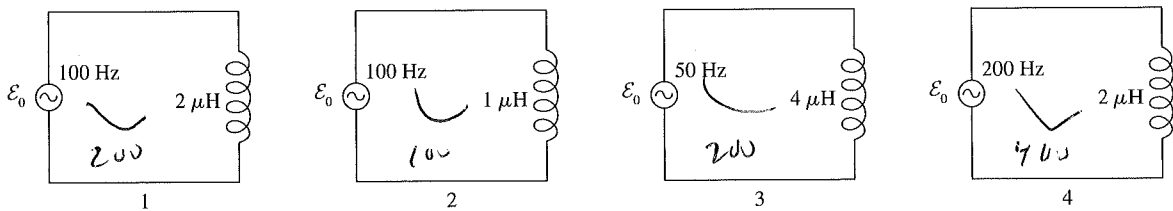

Rank in order, from largest to smallest, the inductive reactances $(X_L)_1$ to $(X_L)_4$.

Order: 4, 1=3, 2.
 Explanation:
 $X_L = \omega L$

36.5 The Series RLC Circuit

17. The resonance frequency of a series RLC circuit is 1000 Hz. What is the resonance frequency if:

a. The resistance R is doubled?

1000 Hz

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

b. The inductance L is doubled?

707 Hz

c. The capacitance C is doubled?

707 Hz

d. The peak emf \mathcal{E}_0 is doubled?

1000 Hz

e. The frequency ω is doubled?

500 Hz


18. For these combinations of resistance and reactance, is a series RLC circuit in resonance (Yes or No)? Does the current lead the emf, lag the emf, or is it in phase with the emf?

R	X_L	X_C	Resonance?
100 Ω	100 Ω	50 Ω	no
100 Ω	50 Ω	100 Ω	no
100 Ω	75 Ω	75 Ω	yes

Current?
i lags V, L dominates
i leads V, C dominates
in phase

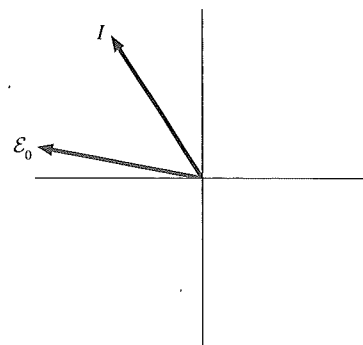19. In this series RLC circuit, is the emf frequency less than, equal to, or greater than the resonance frequency ω_0 ? Explain.


V leads i , inductor dominates.
 ωL is "too big"
 $\omega > \omega_0$



20. The resonance frequency of a series RLC circuit is greater than the emf frequency. Does the current lead or lag the emf? Explain.

ωL is too small ($< \omega_0 L$)
 $\frac{1}{\omega C}$ is too big. Cap. dominates V lags i .
 i leads V , ($\text{or } \mathcal{E}$)

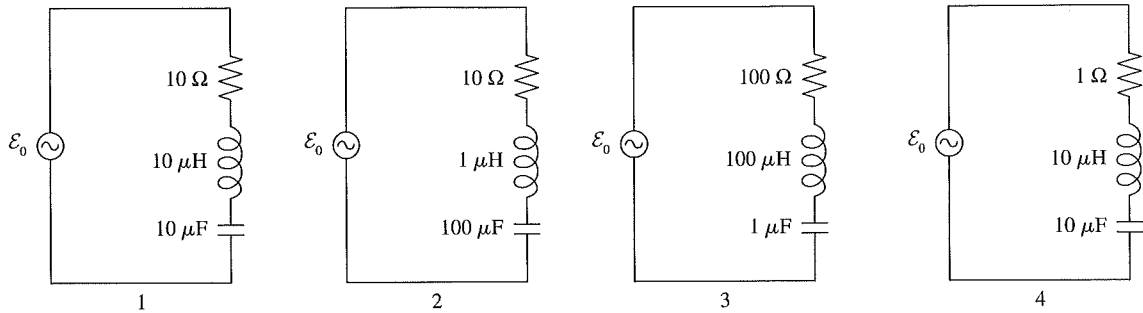21. Consider these four circuits. They all have the same resonance frequency ω_0 .



Rank in order, from largest to smallest, the maximum currents $(I_{\max})_1$ to $(I_{\max})_4$.

Order: 4, 1=2, 3

Explanation:

Smaller R , $\uparrow i$

22. The current in a series RLC circuit lags the emf by 20° . You cannot change the emf. What two different things could you do to the circuit that would increase the power delivered to the circuit by the emf?

V lags i , inductor dominates.
 you could decrease L
 or decrease C

36.6 Power in AC Circuits

23. An average power dissipated by a resistor is 4.0 W. What is P_{avg} if:

a. The resistance R is doubled?

$$P = \frac{V^2}{R} \quad R \uparrow 2x, \quad P \downarrow 2x \quad (2W)$$


b. The peak emf \mathcal{E}_0 is doubled?

$$V \uparrow 2x, \quad V^2 \uparrow 4x, \quad P \uparrow 4x \quad (16W)$$

c. Both are doubled simultaneously?

$$(8W)$$

24. Consider these three circuits.

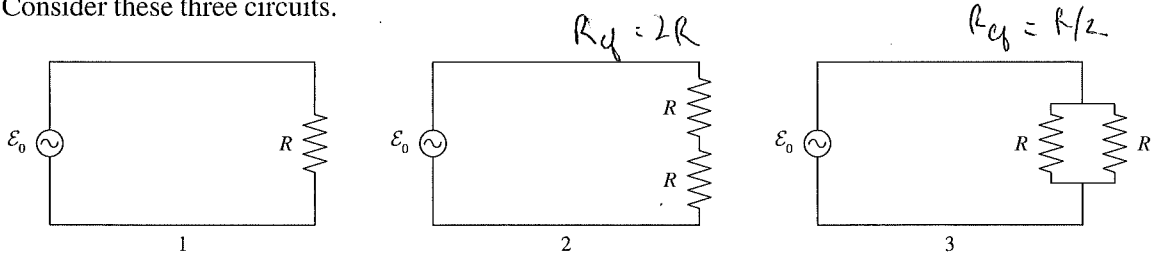

Rank in order, from largest to smallest, the average powers P_1 to P_3 delivered by the three emfs.

Order: 3, 1, 2
 Explanation: