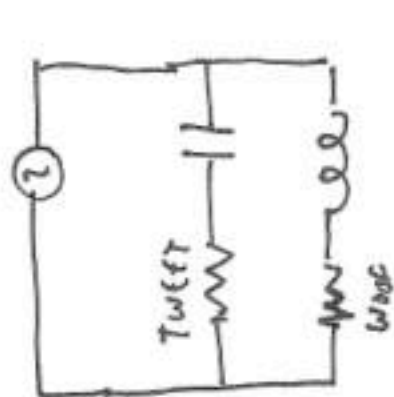


Homework 14 Solution

31.40




$$Z_T = \sqrt{\left(\frac{1}{\omega C}\right)^2 + R^2}$$

$$Z_W = \sqrt{(\omega L)^2 + R^2}$$

Currents equal when $Z_T = Z_W$ because $V = IZ$.
(in magnitude)

Crossover is $Z_T = Z_W \rightarrow \frac{1}{\omega C} = \omega L \quad \omega = \frac{1}{\sqrt{LC}}$

31.42

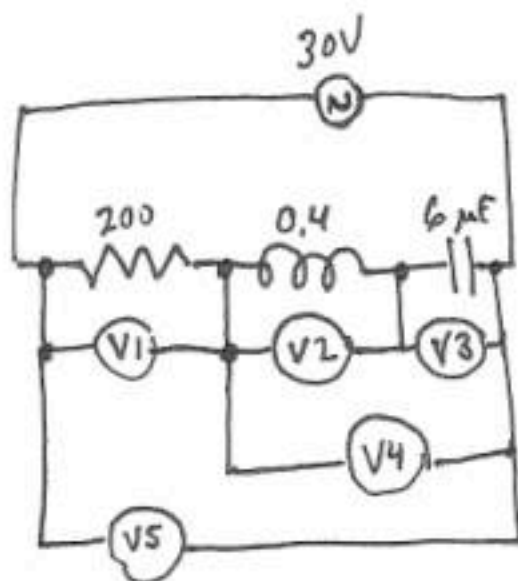

$$\omega = 200 \text{ rad/sec}$$

$$Z_{TL} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$= 779 \Omega$$

$$V = IZ \rightarrow I = 38 \text{ mA}$$

$$V_1 = IR = 7.7 \text{ V}$$

$$V_2 = IX_L = I\omega L = 3.1 \text{ V}$$

$$V_3 = IX_C = I/\omega C = 32.1 \text{ V}$$

To get
RMS
Values
 $\times \frac{1}{\sqrt{2}}$

$$V_4 = IZ_{LC} \quad Z_{LC} = \omega L - \frac{1}{\omega C} \Rightarrow V_4 = 29 \text{ V}$$

Check $29^2 + 7.7^2 = 30^2 \checkmark$