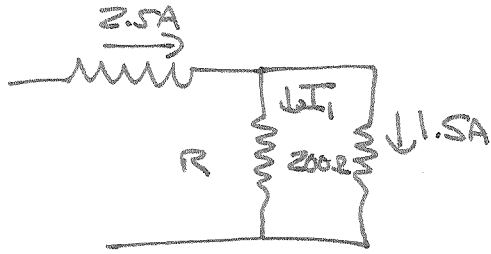


Physics 152, HW#5

Mastering Physics : 9 Questions  
from Chapter 23

Two written Questions

23.19



WHAT IS R?

By JUNCTION RULE:  $I_1 + 1.5A = 2.5A$


$$\Rightarrow I_1 = 1A$$

R AND  $200\Omega$  RESISTOR ARE IN PARALLEL  $\Rightarrow \Delta V_1 = \Delta V_2$

$$\Delta V = IR \Rightarrow \Delta V_1 = (1.5A)(200\Omega) = 300V$$


$$\Delta V_1 = I_1 R \Rightarrow R = \frac{\Delta V_1}{I_1} = \frac{300V}{1A} = 300\Omega$$

23. <sup>55</sup>~~56~~

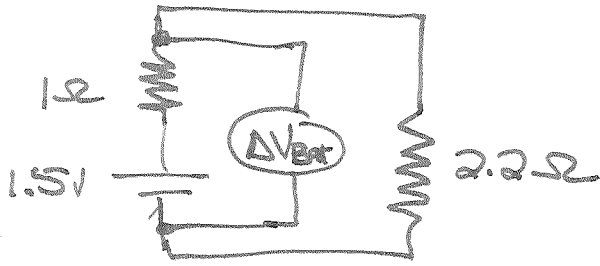

$$\Delta V_{\text{Bat}} = ?$$

Label Points as shown:

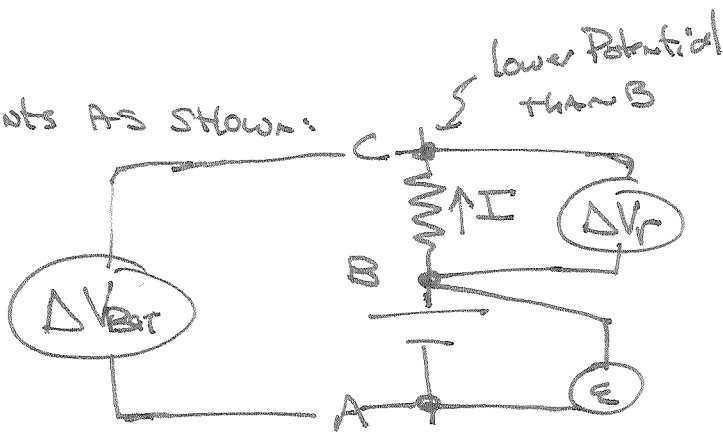

$$\Delta V_{\text{Bat}} = V_C - V_A$$

$$\Delta V_r = V_B - V_C$$

$$\mathcal{E} = V_B - V_A$$

$$\Rightarrow \mathcal{E} - \Delta V_r = V_C - V_A$$
$$= \Delta V_{\text{Bat}}$$

By Ohm's Law  $\Delta V_r = I r = I (2.2 \Omega)$

$$\Rightarrow \Delta V_{\text{Bat}} = \mathcal{E} - I (1 \Omega)$$

To Find  $I$ :  $R_{\text{eq}} = 1 \Omega + 2.2 \Omega = 3.2 \Omega$

$$\therefore I = \frac{\mathcal{E}}{R_{\text{eq}}} = \frac{1.5 \text{ V}}{3.2 \Omega} = 0.46875 \text{ A}$$

$$\therefore \Delta V_{\text{Bat}} = 1.5 \text{ V} - 0.46875 \text{ A} (1 \Omega) = 1.03125 \text{ V} = 1.0 \text{ V}$$

b) WHAT FRACTION Dissipated?  $\frac{\Delta P}{P} = ?$


$\Delta P$  = Power used by INTERNAL Resistance

$$P_R = I^2 R \Rightarrow \Delta P = (0.46875 \text{ A})^2 (1 \Omega) = 0.2197 \text{ watt}$$

$$P = \text{Power supplied by EMF} \Rightarrow P_{\text{EMF}} = I \mathcal{E} = (0.46875 \text{ A})(1.5 \text{ V}) \\ = 0.703125 \text{ watt}$$

$$\therefore \frac{\Delta P}{P} = \frac{0.2197 \text{ watt}}{0.703125 \text{ watt}} = 0.31246 \times 100\% = 31.246\% \\ = 31\%$$

23.23

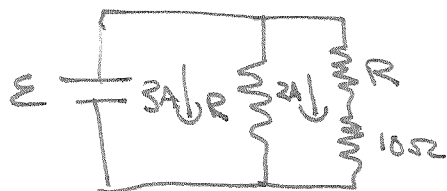

a) what is R?

THE Resistor R on the left AND THE R/10\Omega Combo on the RIGHT ARE in parallel with battery

$$\Rightarrow \Delta V_1 = \Delta V_2 = \mathcal{E}$$

$$\Delta V_p = IR \Rightarrow \Delta V_1 = (3A)R, \quad \Delta V_2 = (2A)(\underbrace{R+10\Omega}_{\text{Series}}) = 2A R + 20V$$


$$\Rightarrow (3A)R = (2A)R + 20V \Rightarrow [(3A-2A)]R = 20V$$

$$\Rightarrow (1A)R = 20V \Rightarrow R = \frac{20V}{1A} = 20\Omega$$

$$b) \mathcal{E} = \Delta V_1 = (3A)R = (3A)(20\Omega) = 60V$$

$$\text{If you prefer: } \mathcal{E} = \Delta V_2 = (2A)(R+10\Omega) = (2A)(20\Omega+10\Omega) \\ = (2A)(30\Omega) = 60V$$

# Heating A Water Bath :

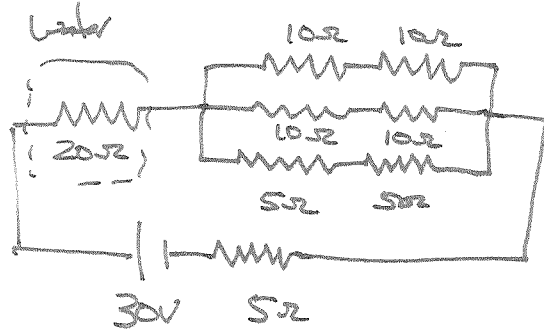

$$m = 10\% \times \frac{\text{kg}}{1000} = 0.104 \text{ kg}$$

Water at  $T_i = 10.7^\circ\text{C}$


How long until  $T_f = 58.7^\circ\text{C}$

$$\text{Heat} = mc\Delta T$$

Heat Supplied by 20Ω Resistor

$$P_R = I^2 R \Rightarrow \text{Need Current through it}$$

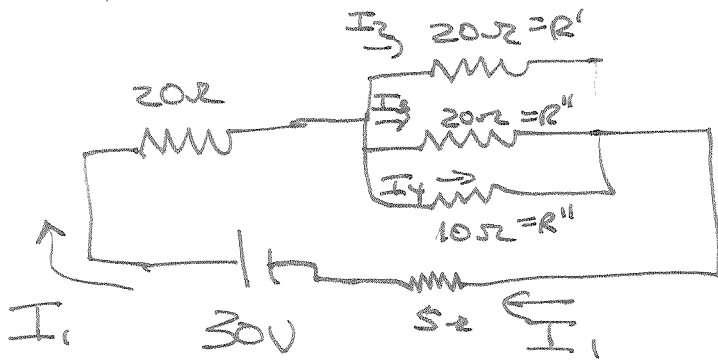Luckily 20Ω Connected in Series to battery  $\Rightarrow$  Find  $R_{eq}$



Notice I used Series


Formulas to simplify

$R', R'', R'''$  in ~~Series~~ Parallel

$$\Rightarrow \frac{1}{R^{(4)}} = \frac{1}{R'} + \frac{1}{R''} + \frac{1}{R'''} = \frac{1}{20\Omega} + \frac{1}{20\Omega} + \frac{1}{10\Omega} = \frac{4}{20\Omega} = \frac{1}{5\Omega}$$

$$\Rightarrow \frac{1}{R^{(4)}} = \frac{1}{20\Omega} + \frac{1}{20\Omega} + \frac{1}{10\Omega} = \frac{1}{20\Omega} + \frac{1}{20\Omega} + \frac{2}{20\Omega} = \frac{4}{20\Omega} = \frac{1}{5\Omega}$$

$$\Rightarrow R^{(4)} = 5\Omega$$

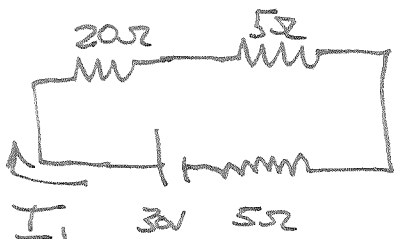

$$R_{eq} = 20\Omega + 5\Omega + 5\Omega = 30\Omega$$


$$I_1 = \frac{V}{R_{eq}} = \frac{30V}{30\Omega} = 1A$$

$$P_R = I_1^2 R_1 = (1A)^2 (20\Omega) = 20 \text{ watt} = 20 \text{ J/s}$$

$$P_R = \frac{\text{Heat}}{\Delta t} \quad \text{Heat} = mc \Delta T = (0.104 \text{ kg}) (4190 \frac{\text{J}}{\text{kg} \cdot ^\circ\text{C}}) (58.7^\circ\text{C} - 10.7^\circ\text{C})$$
$$= (0.104 \text{ kg}) (4190 \frac{\text{J}}{\text{kg} \cdot ^\circ\text{C}}) (48^\circ\text{C}) =$$
$$20916.48 \frac{\text{J}}{\text{watt}}$$

$$20 \text{ J/s} = \frac{20916.48 \text{ J}}{\Delta t} \Rightarrow \Delta t = \frac{20916.48 \text{ J}}{20 \text{ J/s}} = 1045.824 \text{ s}$$
$$= 1050 \text{ s}$$


23.68

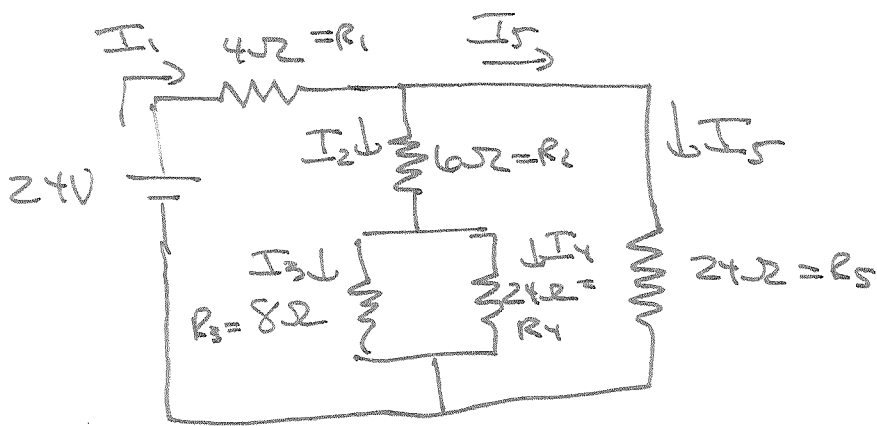

label currents as shown.


$R_1$  in series with battery
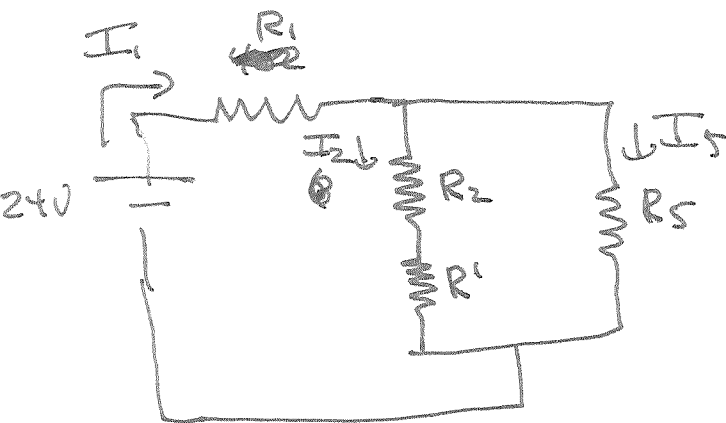
$$R_3 \text{ \& } R_4 \text{ in parallel} \Rightarrow R' = \frac{R_3 R_4}{R_3 + R_4} = \frac{(8\Omega)(24\Omega)}{(8\Omega + 24\Omega)} = \frac{192\Omega^2}{32\Omega} = 6\Omega$$



$R_2$  +  $R'$  in series
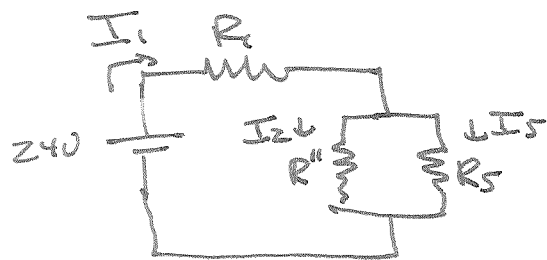
$$\Rightarrow R'' = R_2 + R' = 6\Omega + 6\Omega = 12\Omega$$




$R''$  +  $R_5$  in parallel  $\Rightarrow$

$$R''' = \frac{R'' R_5}{R'' + R_5} = \frac{(12\Omega)(24\Omega)}{(12\Omega + 24\Omega)} = \frac{288\Omega^2}{36\Omega}$$

$$= 8\Omega$$




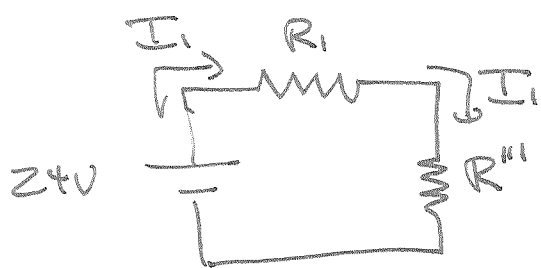

Series  $\Rightarrow$

$$R_{eq} = R_1 + R'' = 4\Omega + 8\Omega = 12\Omega$$
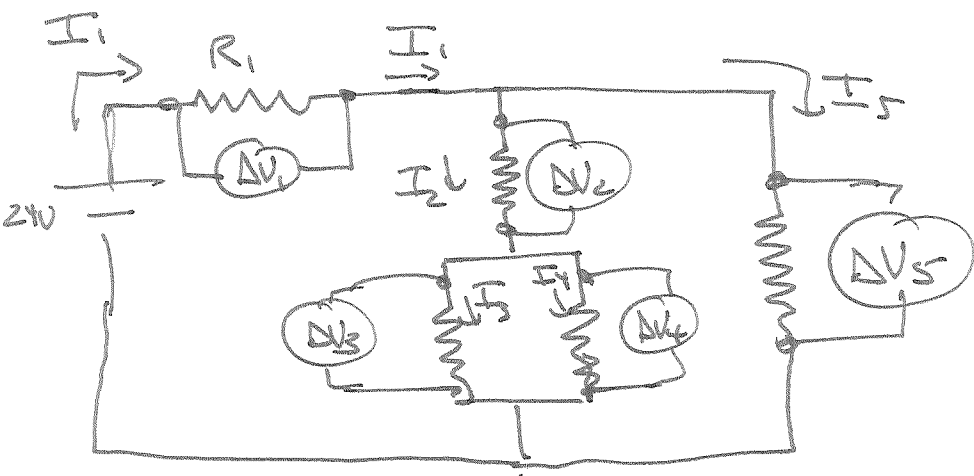
$$I_1 = \frac{\mathcal{E}}{R_{eq}} = \frac{24V}{12\Omega} = 2A$$



$$DV_1 = I_1 R_1 = (2A)(4\Omega) = 8V$$

A little checking shows  $DV_1 + DV_5 = \mathcal{E} \Rightarrow DV_5 = \mathcal{E} - DV_1 = 24V - 8V = 16V$

$$DV_5 = I_5 R_5 \Rightarrow I_5 = \frac{DV_5}{R_5} = \frac{16V}{\cancel{24\Omega}} = 0.666\dots A = \frac{2}{3}A$$

Junction Rule:  $I_1 = I_2 + I_5 \Rightarrow I_2 = I_1 - I_5 = 2A - \frac{2}{3}A = \frac{4}{3}A = 1.333A$

$$DV_2 = I_2 R_2 = \left(\frac{4}{3}A\right)(6\Omega) = 8V$$

A little more checking shows  $\Delta V_1 + \Delta V_2 + \Delta V_3 = \mathcal{E}$

$$\Rightarrow \Delta V_3 = \mathcal{E} - \Delta V_1 - \Delta V_2 = 24V - 8V - 8V = 8V$$


$$\Delta V_3 = I_3 R_3 \Rightarrow I_3 = \frac{\Delta V_3}{R_3} = \frac{8V}{8\Omega} = 1A$$

$$\Delta V_4 = \Delta V_3 \text{ since Parallel, } I_4 = \frac{\Delta V_4}{R_4} = \frac{8V}{24\Omega} = \frac{1}{3}A = 0.\overset{33}{3}A$$

So IN SUMMARY:

	$I_i$	$\Delta V_i$
$R_1$	2A	8V
$R_2$	$\frac{4}{3}A = 1.3A$	8V
$R_3$	1A	8V
$R_4$	$\frac{1}{3}A = 0.33A$	8V
$R_5$	$\frac{2}{3}A = 0.67A$	16V

23.21

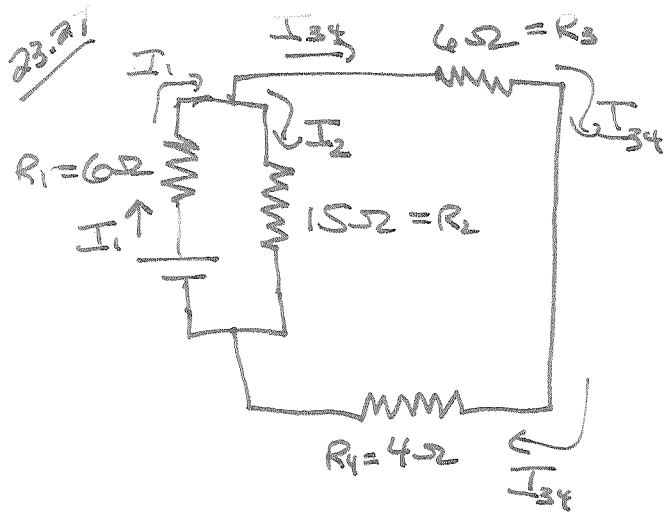

This is DRAWN STRANGET,  
Labeling Currents as shown helps

$R_3$  &  $R_4$  ARE IN SERIES


$R_1$  IN SERIES WITH BATTERY

Current then splits to go through  $R_2$  AND


$R_3/R_4$ . FINGER TEST  $\rightarrow R_2$

IN PARALLEL WITH  $R_3/R_4$

So a better picture is:

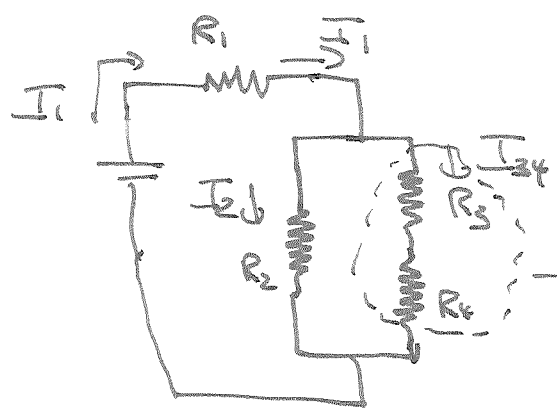

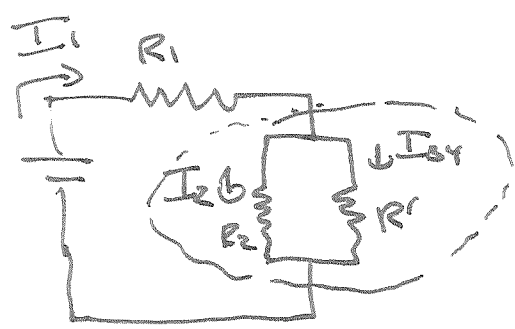
$$R' = R_3 + R_4 = 6\Omega + 4\Omega = 10\Omega$$



$$R'' = \frac{R_2 R'}{R_2 + R'}$$

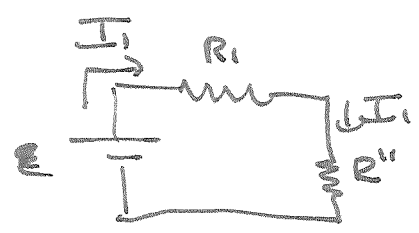
$$R'' = \frac{(15\Omega)(10\Omega)}{(15\Omega + 10\Omega)} = \frac{150\Omega^2}{25\Omega} = 6\Omega$$



$$R_{EQ} = R_1 + R'' = 6\Omega + 6\Omega = 12\Omega$$

$$I_1 = \frac{\mathcal{E}}{R_{EQ}} = \frac{24V}{12\Omega} = 2A$$

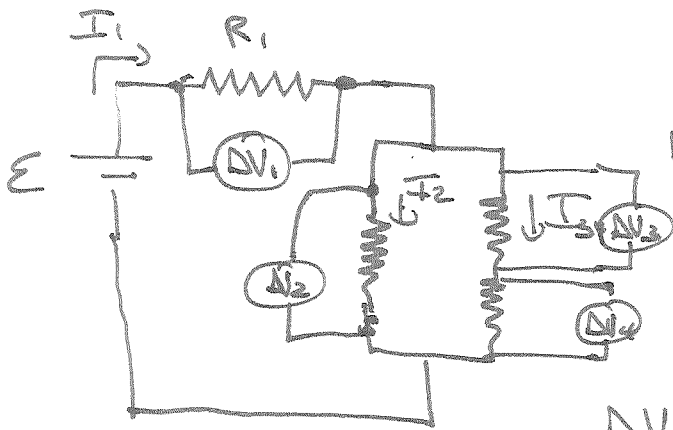Now Find  $\Delta V_1 = I_1 R_1$      $\Delta V_1 = (2A)(6\Omega) = 12V$



$$\Delta V_1 + \Delta V_2 = \varepsilon \Rightarrow \Delta V_2 = \varepsilon - \Delta V_1$$

$$\Delta V_2 = 24V - 12V = 12V$$

$$\Delta V_2 = I_2 R_2 \Rightarrow I_2 = \frac{\Delta V_2}{R_2} = \frac{12V}{15\Omega} = 0.8A$$

Junction Rule:  $I_1 = I_2 + I_{3+4} \Rightarrow I_{3+4} = I_1 - I_2 = 2A - 0.8A = 1.2A$

$$\Delta V_3 = I_{3+4} R_3 = (1.2A)(6\Omega) = 7.2V$$


$$\Delta V_4 = I_{3+4} R_4 = (1.2A)(4\Omega) = 4.8V$$

} Notice  $\Delta V_3 + \Delta V_4 = 12V = \Delta V_2$   
 Since they're in parallel

In summary:

	$I_i$	$\Delta V_i$
$R_1$	2A	12V
$R_2$	0.8A	12V
$R_3$	1.2A	7.2V
$R_4$	1.2A	4.8V

23.29

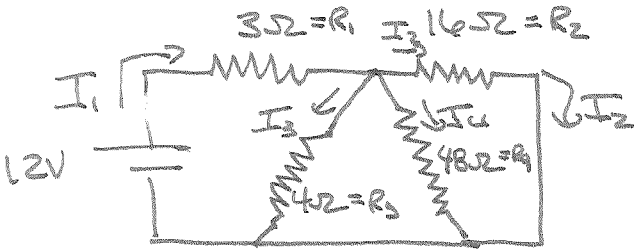

Again, STRANGELY DRAWN

Label Currents AS SHOWN


Current From Battery must go

through  $R_1 \Rightarrow I_1$  in series.

$I_1$  then splits into 3

Finger test shows  $R_2, R_3, R_4$  in Parallel


So A Better DRAWING:

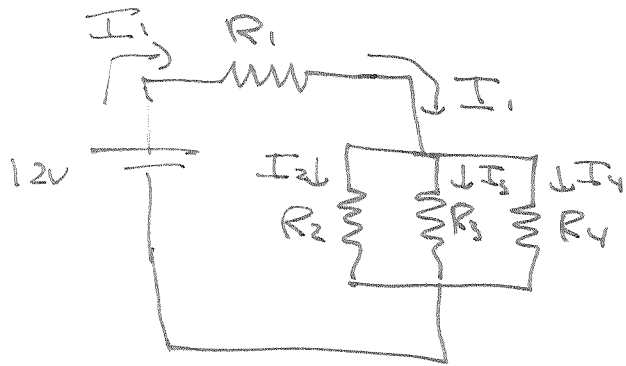

$$\text{IN Parallel} \Rightarrow \frac{1}{R'} = \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$


$$\Rightarrow \frac{1}{R'} = \frac{1}{16\Omega} + \frac{1}{4\Omega} + \frac{1}{48\Omega} = \frac{3}{48\Omega} + \frac{12}{48\Omega} + \frac{1}{48\Omega}$$
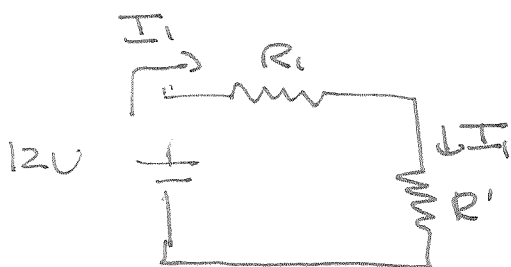
$$\Rightarrow \frac{1}{R'} = \frac{16}{48\Omega} = \frac{1}{3\Omega} \Rightarrow R' = 3\Omega$$



$$\text{Series} \Rightarrow R_{EQ} = R_1 + R' = 3\Omega + 3\Omega = 6\Omega$$
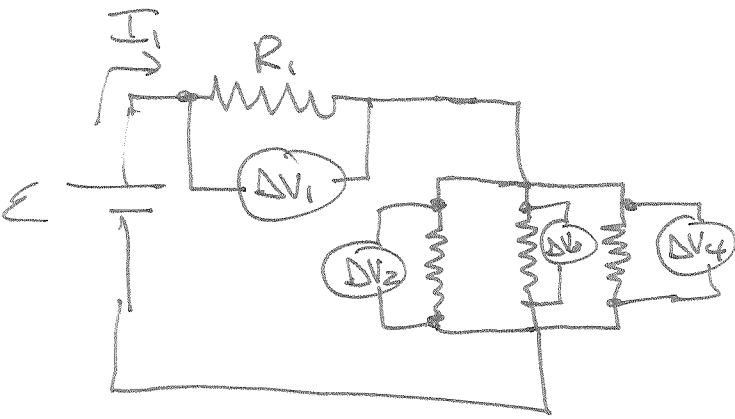
$$I_1 = \frac{\mathcal{E}}{R_{EQ}} = \frac{12V}{6\Omega} = 2A$$



$$\Delta V_1 = I_1 R_1 = (2A)(3\Omega) = 6V$$

$$\text{Parallel} \Rightarrow \Delta V_2 = \Delta V_3 = \Delta V_4$$

$$\Delta V_1 + \Delta V_2 = \varepsilon \Rightarrow \Delta V_2 = \varepsilon - \Delta V_1$$

$$\Rightarrow \Delta V_2 = 12V - 6V = 6V$$


$$\Delta V_2 = I_2 R_2 \Rightarrow I_2 = \frac{\Delta V_2}{R_2} = \frac{6V}{16\Omega} = 0.375A = 0.38A$$

$$I_3 = \frac{\Delta V_3}{R_3} = \frac{6V}{4\Omega} = 1.5A$$

$$I_4 = \frac{\Delta V_4}{R_4} = \frac{6V}{48\Omega} = 0.125A = 0.13A$$

Notice how  $I_2 + I_3 + I_4 = I_1$  As Junction Rule Requires

23.52

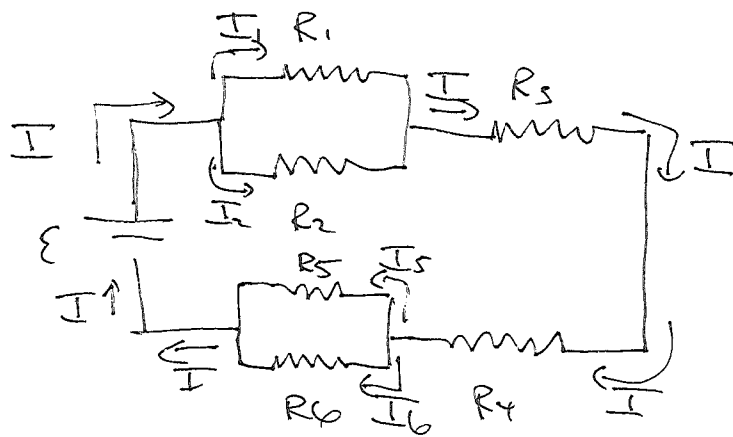

$$R_1 = 50\Omega$$

$$R_2 = 35\Omega$$

$$R_3 = 45\Omega$$

$$R_4 = 70\Omega$$

$$R_5 = 25\Omega$$

$$R_6 = 35\Omega$$

$$\text{MAX power, } P_{\text{max}} = 0.6 \text{ Watt}$$

a.) Which Resistor uses the most power?

It's kind of tricky but  $R_3$  &  $R_4$  are in series with the battery.

The current entering the first junction is the same as the battery's.

Junction Rule  $\Rightarrow I_1 + I_2 = I \Rightarrow$  SAME current  $I$  going through  $R_3$  AND  $R_4$ .

At the other junction, we get  $I_5 + I_6 = I$

~~$I_1 + I_2 = I$~~   $\Rightarrow$  Current through  $R_1$  &  $R_2$  smaller than current through  $R_3$  &  $R_4$

$I_5 + I_6 = I \Rightarrow$  Current through  $R_5$  &  $R_6$  smaller than current through  $R_3$  &  $R_4$

$P = I^2 R \Rightarrow$  Resistor with LARGEST current and RESISTANCE value uses most power.  $R_4 = 70\Omega$  is LARGEST Resistor and has the largest current  $\Rightarrow$  uses most power.

b.) What is MAX Current From battery?

Since  $R_4$  is using the most power, ~~then~~ if it's using the MAX then everybody else is using less.

$$P = I^2 R \Rightarrow P_{\text{MAX}} = \underset{\substack{\uparrow \\ \text{Current} \\ \text{through } R_4}}{I^2} R_4$$

but since  $R_4$  in Series with battery  $I_4 = I$


$$\Rightarrow P_{\text{MAX}} = I^2 R_4 \Rightarrow I^2 = \frac{P_{\text{MAX}}}{R_4} \Rightarrow I = \sqrt{\frac{P_{\text{MAX}}}{R_4}} = \sqrt{\frac{0.6 \text{ watt}}{70 \Omega}}$$

$$\Rightarrow I = 0.0926 \text{ A} \quad \left( \text{Unit: } \frac{\text{Watt}}{\Omega} = \frac{\text{J/s}}{\text{V/A}} = \frac{\text{J/s}}{\text{J/C}} \cdot \text{A} = \frac{\text{C}}{\text{s}} \cdot \text{A} = \text{A} \cdot \text{A} = \text{A}^2 \right)$$

$\sqrt{\text{A}^2} = \text{A}$

c.) What is MAX emf?

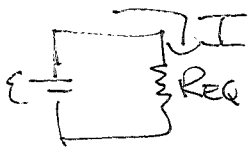
$I = \text{Current From battery} \Rightarrow \text{Also Current in Equivalent Circuit}$



$$\varepsilon = I R_{\text{EQ}} \Rightarrow \text{FIND EQUIVALENT RESISTANCE}$$

$$R_1 \& R_2 \text{ in parallel} \Rightarrow R' = \frac{R_1 R_2}{R_1 + R_2} = \frac{(50 \Omega)(35 \Omega)}{(50 \Omega + 35 \Omega)} = 20.588 \Omega$$
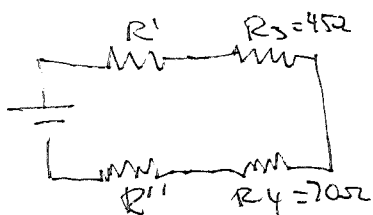
$$R_5 \& R_6 \text{ in parallel} \Rightarrow R'' = \frac{R_5 R_6}{R_5 + R_6} = \frac{(25 \Omega)(35 \Omega)}{(25 \Omega + 35 \Omega)} = 14.583 \Omega$$




$$\text{Series} \Rightarrow R_{\text{EQ}} = R' + R_3 + R_4 + R'' = 150.171 \Omega$$

$$\Rightarrow \varepsilon = I R_{\text{EQ}} = (0.0926 \text{ A})(150.171 \Omega) = 13.9 \text{ V} = \underline{14 \text{ V}}$$



# Written Question #1

a)

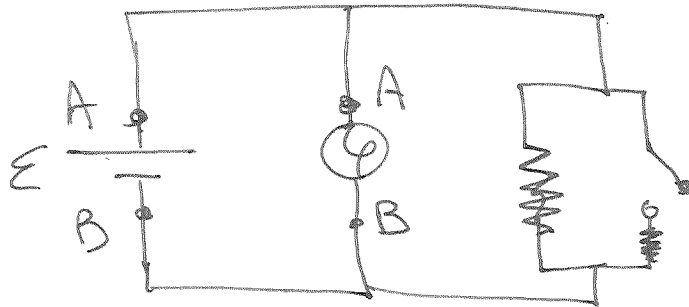

WHAT HAPPENS TO LIGHT BULB WHEN SWITCH CLOSED?

THE LIGHT BULB IS CONNECTED IN PARALLEL TO THE BATTERY. <sup>SINCE</sup> AS SHOWN,  $V_{LB} = V_A - V_B$  AND  $\epsilon = V_A - V_B$ .  
↑  
LIGHT BULB


CLOSING THE SWITCH HAS NO EFFECT ON THIS. SO

$P_{LB} = \frac{DV_{LB}^2}{R_{LB}}$  TELLS US THAT THE POWER DISSIPATED

BY THE LIGHT BULB STAYS THE SAME  $\Rightarrow$  STAYS THE SAME BRIGHTNESS


$$P_{LB} = \frac{\overset{\text{CONSTANT}}{\epsilon^2}}{\underset{\text{CONSTANT}}{R_{LB}}}$$

b.)

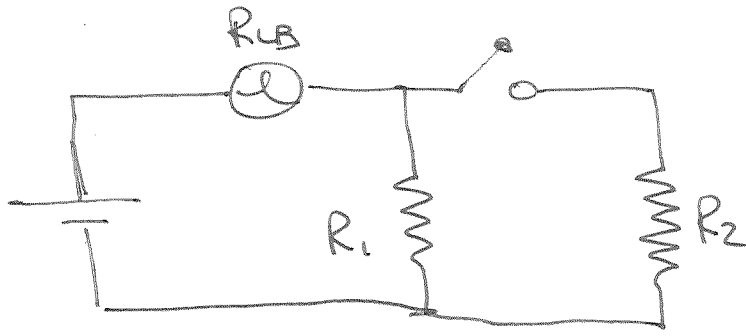


WHAT HAPPENS TO LIGHTBULB WHEN SWITCH CLOSED?

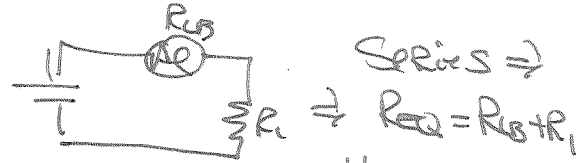WITH SWITCH OPEN  $R_2$  IS NOT IN CIRCUIT  $\Rightarrow$




CLOSING THE SWITCH ADDS A RESISTOR  $R_2$  IN PARALLEL

TO  $R_1$  SINCE

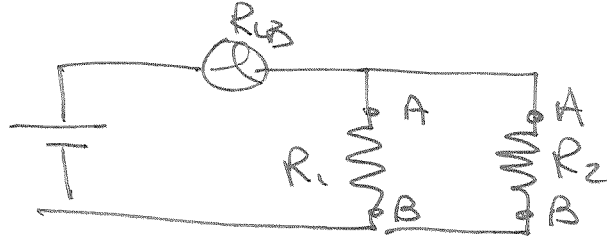

$$\Delta V_1 = \Delta V_2 = V_A - V_B$$

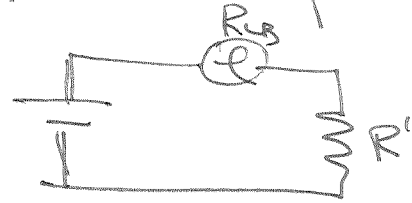THE EQUIVALENT RESISTANCE OF RESISTORS IN PARALLEL IS SMALLER THAN INDIVIDUAL VALUES  $\Rightarrow$




WHERE  $R'$  IS SMALLER THAN  $R_1$

① LIGHTBULB AND  $R'$  IN SERIES  $\Rightarrow R_{EQ} = R_{LB} + R'$  SO SINCE  $R'$  SMALLER THAN  $R_1$ , THE EQUIVALENT RESISTANCE IS SMALLER WITH SWITCH CLOSED.  $\Rightarrow$  CURRENT FROM BATTERY INCREASES

THE LIGHTBULB IS CONNECTED IN SERIES TO THE BATTERY

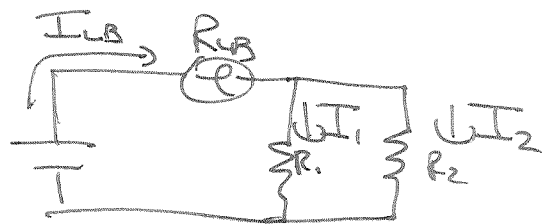
(WITH SWITCH OPEN OR CLOSED)  $\Rightarrow$  MUST HAVE SAME AMOUNT OF CURRENT THROUGH LIGHTBULB AND BATTERY.



SO MORE CURRENT FROM BATTERY  $\Rightarrow$  MORE CURRENT THROUGH LIGHTBULB.

$$P_{LB} = I^2 R_{LB} \Rightarrow \text{MORE POWER} \Rightarrow \text{BRIGHTER}$$

#2  
~~#1~~

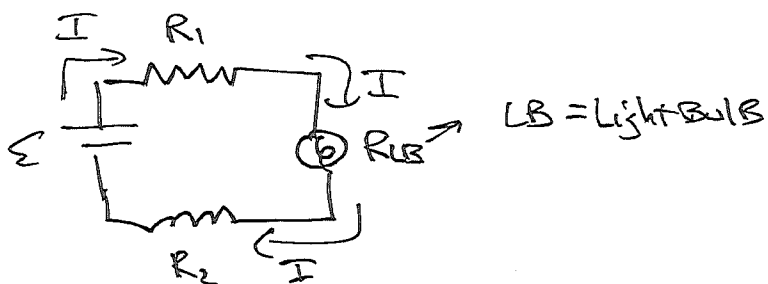

a.) ADD ONE RESISTOR to Circuit to make lightbulb DIMMER.


initially, All 3 are in Series  $\Rightarrow R_{EQ} = R_1 + R_L + R_2$

$$\text{AND } I = \frac{\epsilon}{R_{EQ}}$$

To MAKE lightbulb DIMMER, we need to make  $R_{EQ}$  LARGER


AND keep lightbulb in Series with Battery so that the smaller current coming out of battery  $\Rightarrow$  smaller current through bulb.

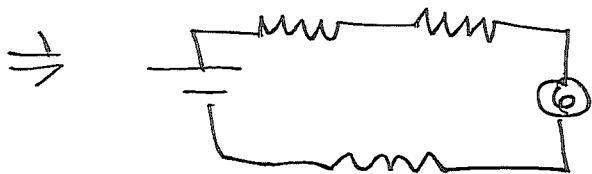$R_{EQ}$  becomes LARGER by adding another resistor in series




b.) MAKE BRIGHTER  $\rightarrow$  SAME BASIC IDEA <sup>but</sup> we want to make  $R_{EQ}$  smaller while keeping lightbulb in series with Battery.  $\Rightarrow$  ADD Resistor in parallel to one of the resistors AND NOT the lightbulb.

(SEE next page)

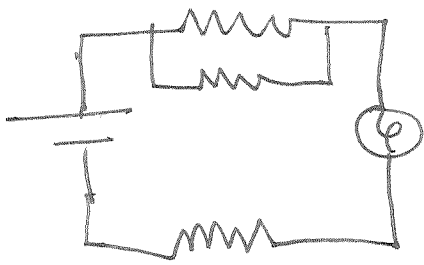


OR

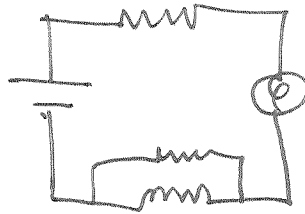

Makes  $R_{EQ}$  smaller  
 AND light bulb in  
 series with battery  
 $\Rightarrow$  More current through  
 light bulb  $\Rightarrow$  brighter

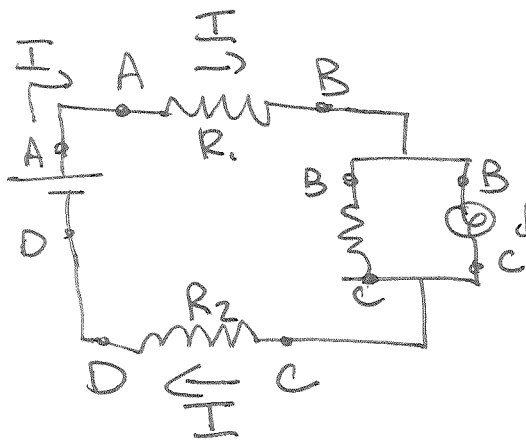But Adding Resistor to light bulb will make it dimmer!



$\Delta V_1 = V_A - V_B = IR_1$ ,  $\Delta V_2 = V_C - V_D = IR_2$

while  $\Delta V_{LB} = V_B - V_C$

↑  
Lightbulb

Notice THAT  $\Delta V_1 + \Delta V_{LB} + \Delta V_2 = V_A - V_B + V_B - V_C + V_C - V_D = \mathcal{E}$

$\Rightarrow \Delta V_{LB} = \mathcal{E} - \Delta V_1 - \Delta V_2$  (Resistors  $R_1$  &  $R_2$  in series with battery  $\Rightarrow$  current through them must also increase)

Ohm's LAW  $\Rightarrow \Delta V_1 = IR_1$ ,  $\Delta V_2 = IR_2$ . When we ADD a Resistor in parallel, THE AMOUNT OF current <sup>I</sup> DOES INCREASE

But SO DOES  $\Delta V_1$  AND  $\Delta V_2$ .  $\Delta V_1 = IR_1$ ,  $\Delta V_2 = IR_2$ . SINCE  $\mathcal{E}$  is constant,


INCREASING  $\Delta V_1$  AND  $\Delta V_2$  MEANS THAT  $\Delta V_{LB}$  must decrease

$\circ$  SINCE  $\Delta V_{LB} = \mathcal{E} - \Delta V_1 - \Delta V_2$

$P_{LB} = \frac{\Delta V_{LB}^2}{R_{LB}} \Rightarrow$  Less power for light bulb  $\Rightarrow$  DIMMER

c.) Keep BRightness the same.

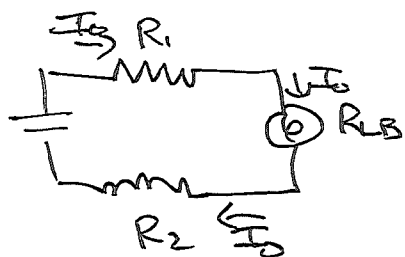(IN ORDER to keep lightBULB the same we need to keep the CURRENT Flowing through it the same.



$$R_{EQ} = R_1 + R_B + R_2 \Rightarrow I_0 = \frac{\mathcal{E}}{R_1 + R_B + R_2}$$

$\Rightarrow$  we need to keep the VOLTAGE ACROSS the COMBINATION EQUAL to the battery's EMF

$\Rightarrow$  ADD New Resistor in parallel to Battery that way the VOLTAGE ACROSS the ORIGINAL combo stays the same.

